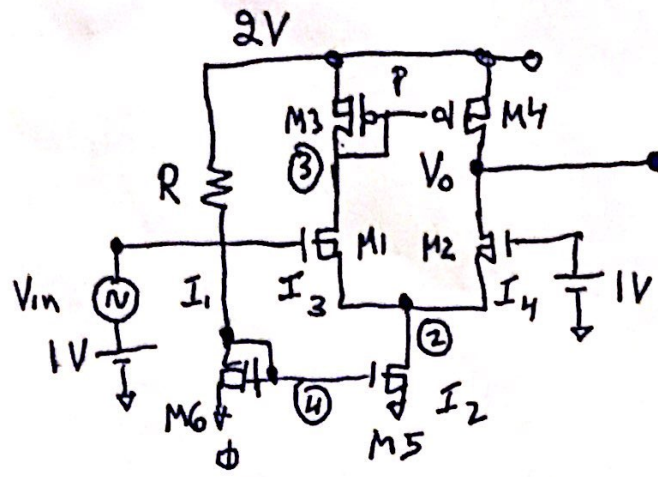


You design

20%



① given:  $\mu_n C_{ox} = 150 \text{ E-}6 \frac{\text{A}}{\text{V}^2}$   $\frac{1}{\lambda_p} = \frac{1}{\lambda_n} = 20\text{V}$   
 $\mu_p C_{ox} = 50 \text{ E-}6 \frac{\text{A}}{\text{V}^2}$   
 $V_{TP} = V_{TN} = 0.5\text{V}$

A) you choose  $R$ ,  $\frac{W}{L}$  (all M's) <sup>MICRONS</sup>

IF  $V_{in} = \phi$  Find operating Voltages and Currents

$V_{(3)}, V_{(2)}, V_{(4)} = ?$   
 $I_2, I_3, I_4, I_1 = ?$

- can ignore  $\lambda$ 's  
 - assume  $V_o = 1\text{V}$

② Sketch To Small Signal <sup>diagram</sup> eq. Circuit (use  $\lambda = 0$  for M5)  
 using  $g_m, R_o$

Find the gain  $\frac{V_o}{V_{in}} = ?$  in eq FORM  
 in value

③ please draw The Layout of This ~~ANST~~ circuit (relatively scale) including metal connections, label M's, use  $R = 1\text{k}\Omega$

④ Make any comments on your work choices you like