



Welcome to
046188 Winter semester 2013
Mixed Signal Electronic Circuits
Instructor: Dr. M. Moyal

Lecture 03 (part b)
(1st ½ and back to lect. 2 continue what we did not finished)

FLASH ADC

Agenda - you will get familiar with


www.gigalogchip.com

Flash ADCs – no error sources


Summary lect. 01,02



Physical model

 


Small signal

 

Linear region	$V_{GS} > V_{TH}$	$V_{DS} < V_{GS} - V_{TH}$
	$I_D = \mu \cdot C_{ox} \cdot \frac{W}{L} \cdot \left[(V_{GS} - V_{TH}) \cdot V_{DS} - \frac{1}{2} V_{DS}^2 \right]$	
	$g_m = \mu \cdot C_{ox} \cdot \frac{W}{L} \cdot V_{DS}$	
	$g_{ds} = \mu \cdot C_{ox} \cdot \frac{W}{L} \cdot (V_{GS} - V_{TH} - V_{DS})$	
Saturation region	$V_{GS} > V_{TH}$	$V_{DS} > V_{GS} - V_{TH}$
	$I_D = \frac{1}{2} \cdot \mu \cdot C_{ox} \cdot \frac{W}{L} \cdot (V_{GS} - V_{TH})^2 \cdot (1 + \lambda \cdot V_{DS})$	
	$g_m = \mu \cdot C_{ox} \cdot \frac{W}{L} \cdot (V_{GS} - V_{TH}) = \sqrt{2 \cdot \mu \cdot C_{ox} \cdot \frac{W}{L} \cdot I_D} = \frac{2 \cdot I_D}{V_{GS} - V_{TH}}$	
	$g_{ds} = \frac{\lambda \cdot I}{L}$	$r_{ds} = \frac{L}{\lambda \cdot I}$



[B]

 It is assumed that the quantization noise exhibits a white spectrum



The power-of-noise spectral density is:
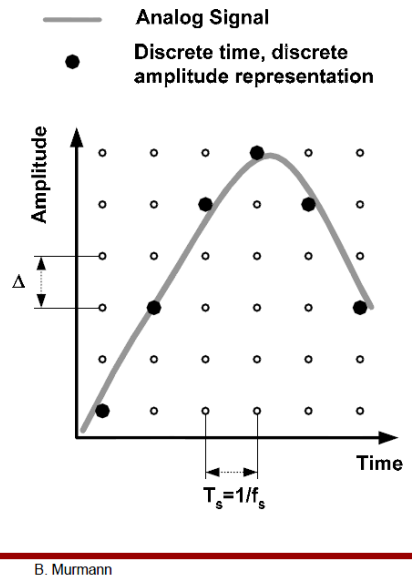 
$$n_0^2(f) = \frac{\Delta^2}{12 \cdot \frac{F_s}{2}}$$



B. Murmann

Quantization error

Small signal

Small Signal Equivalent Circuit –Capacitances

linear

$$C_i = C_{ox} \cdot WL$$

$$C_{dep} = \frac{\epsilon_{sl}}{X_{dep}} \cdot WL$$

$$C_{gs} = C_{gs,ov} + \frac{C_i}{2}$$

$$C_{gd} = C_{gd,ov} + \frac{C_i}{2}$$

$$C_{sb} = C_{js} + \frac{C_{dep}}{2}$$

$$C_{db} = C_{jd} + \frac{C_{dep}}{2}$$


saturation

$$C_{gs} = C_{gs,ov} + \frac{2}{3} C_i; \quad C_{gd} = C_{gd,ov}$$

$$C_{sb} = C_{js} + \frac{2}{3} C_{dep}; \quad C_{db} = C_{jd}$$


$$C_{gb} = \frac{1}{10} C_i$$

$$C_j = \frac{C_{jp}}{\sqrt{1 - \Phi_T}}$$
 
$$\Phi_T = \frac{kT}{q} \ln \left(\frac{N_D N_A}{n_i^2} \right)$$


wi : weak inversion
 
$$I_{DSwi} = I_{D0} \frac{W}{L} \exp \frac{V_{GS}}{n k T / q}$$



2003 → 6b & 2Gs/s (180nm CMOS)

2004 → 6b & 300Ms/s (0.25um CMOS)

2005 → 6b & 1.2Gs/s (130nm CMOS)

2006 → 4b & 1.25Gs/s (90nm CMOS)



Flash ADC- beginning..This lecture.

Other ADC's – later...

SAR ADC


Pipelined ADC

Over sampling ADCs

Folding/Interpolating

Algorithmic ADC

Combined Parallel ADCs

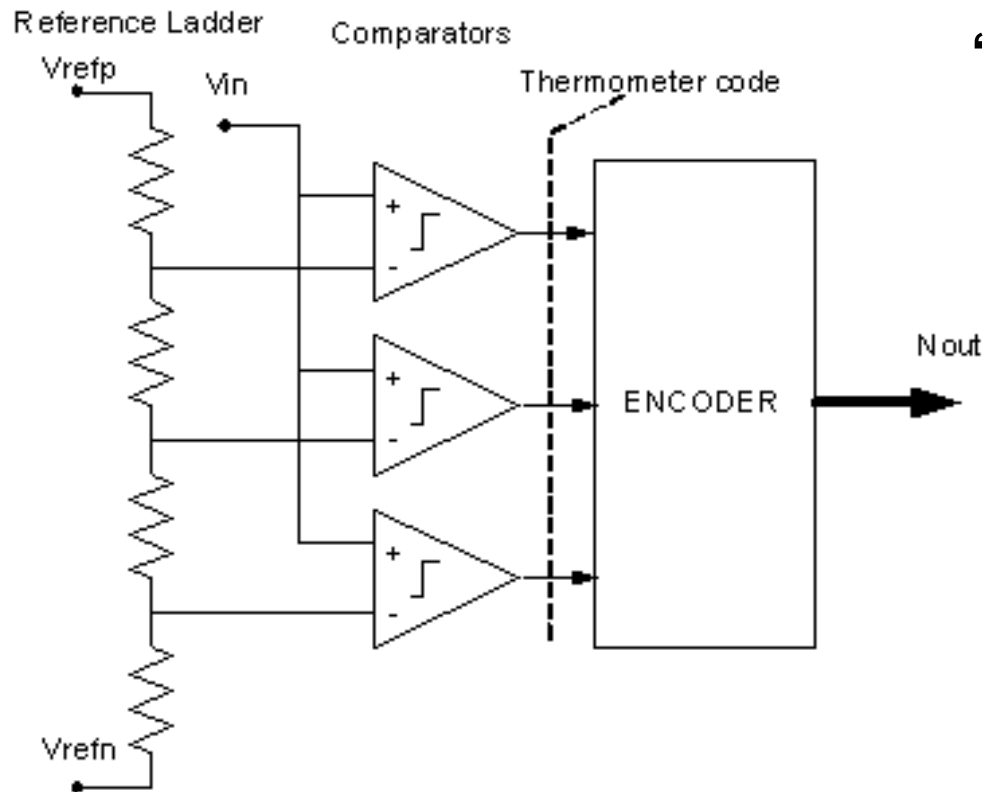

“Classic mixed signal”

No Feed Back No Amplifiers all in “Open Loop”


Monotonic increasing: no missing codes due to R

Comparator is the main element.



What's a Comparator



 It's a chain of gain stages (unlike op amp) to achieve fast response




Symbol

  

2 types :

**Analog-Time Cont.
clocked-Latched
(Later lectures)**

FLASH continue: Operation Equation

 

$$V1 = R1 / (R1 + R2 + R3 + \dots + Rj) * Vref$$

Simple voltage divider

if $R1 = R2 = R3 = \dots = Rj = R$)

$$Vi = iR * Vref / (\sum_{i=1}^j Ri)$$

$$V3 = 3R * Vref / (\sum_{i=1}^j Ri)$$

$$V2 = 2R * Vref / (\sum_{i=1}^j Ri)$$


$$V1 = R * Vref / (\sum_{i=1}^j Ri)$$

For n bit need $2^n - 1$ comparators

$$Vi = iR * Vref / (\sum_{i=1}^j Ri)$$

For n bit need 2^n resistors

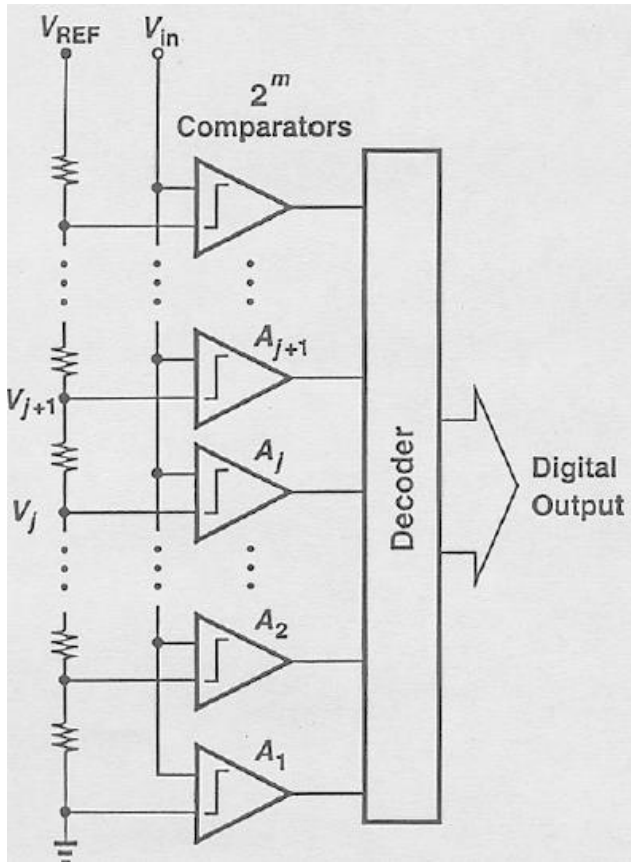FLASH continue: Number of Comparator Needed



Suited well up to 7-8 bits of resolution – 127 - 255 comparators

Flash speed: as the comparator, logic, and input impedance driving the comparators.

Output levels are like a “thermometer”

Example
Bot to top

11111100000
11111000000
11110000000
11100000000
11000000000
11000000000
10000000000

INPUT LEVELS	BINARY CODE	GRAY CODE
	d c b a	d c b a
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101
10	1010	1111
11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000

Table 3.2: Binary-Gray code implementation

total number of comparators required is $2^N - 1$, where N is the resolution of the ADC




A good way to see the errors lets go over flash design

An 8 bits Flash ADC

Assuming:

 Process 0.18um, $c_{ox} \sim 6\text{ff}/\mu\mu$, $K_n = 60\text{e-}6$ $K_p = 20\text{e-}6$




$$K_n = \mu C_{ox}$$



Step1: Choose an architecture – our task

Architecture – now to the details..

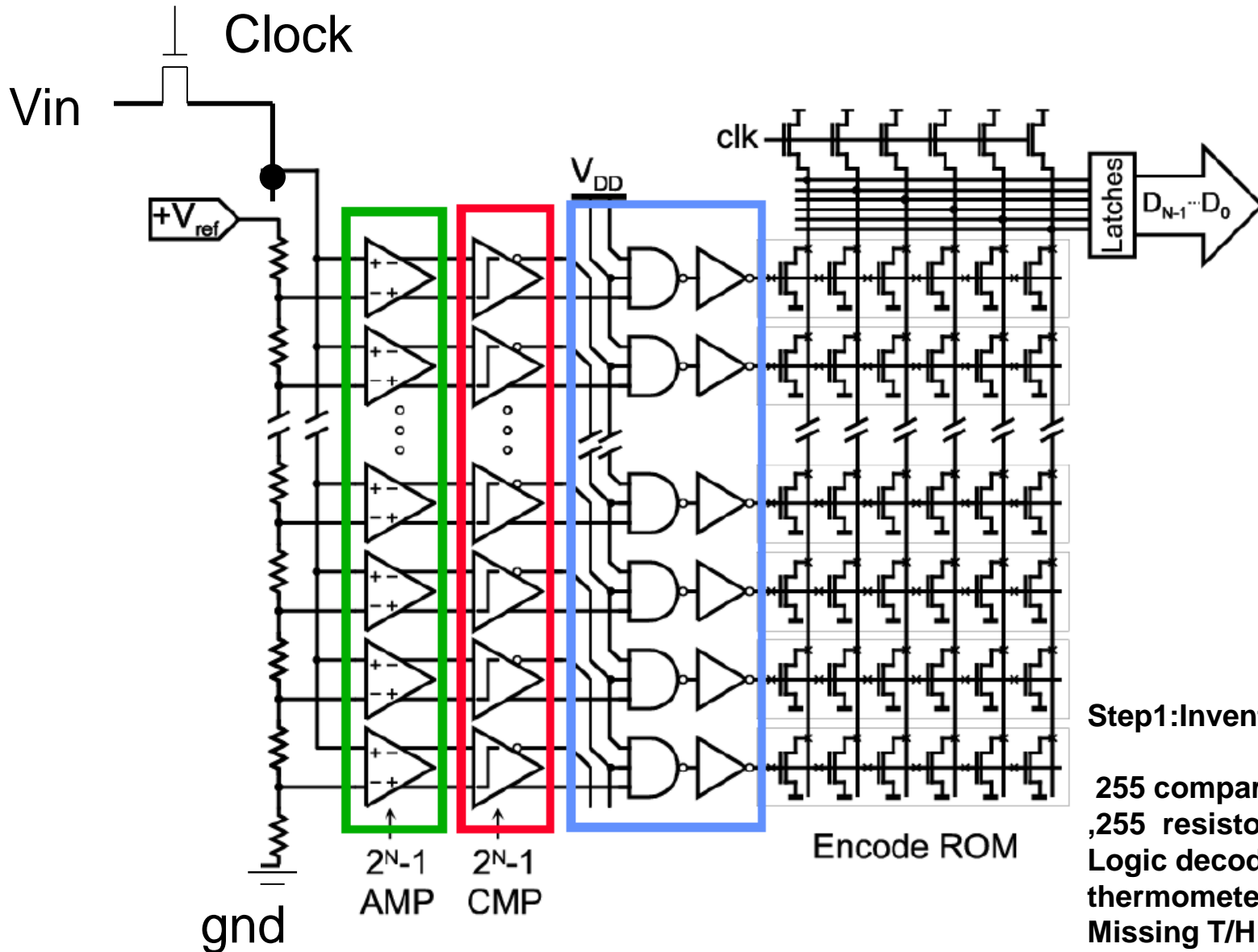

Step1:Inventory:

- 255 comparators/amp
- 255 resistors
- Logic decoder
- thermometer/binary
- Missing T/H
- References

Source : K.. Leuven



And how to deal/fix it..

Comparator Offset

Resistor mismatches

Power

Speed limit first stage

Signal Feed through

Gain

Dynamic Range – Max V_{ref}

Comparator Meta stability (and speed)

Following stages – (bubbles)

Clock distribution



Detail look each error-element in the FLASH

Now we don't have the tools to do this so we
Stop learn and get back to this in ~lect 5.



End lecture 3 (part b)