

Welcome to  
7718 semester 1 2022  
Mixed Signal Electronic Circuits

Instructor: Dr. Miki Moyal



Lectures

<http://www.gigalogchip.com/lectures.html>

## Lecture 06

*ADC Types*

*FLASH ADC*

Quick summary up to date


Covered Transistor Basics sampling.....

Covered Transistor/passives noises.....

Covered Quantization Noise of ADC/DAC

Covered Timing Jitter/inaccuracy.....

Covered Mismatch of elements.....

 

$$\sigma(\Delta V_T) = \frac{C_1}{\sqrt{W_{eff} \times L_{eff}}}$$

=====

=====

So Now lets have more fun: look at real blocks work.. ADCs/DACs, etc..

And their relations to transistor ICs.

=====

=====

$$g_m = \sqrt{2\mu C_{ox} \left(\frac{W}{L}\right) I_{ds}}$$

$$\Delta I_{ds} = g_m \cdot \Delta V_{gs}$$

$$f_s X(f) + f_s X(f - f_s) + f_s X(f - 2f_s) + f_s X(f - 3f_s) + \dots$$

$$f_s X(f + f_s) + f_s X(f + 2f_s) + f_s X(f + 3f_s) + \dots$$

**Quantization energy -**

$$\frac{1}{V_{LSB}} \int_{-V_{LSB}/2}^{+V_{LSB}/2} V_{err}^2(V_{in}) dV_{in} = \frac{V_{LSB}^2}{12}$$

**Thermal Noise**

$$I_{noise}^2 = \left(\frac{2}{3}\right) 4 \cdot k \cdot T \cdot \gamma \cdot g_m \cdot \Delta f$$

$$V_{in,noise}^2 = \frac{\left(\frac{2}{3}\right) 4 \cdot k \cdot T \cdot \gamma}{g_m} \Delta f$$


## Agenda

ADC Architectures – on going lectures

Flash ADCs

Flash – Design and Error Sources

# Flash ADC FoM History

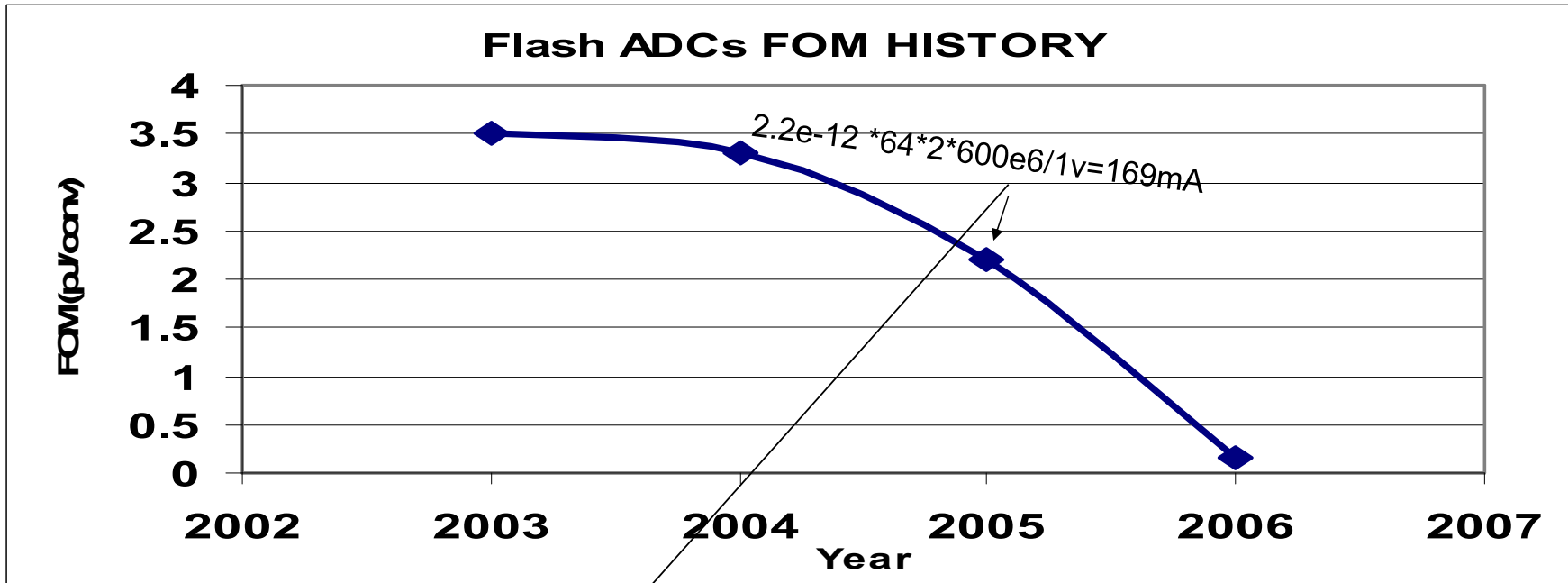

- 2003 → 6b & 2Gs/s (180nm CMOS)
- 2004 → 6b & 300Ms/s (0.25um CMOS)
- 2005 → 6b & 1.2Gs/s (130nm CMOS)
- 2006 → 4b & 1.25Gs/s (90nm CMOS)

$$FOM = \frac{P}{2^{ENOB} \times 2 \times ERBW}$$


## Common Architectures

- Flash ADC – This lecture.**
- Two Steps (Sub Ranging) ADC – if time allow.**

### Other ADC's

- SAR ADC
- Pipelined ADC
- Over Sampling ADC
- Folding/Interpolating ADC
- Algorithmic ADC
- Combined Parallel ADC

## The ENOB: General trends

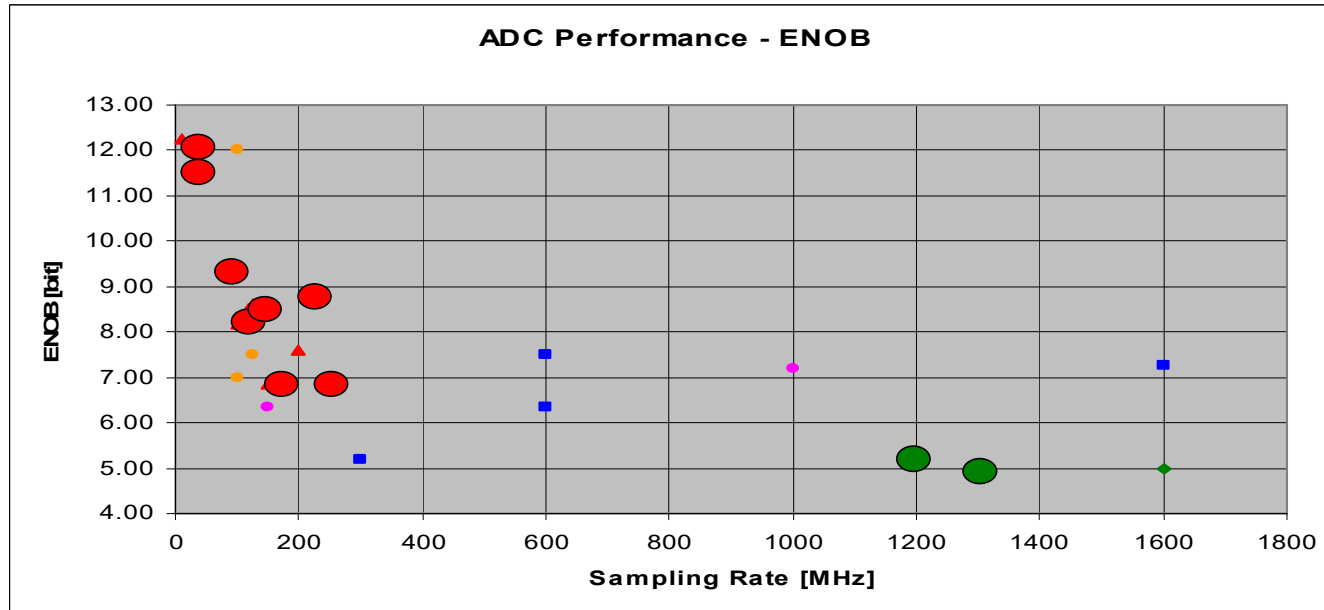

Green – Flash

Red – Pipe Line

Blue – Folding

Pink – Open Loop Pipe line

Sigma delta ADC ?

(0-200MHz, 9-14bit)

□ SNDR (AC) Measured Converter S/N

□ N Quantization

□ D Distortions

## Basic split

- Architecture suited for very *high input frequency* (less bits)
  - Flash ADC
  - Folding ADC
  - Open Loop Pipe Line – can still have many bits
  - Time interleaved ADC
  
- Architecture for *high precision* (more bits)
  - Flash Sub Ranging ADC
  - SAR ADC
  - Sigma Delta ADC
  - Pipeline ADC
  - Time interleaved ADC

## Basic Split

Architecture suited for very *high input frequency* (less bits)

- Flash ADC
- Folding ADC
- Open Loop Pipe Line – can still have many bits
- Time interleaved ADC

Architecture for *high precision* (more bits)


- Flash Sub Ranging ADC
- SAR ADC
- Sigma Delta ADC
- Pipeline ADC
- Time interleaved ADC



Rest of the slides will address only the FLASH  
ADC ( and its types)

## Basic flash ADC



### “Classic Mixed Signal”

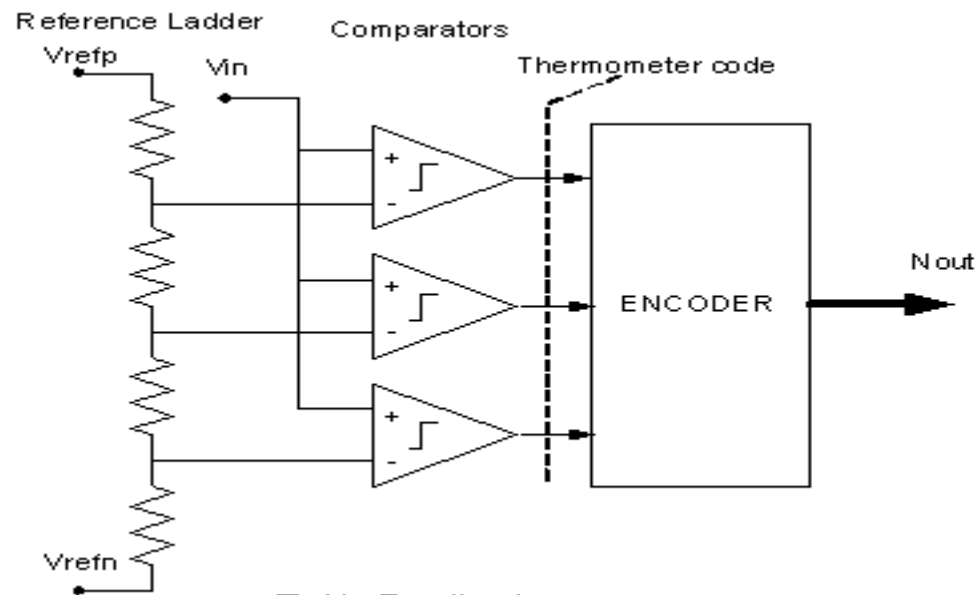


- No Feedback
- No Amplifiers all in “Open Loop”
- Monotonic increasing: no missing codes due to R
- Comparator is the main element.

What's a Comparator- done on prev. lectures.

  - It's a chain of gain stages (unlike op amp) to achieve fast response



## FLASH continue: Operation equation

 

$$V_1 = \frac{R_1}{(R_1 + R_2 + R_3 + \dots + R_j)} \cdot V_{ref}$$

Simple voltage divider

$$\text{if } R_1 = R_2 = R_3 = \dots = R_j = R$$

$$V_i = iR * V_{ref} / (\sum_{i=1}^j R_i)$$

$$V_3 = 3R * V_{ref} / (\sum_{i=1}^j R_i)$$

$$V_2 = 2R * V_{ref} / (\sum_{i=1}^j R_i)$$


$$V_1 = R * V_{ref} / (\sum_{i=1}^j R_i)$$

❑ For n bits need  $2^{n-1}$  Comparators

❑ For n bit need  $2^n$  Resistors
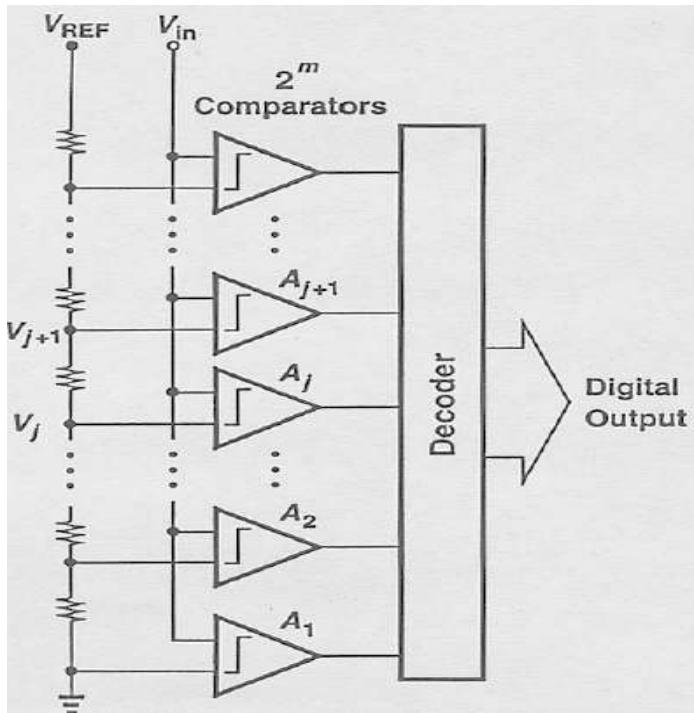
## FLASH continue: number of comparator needed

- ❑ Suited for up to 7-8 bits of resolution
  - ❑ 127 - 255 Comparators
- ❑ Flash speed
  - ❑ As the comparator, logic, and input impedance driving the comparators.
- ❑ Output is like a thermometer



**Example**  
**Bottom-to-Top**  
**1111111111**

maximum input

..  
 ...  
**0000000111**  
**0000000011**  
**0000000001**  
**00000000001**  
**00000000000**

**Input passed LSB,**  
 no input

Total number of Comparators required is  $2^N - 1$ , where  $N$  is the resolution of the ADC

8 bit 257 lines 000000000000000000000000..

## FLASH – detail each element

- Comparator Offset
- Resistor Mismatches
- Power
- Speed limit first stage
- Signal Feed Through
- Gain
- Dynamic Range – Max  $V_{ref}$
- Comparator Meta Stability (and speed)
- Following stages – (bubbles)
- Clock distribution

## FLASH – design example

- ❑ A good way to see the errors is to go over the flash design

### Task: Need to build: 8 bits Flash ADC

- ❑ Assuming:

- ❑ Process 0.18um/1.8V
- ❑  $C_{ox} \sim 6\text{ff}/\mu^2$ ,
- ❑  $K_p = 20\text{e-}6$
- ❑  $K_n = 60\text{e-}6$


$$K_n = \mu C_{ox}$$

We can control the rest: sizes , we are the artists..

## Step1: Choose an Architecture – our task



# FLASH – Architecture

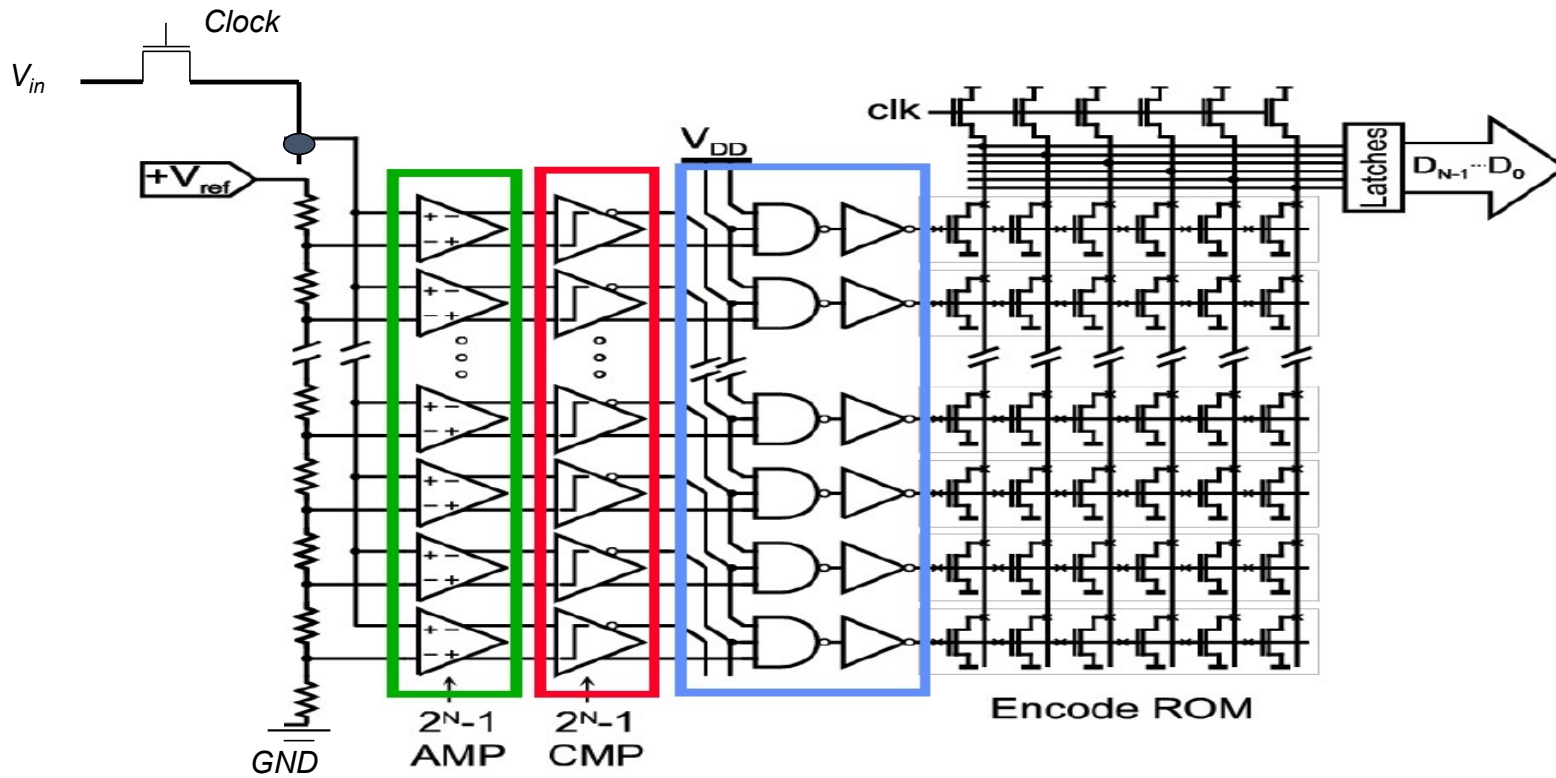

Source : K.. Leuven

❑ Step1:Inventory:


- ❑ 255 Comparators/Amp, 255 resistors
- ❑ Logic decoder
- ❑ Thermometer/binary
- ❑ Missing T/H
- ❑ References

## Step 2:

- ❑ Design the Converter:
- ❑ (W/L) with Correct Accuracy:



Find/look for:

 - ❑ Accuracy:
  - ❑ where in the design Non Linearity is created
- ❑ Comparator offsets – Random mechanism
- ❑ Resistor ladder – Random




  
## Design Example

- Comparator Offset:
  - Find W/L of the Comparator



  Offset – at which  $V_{os}$  the comparator switch without “effecting”  $I_{sb}$



$$\begin{aligned}
 V_{os1} &= \Delta R / R \cdot (I / gm) \\
 V_{os1} &= C1 / \sqrt{W_{eff} * L_{eff}} \\
 &= \\
 M2 &= M1
 \end{aligned}$$

## Comparator offset

- ❑ Given process 180nm
- ❑  $C_1$  is:

$$C_1 = 5(mV / \mu)$$

We use the equation from prev.

$$\sigma(\Delta V_t) = C_1 / \sqrt{W_{eff} * L_{eff}}$$

But, now we need 3 Sigma's – so “no” error is created - yield

$$V_{os} \leq 3 \cdot \sigma(\Delta V_t) \quad \text{oopsss.. now yield is important...3..}$$

Remember:

- ❑ Could be the biggest problem: bad for low voltage technologies

## Comparator Offset Calculations cont.

$$V_{os} \text{ (max)} = 1 / 2 \cdot LSB$$

$$V_{os} = 3 \cdot C1 / \sqrt{W_{eff} * L_{eff}}$$

$$V_{Fs} = 1V \quad V_{lsb} = 1 / 255 = 3.92 \text{ mV}$$

$$C1 = 5(mV / \mu) \rightarrow \text{Process given}$$

$$\sqrt{W_{eff} * L_{eff}} = 5 \text{ mV} / (1 / 2 (V_{Fs} / 255)) = 3 \cdot (10 \text{ mV} / 3.92 \text{ mV})$$


$$W_{eff} \cdot L_{eff} = 58.52$$

□ **Implies  $L=0.18\mu$   $W=325\mu$**

We assumed comp input stage was all..but got feeling how big can things be...

## Ladder Mismatches – Length Determinations

### Silicon Resistors

 

$R_p \sim 90\% - 99\%$  of  $R$  Salicide is removed = 2

$R_{nc} \sim$  Exposed Area to Salicide  $\sim 5 \frac{\Omega}{\nu}$

$R_c \sim$  Contact Resistor to Metal  $\sim 1 - 20 \frac{\Omega}{CT}$

### R Matching

$$G\left(\frac{\Delta k}{R}\right) = \sqrt{\left(\frac{A_{Rp}}{\sqrt{W \times L}}\right)^2 + \left(\frac{A_{Rnc}}{\sqrt{W_{nc} \times L_{nc}}}\right)^2 + \left(\frac{A_{nc}}{\sqrt{\text{Contact Area}}}\right)^2}$$


Example:

- Ignore all but poly resistance (see next slide), and
- If  $\frac{\Delta R}{R} = 2\%$  (1um x1um) – Process given
- Take 3 sigma's = 1u x 1u  $\rightarrow$  6%.

$$\Delta R < \frac{R}{2^{n-1}} \cdot 0.5 \gg \text{Need } \frac{\Delta R}{R} \text{ of } 1/2 \text{ LSB} = 0.196\% \text{ (} 100/510 \text{)}$$

$$\frac{0.06}{\sqrt{\text{Area}}} = 0.00196 \gg \text{Area} = 937 \mu^2 \gg \text{use } 1 \times 937 \mu\text{m}$$

 Generally: matching possible up to 10-11bit




Need  $1/2$  LSB=0.196%

R Length =937um

# Get Rid of Contact Errors

## Avoid Contacts – Matched Resistors

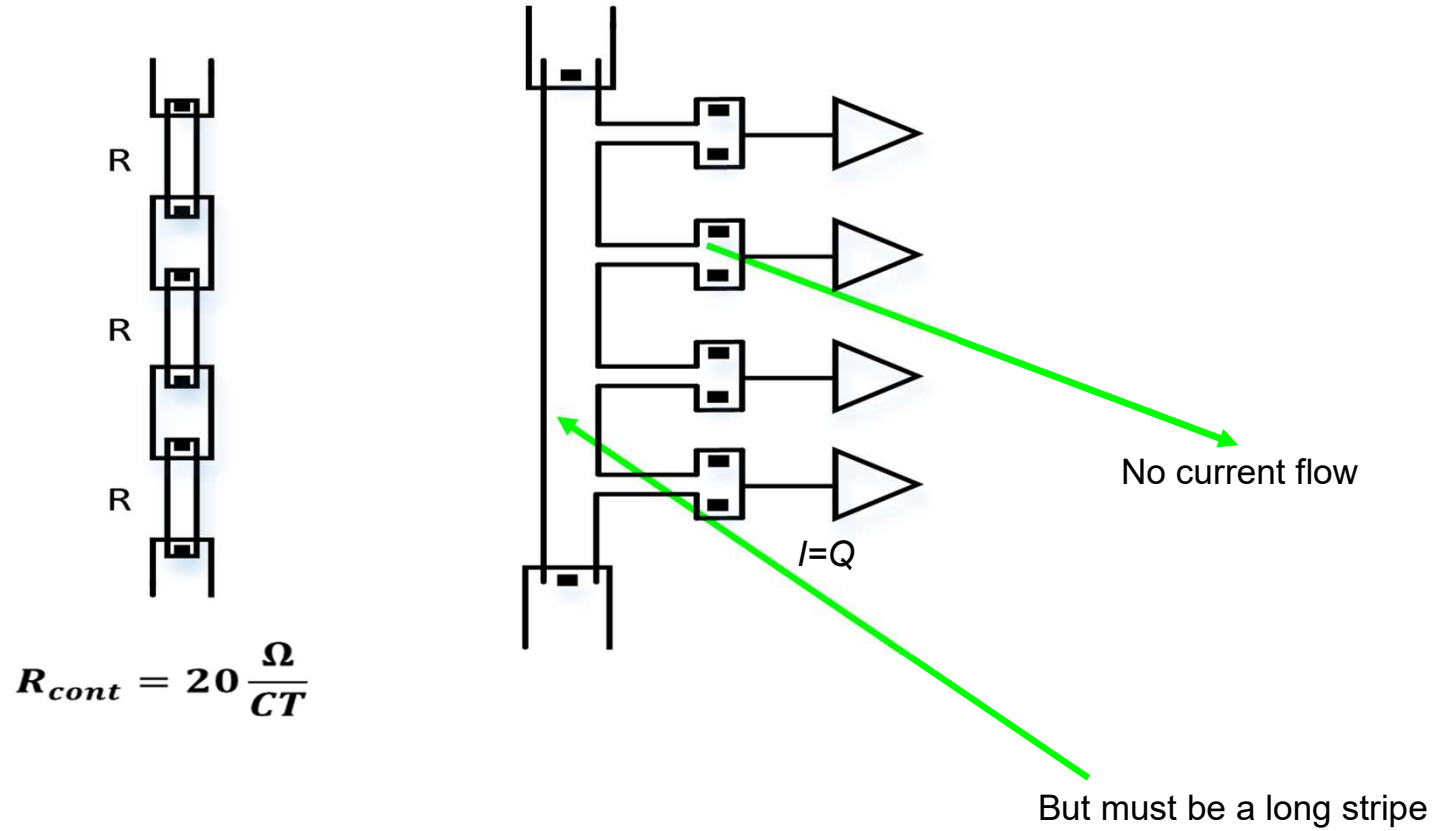

## Step 3. Power Dissipation



## Power – An Estimation

Power (due to comparators  $I_{in}$ )

$$P = V_{OD} \times I_{comp} = V_{OD} \times 2 \times k \frac{W}{2L} (V_{GS} - V_T)^2 [2^n - 1]$$

For:

$$K_n = 60E - 6,$$

$$L = 0.18\mu$$

$$W = 325\mu$$


$$\text{and if } V_{GS} - V_T = 0.1$$

$$I_{DS} = \mu C_{ox} \left( \frac{W}{2L} \right) (V_{GS} - V_T)^2 \times 255 = 541\mu A \times 255 = 138mA$$

big assumption

*P= Without T/H, logic, clock, resistor ladder we re at 248mW*

 - Should we increase L? (keep  $W \times L$ , drop Power?)
- Should we check real speed to get I?
- Should we calibrate offset and not increase  $W/L$ ?



Stop and re think:  
Isn't power based on I,  
shouldn't we look at speed first? For min I

And we didn't even start talking about thermal noises..etc..

We have R we have comp gm(l and w/l)...




So should be **\*\*easy to check.\*\***

If in fs/2 we don't generate  $> 1/2\text{LSB}$ ..(from  $4KT R$ , and  $8/3KT/gm$

What's the catch ? do all comp contribute ?


## Step 4. meet speed limits
   
# Speed Limit due to Front Stage – A Model




$$R_p \parallel R_n = \frac{1}{k_p \frac{W}{L} (V_{DD} - V_T)} \parallel \frac{1}{k_n \frac{W}{L} (V_{DD} - V_T)}$$

$V_s$

 

 $C_{in}$  is so large that  $R_{in}$  is important



1st identify region of operation  $v_{ds} \sim 0$

$$I_{ds} = \mu C_{ox} \left( \frac{W}{L} \right) [(V_{gs} - V_{th}) \cdot V_{ds} - \frac{1}{2} V_{ds}^2] \quad V_{gs} - V_{th} > V_{ds}$$

## Speed Limit due to Front Stage – Acquisition Time

$$\begin{aligned}
 1) \quad & V_{in} = V_o(1 - e^{-t/RC}) \\
 2) \quad & V_{in} + \frac{\Delta}{2} = V_o \\
 3) \quad & \Delta = \frac{V_o}{2^n - 1} \Rightarrow \frac{V_{in}}{V_o} = 1 - \frac{1}{2(2^n - 1)}
 \end{aligned}$$

Plug into [1]  $\gg 1 - \frac{1}{2(2^n - 1)} = 1 - e^{-t/RC}$


If  $\frac{1}{(2^n - 1)} \approx \frac{1}{2^n} \gg t = RC \cdot \ln 2 \cdot (n + 1)$

$t = 0.693RC \cdot (n + 1)$


or

8bits  $\gg RC \cdot \ln(255 \cdot 2)$

need 6.23 RC's

 
 
$$\begin{aligned}
 R &= R_p \parallel R_n \\
 C &= C_T \quad (\text{ADC})
 \end{aligned}$$



n [bits]	# of RC's
4	3.46
8	6.23
10	7.62

## Speed limit due to front stage – calculation

$$C_{ox} = 6 \text{ ff}/\mu^2 \quad R = 50\Omega \text{ (an Assumption)}$$

$$W/L = \frac{325}{0.18} \quad \text{From offset calculations } W/L=325/0.18$$

$$C_T = \frac{2}{3} C_{ox} \cdot 255 + C_{Routing} \quad \text{Assume all in Saturation (Too optimistic)}$$

$$C_T = 6 \text{ ff} \times 325 \times 0.18 \times 255$$

$$C_T = 59.7 \text{ pF}$$

$$t(8 \text{ bits}) = 6.23 RC = 18.6 \text{ ns} \gg 53.7 \text{ MHz}$$



Disappointing low frequency



Stop and re think:

- New buffer to drive low cap?
- Re-look at matching – calibrate to reduce  $C_T$ ?




# Speed limit due to Front Stage – View

 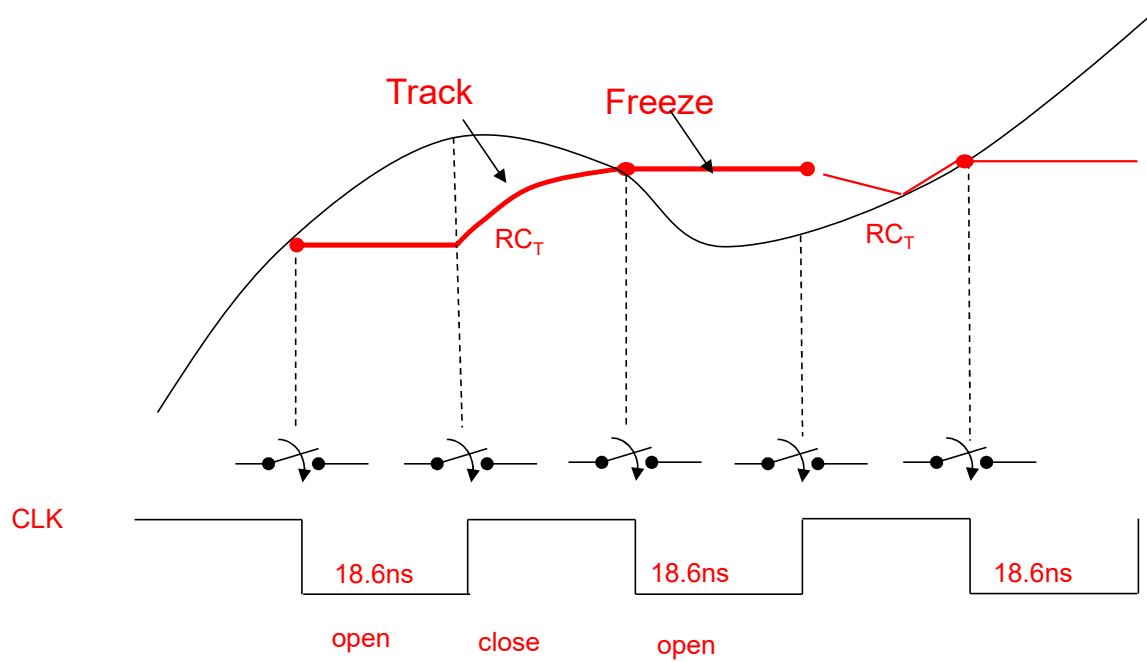

53.7MHz

But when is min to full scale  
Happen ?

Quick summary prev. lecture

   

53.7MHz

Do we FFT the red ? Disaster...

Problem with Cin-speed.. Area..- but

- If  $\frac{\Delta R}{R} = 2\%$  (1 $\mu\text{m} \times 1\mu\text{m}$ ) – Process given
- Take 3 sigma's = 1u x 1u  $\rightarrow$  6%.

$R_{lsb} = R/256$ .  $R_{lsb}$  can be off 50%..

$$\Delta R < \frac{R}{2^{n-1}} \cdot 0.5 \gg \text{Need } \frac{\Delta R}{R} \text{ of } 1/2 \text{ LSB} = 0.196\% \text{ (100/510)}$$

$$\frac{0.06}{\sqrt{\text{Area}}} = 0.00196 \gg \text{Area} = 937\mu^2 \gg \text{use } 1 \times 937\mu\text{m}$$


$$\Delta R < \frac{R}{2^{n-1}} \cdot 0.5$$



# Speed Limit: feed through speed
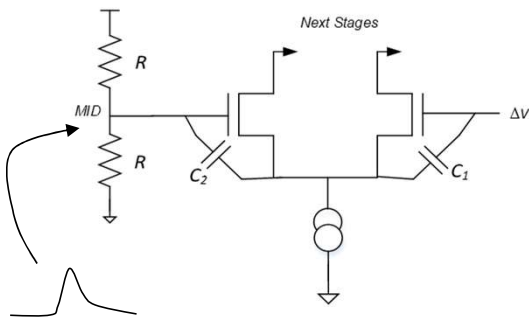
## Signal Feed Through

Who is in Sat?  $C_{gs} = 2/3 C_{ox}$   
 Who is in Off?  $C_{gs} = C_{ov}$ ,  $C_{ox}$  to Bulk =  $C_{ox}$   
 Who is in Lin?  $C_{gs} = 1/2 C_{ox}$



Worst Case Mid Ladder  $R/2$ ,  $\frac{C_1 \cdot C_2}{C_1 + C_2} \approx \frac{1}{2} C_{gs}$

$$\tau = RC = \left(\frac{R}{2}\right) \left[ \frac{2}{3} C_{ox} \frac{n}{3} + \frac{1}{2} C_{ox} \frac{n}{3} \right]$$

To reach 1/2 LSB of 6 bits » 4.8 RC


Add big filter on Ladder

$$\frac{V_{mid}}{V_{in}} = \frac{\pi}{4} \cdot f_{in} \cdot R_{ladder} \cdot C$$


Source : Esscirc 2002. Leuven

C total capacitance  
 Find max input ladder R.  
 for no effect on feed through

 (After matching calculations are satisfied).




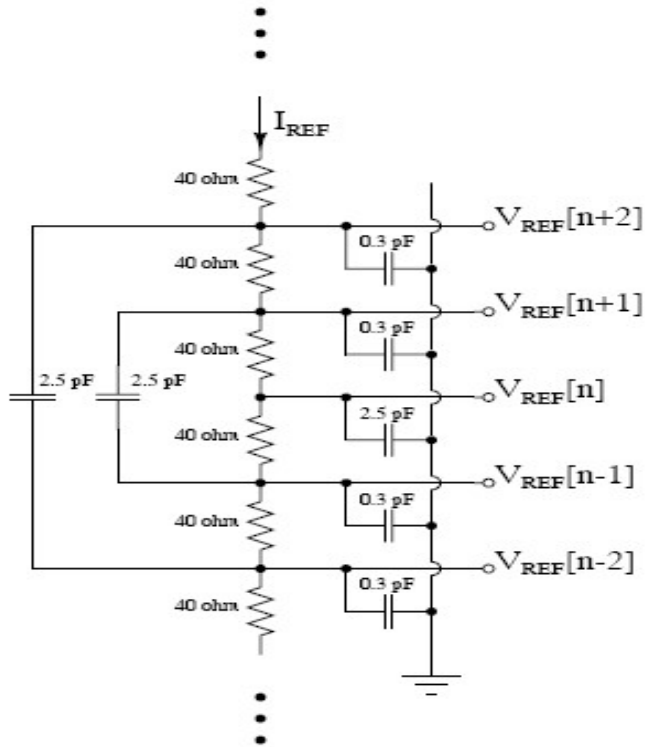
# An Example – reduce/removed feed through effect



Example: Cap stabilization 5b 1GS.s flash  
Source: Esscirc 2006 Helsinki univ, Olli Viitala

## Step 5. Spec of the needed comparator
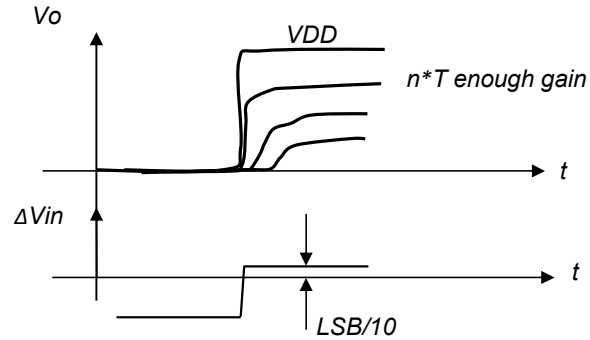 
# Comparator Gain – More in Comparator Design



## Need Enough Gain

$$1. \quad \Delta V = V_1 - V_2 = \frac{1}{10} LSB$$


$$VDD = 1.8V, \quad n \text{ bit}$$

$$A_0 = \frac{1.8}{\frac{V_{FS}}{2^n}} \cdot 10 = \frac{1.8}{\frac{0.5}{2^8}} = 18 \cdot 2^9 = 9,216 = 79dB$$

1 or 2 Stages – Not Enough

2. After gain we need to also look at speed response

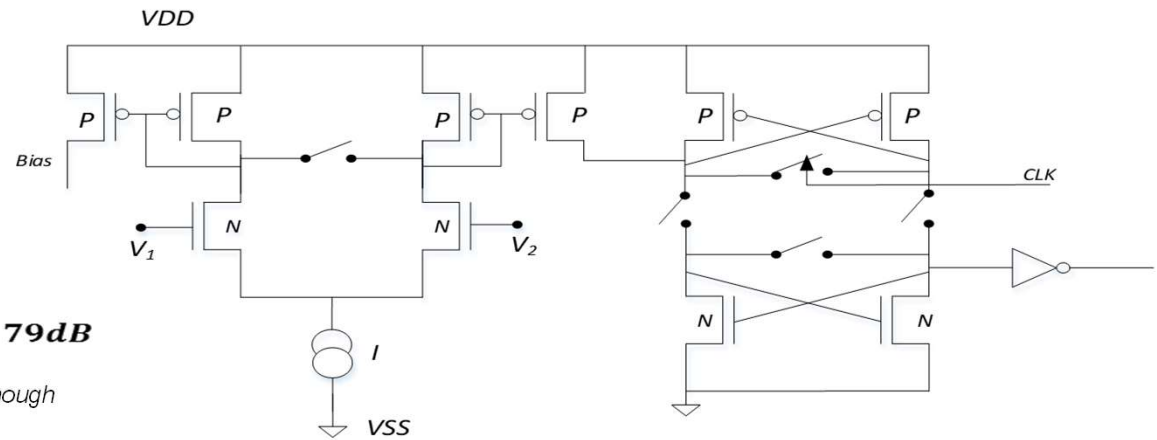3. **Let's creat a Latch on Positive Gain**



Need minimum of 300mV Before the invertor trips


More details in comparator design

## More on Distortions – Variable BW – Flash Specific

capacitors	Saturation	Linear	Off
C gate to S	$2/3C_{ox}+C_{ov}$	$1/2C_{ox}+C_{ov}$	$C_{ov}$
C gate to D	$C_{ov}$	$1/2C_{ox}+C_{ov}$	$C_{ov}$
C gate to B	0	0	$C_{ox}//C_{cb}+..$

$$HD_2 = \frac{V_o \omega C_1 R}{2\sqrt{1 + (2\omega C_0 R)^2}}$$


Source : Esscirc 2002 Leuven

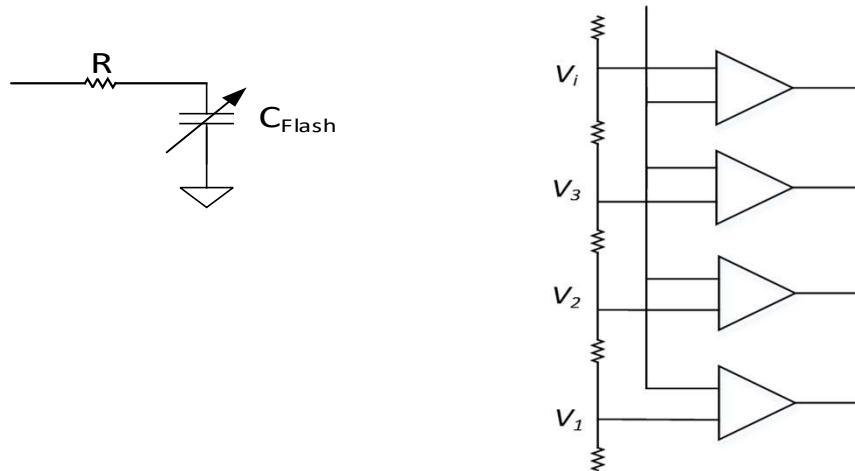

## Step 6. Set the Maximum Dynamic Range

# Dynamic Range – Max Vref


*Full Scale Possible*

 

$V_{FS} = 1.8 - 5\% - 0.7 - 0.3 = 0.71V$   
 (so we made error assuming 1v)  
 In step 2.

$V_{FS}$  limit the ladder full scale  
 Limit the SNRD  $\rightarrow$  VLsb.  
 Need to be maximized most times


 
- Limit the Ladder Full Scale
- Limit the SNR
- Or – 2 Comparator Type



## Step 7. Clock – Jitter Requirement Set Requirements



# Flash Clock Distribution Errors

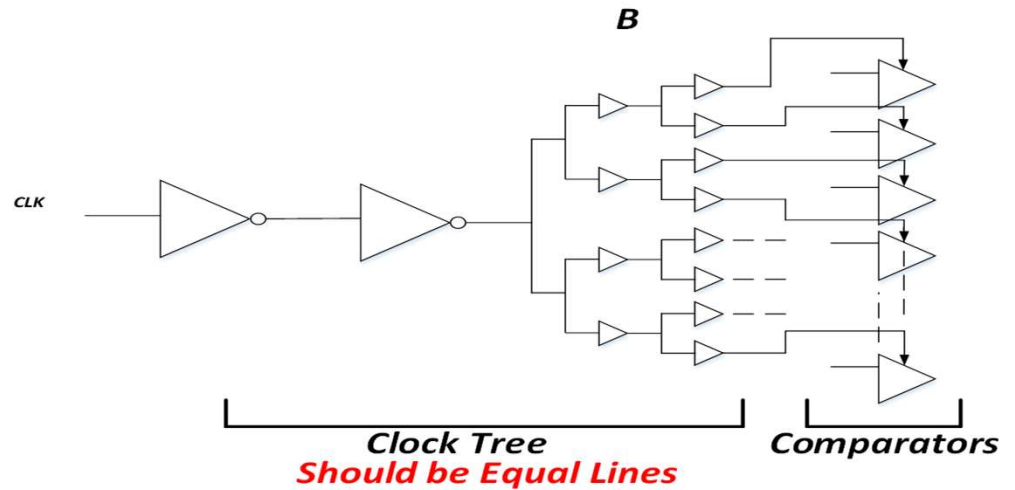 


An Estimation = 1ps/µ

$$T_d = 2\pi\sqrt{LC} \approx 2ps/100\mu m$$

Last Problem

 Deterministic Jitter  $\Delta VCC \rightarrow \Delta Jitter$




Probability Get Hz

Not every Comp Clock signal at the same time

*If NO → S/N bad!*

Step 8. Digital design – can we help the analog ? What can we do there..

# Error Correction

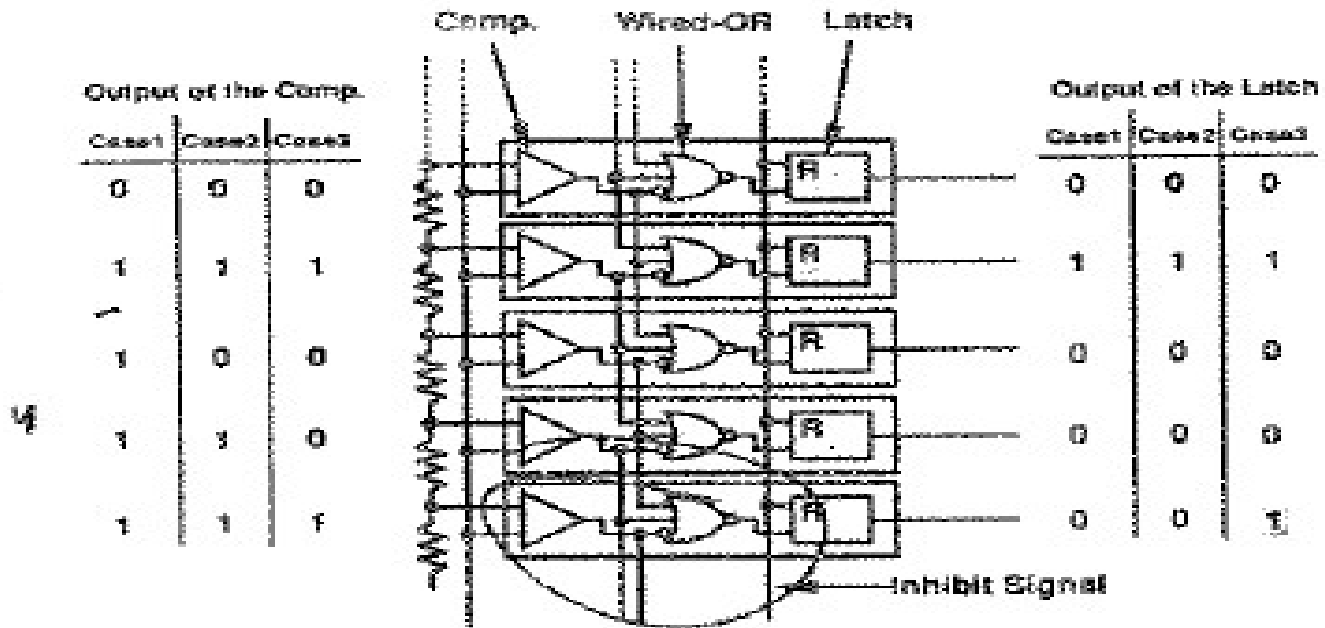

Bubble error look at your neighbour  
 Won't correct two errors

Design Check – Are We Satisfy? Lets look at the FOM value..

□ Definition 2.

$$FOM = \frac{P}{2^{ENOB} \times 2 \times ERBW}$$

$$Energy\ over\ Decision = \frac{Power}{SamplingRate \cdot 2^{Nbit}}$$



Last lect


(FOM = 17 is high → 248mw / (57e6 x 255)= 17e-12

(248 from 138 x VCC.)

Since nothing works well..  
How about other architectures ?

 Question...

- Why does this circuit reduces capacitance of T/H and help drive the large capacitance of the ADC ?



**continue**

***FLASH ADC ARCHITECTURE***

***ALTERNATIVES- \*\*2 Step\*\****

## ALTERNATIVE DESIGNS OF FLASH ADC

Errors: Meta stability- quick re-look.



Differential Architecture

Charge Flash architecture

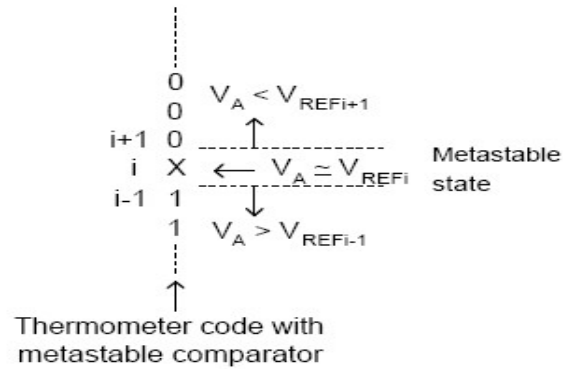 
# Meta stability

Ref.: IEEE JSSC, vol. 31, pp. 1132-1140, Aug. 1996, 7-b 80-MHz flash ADC


Metastability error: occurs in ADCs when undefined comparator outputs pass through the encoder to the converter output bits.



 
Key:  
No one is immune  
even a slow system should have fast comparator



 Normal response is exponential  
It take longer and longer at the 2  
comparator input get closer  
and closer



 X means far from 0 or V+ ( ~vdd/2 )  
You can't design it out  
You can reduce its occurrence






# Differential Designs

Differential /improved implementation  
FLASH architecture

Differential Design

Capacitive Charge FLASH

# DIFFERENTIAL-details

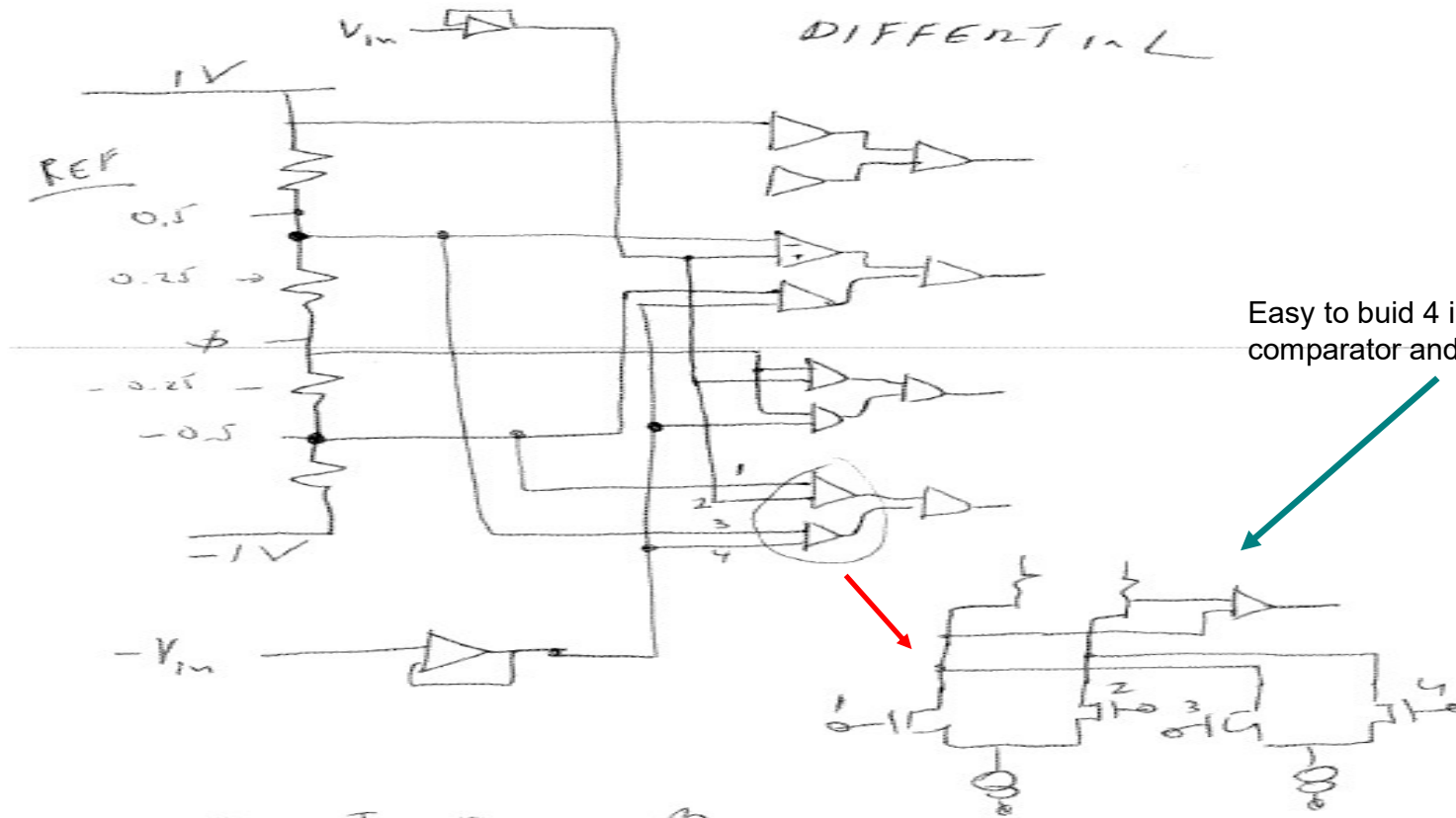

Easy to build 4 input comparator and to sum currents in CMOS :


- \* FLOAT FROM 0
- \* USE CM MID POINT
- \* 2x SIGNAL, ROUTING! ok for 3-4 bits

# DIFFERENTIAL

INL GOES TO 0 In the middle  
Signal is doubled routing is harder

Simple to make differential comparator

## Flash ADC Basics (2)

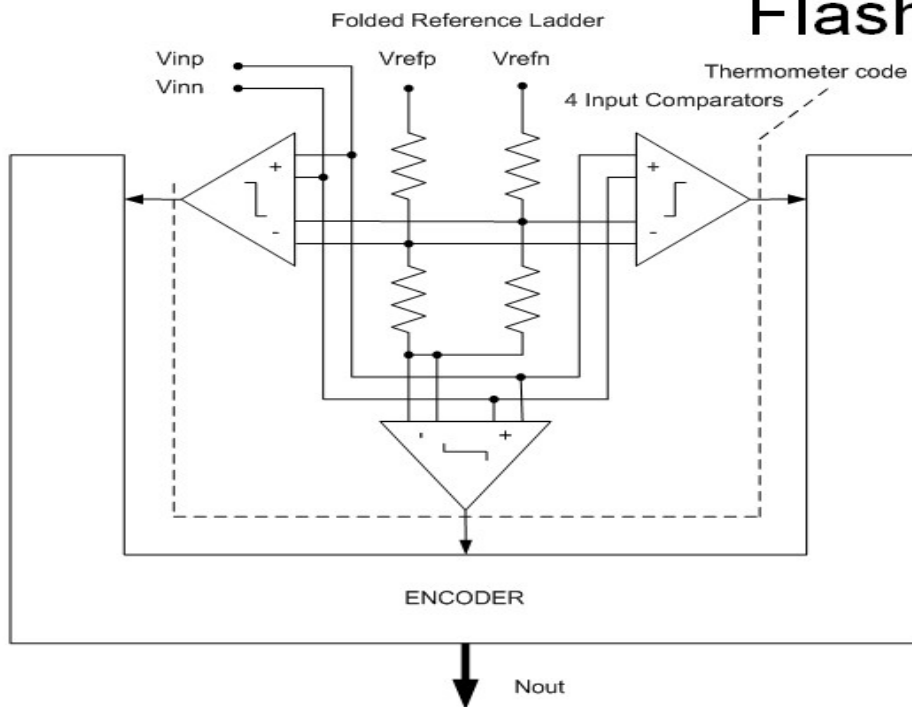

Fully differential implementation:

- wider dynamic range
- better noise immunity
- better linearity

Other reasons :

Symmetry is preserved HD2, HD4 get reduced/cancelled

# CAPACITIVE CHARGE FLAH

## Architecture Alternative: Capacitive Charge ADC

Can we use an inverter as simple gain stage  
Use capacitors to transfer  $V_{in} - V_{ref} \times \text{gain}$ .


Why ?

Inverter is a digital cell no special process needs  
It draw 0 DC current (power)  
very fast and simple, power is lower..

the reason...(Offset cancellation is build in) !


simpler comparator

Example: Create the ladder codes.

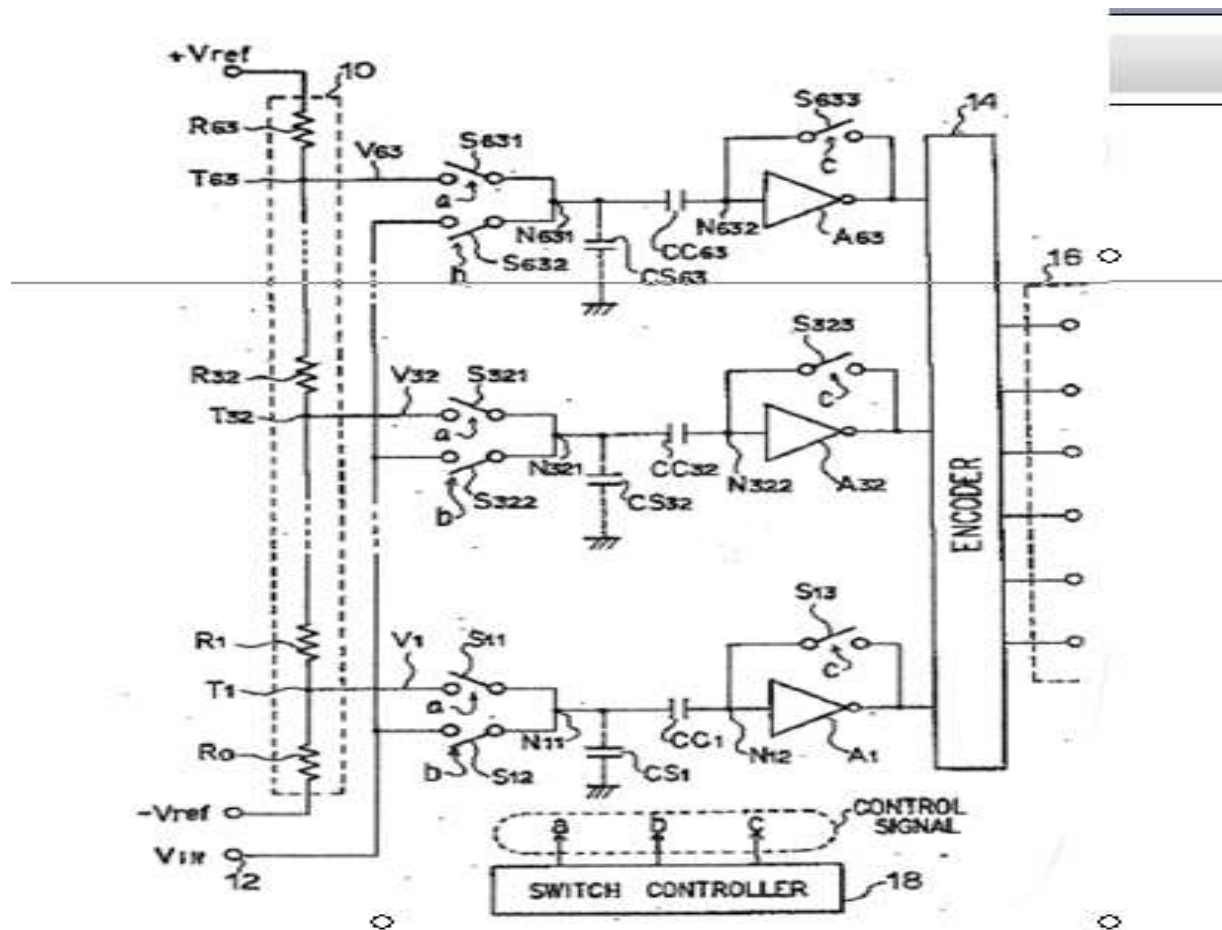

Source: Fairchild Data sheet
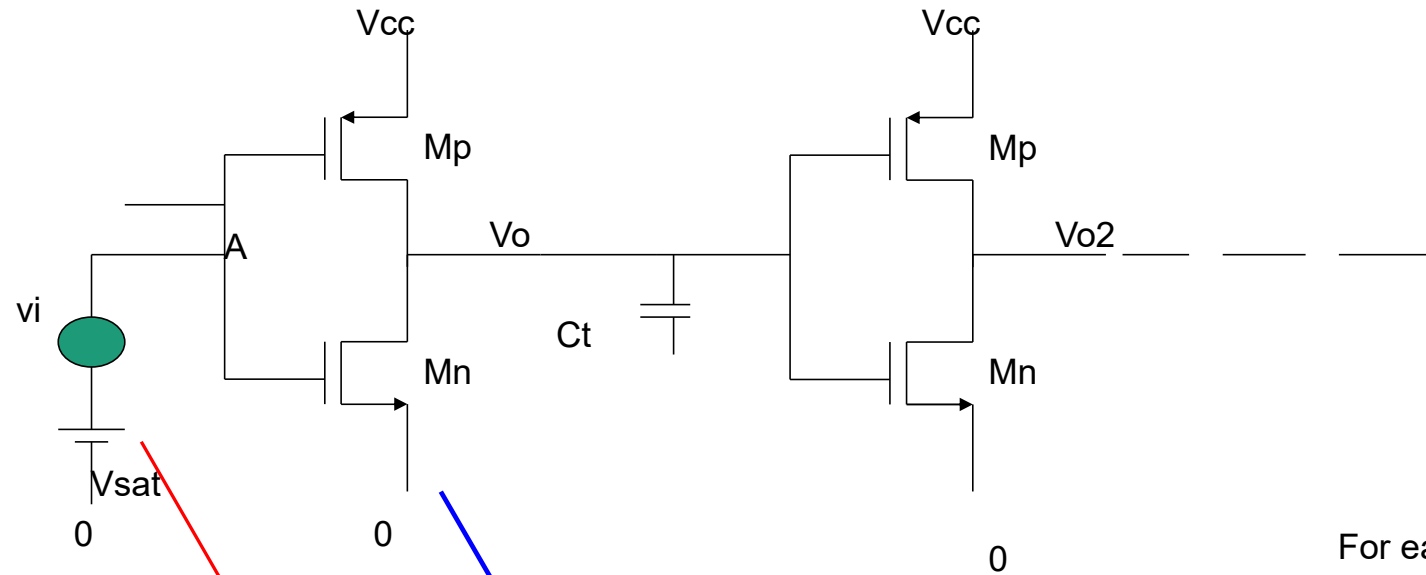
## Operation- Inverter chain- as gain stage



For each stage

$$A_v(\text{dc}) = (g_{Mn} + g_{Mp}) \times r_{op} // r_{on}$$


$$\text{Pole} = 1 / 2\pi C_t (r_{op} // r_{on})$$

Amplification is done but

Next how to fix the DC, mid point ? (in saturation)

Next: Can we create differences with one input- at A


derive  
 ↗

 


$$V_{out} = (V_{REF} - V_{in}) \left[ \frac{C_s}{C_s + C_s} \right] \cdot A$$



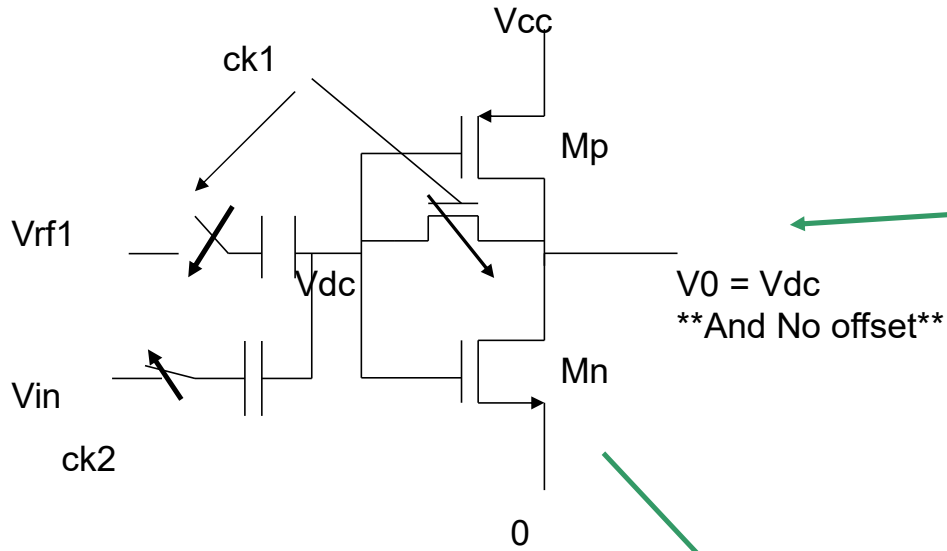
## Insert the second level - Subtraction and gain



Model at  $ck1=1$  (closed)  $ck2=0$

 


 Step 1  
 $Ck1=H$  closed  
 $Ck2=L$  open



$v_0=v_i$  the inv. is for sure in  
 Saturation and in low gain/impedance
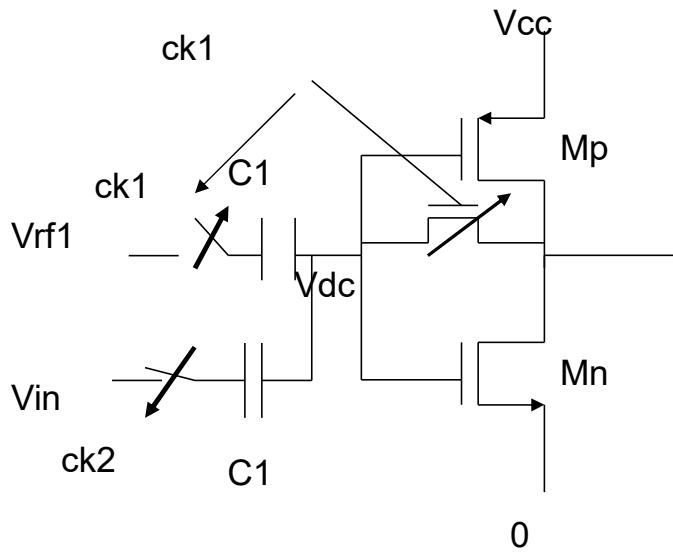
## Insert the second level - Subtraction and gain




Step 2  
 Ck1=0 open  
 Ck2=H closed

$$V_0 = (V_{rf1} - V_{in})A_o(f) + \text{what it was before}(V_{dc})$$



And No offset.

$$Q_1 = C(V_{rf1} - V_x)$$

Model at ck1=1 ck2=0

 

Model at ck2=1 ck1=0

  

## Speed

Speed Estimation:

6 bit ADC, no S/H

At L min 130 nm (  $C_{ox} \sim 13 \text{ff/}\mu\text{m}^2$ ) can get to 1-2 GHz – Flash “only”

Example:

Input Delay = 150ps (  $5.5/2\pi RC_{in} + R_{ladder}C_{gs}/2$  to drive 63 comp/calibrate)

+ 250ps comparator + 100ps logic (25ps/gate) = 500 ps max

Possibly latch after comp and save some of the 100ps. ( 50ps)

Sample at 2.0GHz max through put (Input frequency)

twice the min delay  $\sim 1 \text{ GHz}$

## FLASH ADC- SUMMARY

### *Bad-Good*

Monotonic

Very fast, No amplifiers, Resistors can match well to 10b

Design:

Big input capacitance

Comparator offset is an issue

Clocking routing sampling time

Meta stability

Decoding to avoid bubbles

If S/H is used – Distortion added

Hardware:

Exponential in complexity

High in power for 7 bits or more ( 127 comparators)

Could lead to large die size

References may need to be filtered from kick back

Medium: to scale down in technology → power supply!

Power        ~ 2 to N

Area         ~ 2 to N

Cin          ~ 2 to N


R ladder    ~ 2 to N

Here N is an increase of effective resolution

Since Flash silicon Area and Power grows exponentially  
How about different architecture

# Sub-ranging ADCs

## 4-Bit Flash Vs. 4-Bit Two-Step ADC

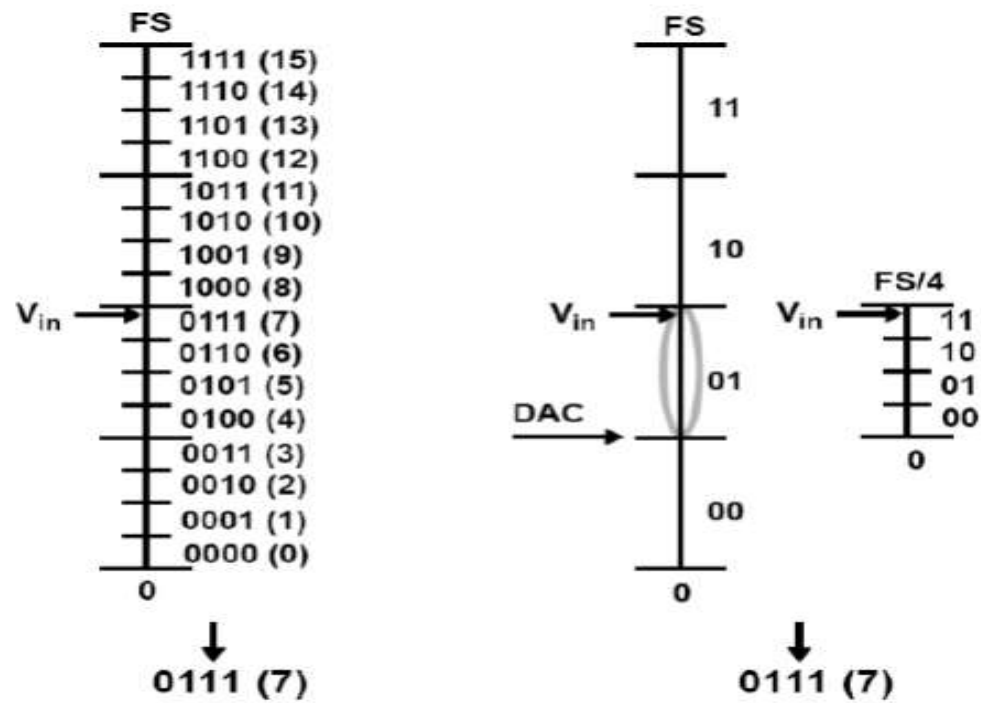

## Two-step: subranging ADC


---

+  $2(2^{N/2}-1)$  comparators

Coarse bank selects which part of reference ladder to connect to fine bank

- Speed limited by settling of fine references

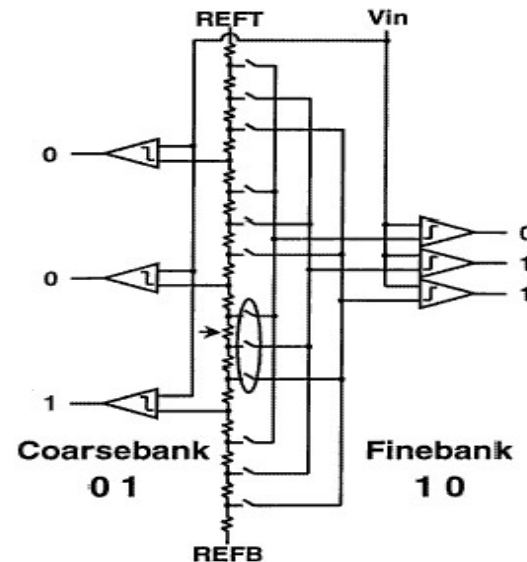parasitic capacitance from  $> 2^N$  switches + large kickback



Source: BRCM


Lost time- Need twice the time and S/H.

Resistor get glitches now impedance is important

New many switches ( 2 to the N – M Coarse connection )



## Sub ranging ADC FOM History

 


2006 → 6b & 1Gs/s (90nm CMOS)

2007 → 10b & 160Ms/s (90nm CMOS)

2008 → 5b & 1.75Gs/s (90nm CMOS)

Operation details : how to reduce number of comparators

## Sub-Ranging ADC Basics

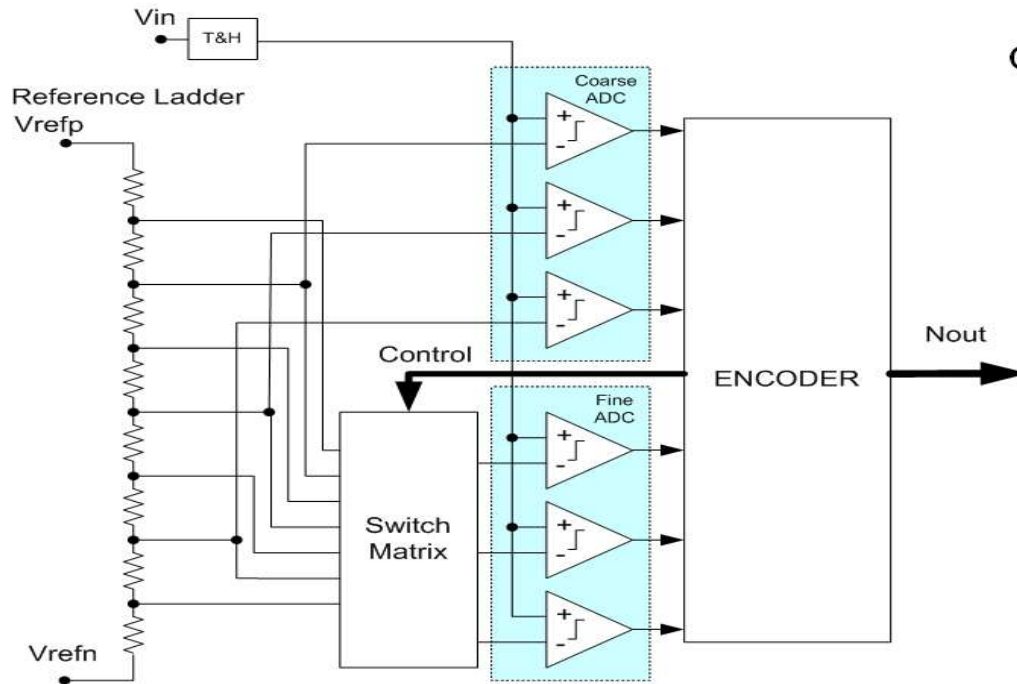


- Conversion is done in two steps
- coarse ADC determines the region of the ladder the fine ADC will use
  - regions can overlap to produce the redundancy that relaxes the offset requirement for the coarse ADC
  - for the fine ADC – strict offset requirements


Fine is waiting for the Coarse (MSBs) – need S/H  
How to partition ? 10 bit can use 31 comparators for Coarse  
and 32 for fine = 63 instead of 1024  
Or 63 for coarse ( 6 bit) and 15 for fine ?
 
## Summary: : Sub-ranging ADCs

- Power efficient
  - Two low resolution ADCs operating in a pipeline manner
- Reduced speed
  - Throughput can be still very high
- T&H is inevitable
  - The most critical component in the architecture
  - Loading is relaxed
- Residue generation
  - Needs  $M+N$  bit accuracy
- Interleaving is possible
- State of FOM is around  $0.5\text{pJ/conv}$




## SH Versus clocked flash

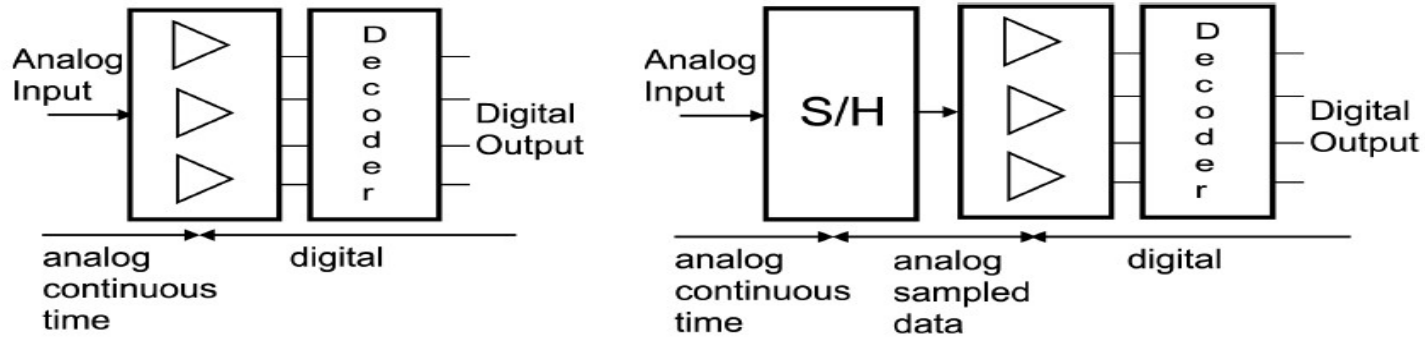

Source: KU Leuven

SH will draw 20-40% more power
 
## Flash architecture with digital corrections 1GHz/6 bits




### Avantages :

- Remove sample and hold – make clocking harder
- Use comparators as sample and hold
- Use pre gain comparator – Option
- Error correction logic
- ROM Grey encoder
- Now task is on the clock to be accurate to all comparators

# Offset Cancellation/reduction

Select 7I for maximum offset possible

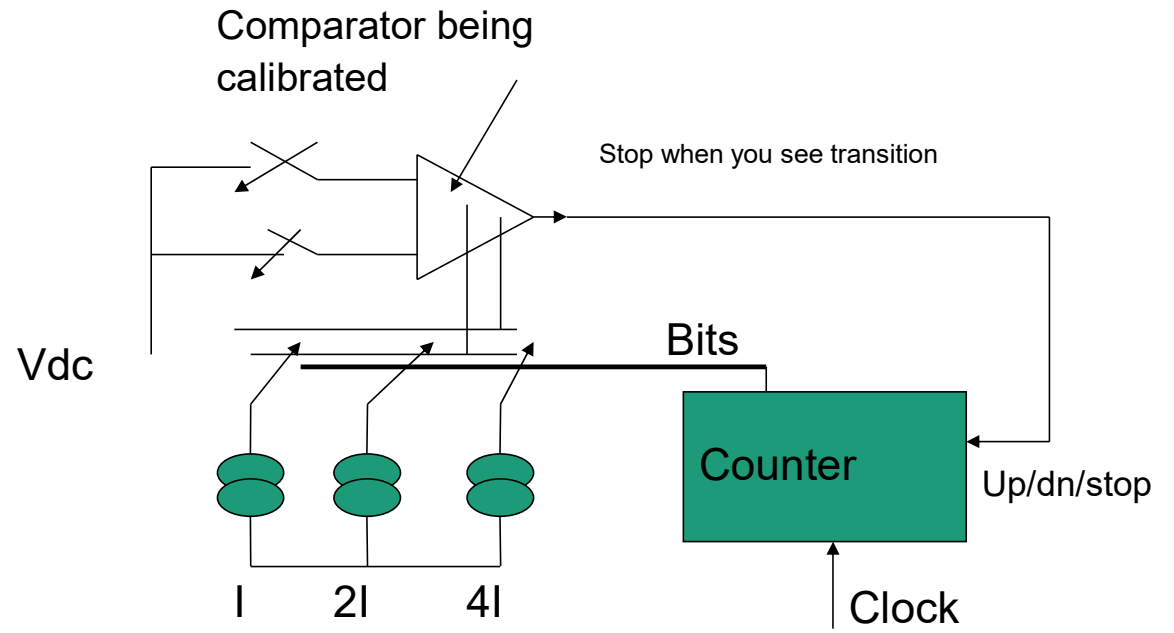

## Alternative offset cancellation

Easy to do in start up.

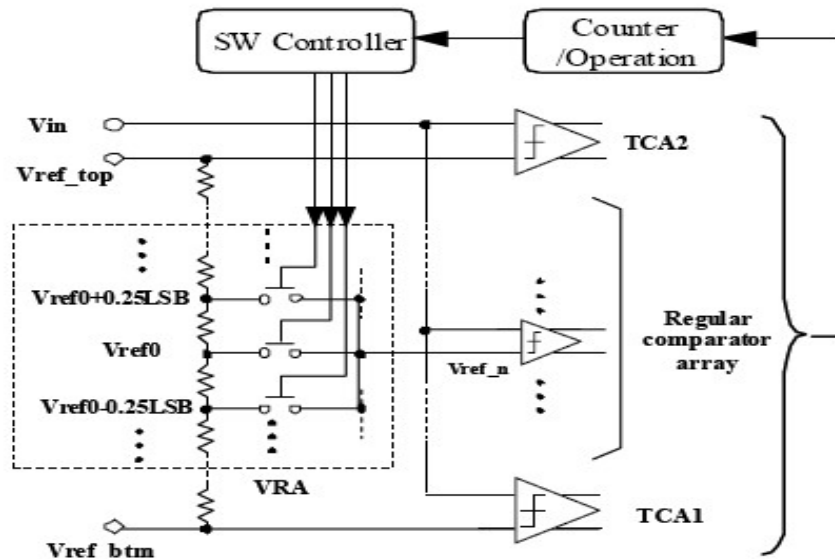


Figure 2: Architecture of offset cancel circuit.

We can go wild with good ideas:

Find offset connect comparator to different point on the ladder

Add small DAC to each comparator find trip point (Feed back)- last foil.

Remember the offset in digital code and offset the digital information

Offset Calibrating Comparator Array for 1.2-V, 6-bit, 4-Gsample/s Flash ADCs using 0.13-um generic CMOS technology

Hiroyuki Okada, Yasuyuki Hashimoto,  
Kohji Sakata, Toshiro Tsukada, Koichiro Ishibashi

E N D lect 06