

Welcome to  
7718 semester 1 2022  
Mixed Signal Electronic Circuits

Instructor: Dr. Miki Moyal



## Lecture 7

**SUCCESIVE APPROXIMATION ADC: Operation**

**Design of Time Continuous SARs**

**Design of Switch C SAR**

**Error sources**

Lectures are placed in my site:  
<http://www.gigalogchip.com/lectures.html>

## Agenda

- ADC Architectures
- SAR ADCs
- Error Sources

### A/D Converter ca. 1954

---

- ◆ 19" × 15" × 26"
- ◆ 150 lbs
- ◆ 500W
- ◆ \$8,500.00




Courtesy,  
Analogic Corporation  
8 Centennial Drive  
Peabody, MA 01960


<http://www.analogic.com>

**Figure 4.3:** 1954 "DATRAC" 11-bit, 50-kSPS SAR ADC  
Designed by Bernard M. Gordon at EPSCO


## Common data acquisition architectures

 


**FLASH ADC**

 


**Sub ranging**

 


**SAR**

 

**Pipe Line**

 

**Sigma Delta**

 


**SD multi bits**


## Which ADC to use and why

miki

Technion

### ADC Architectures

 

 


2006 → 12b & 100Ks/s (180nm CMOS)

2007 → 9b & 50Ms/s (90nm CMOS)

2008 → 9b & 40Ms/s (90nm CMOS)

$$\frac{Energy}{Decision} = \frac{Power}{SamplingRate \times 2^{Nbit}}$$

## Generic ADC:

 

- $V_{\text{residue}}$  is a function of  $V_{\text{in}} - V_{\text{ref}}$ .
- The Residue sets the source of Linearity Errors
- The Comparator set the source Speed (Offset may be a problem )
- Must check always:
  - Distortion (non linearity's) and ckt noise.
  - Speed and Power

## Successive approximation ADC

If  $T_s$  is twice maximum BW


And if  $N$  = desire bits

**It requires minimum of  $p = N \times T_s$  passes to generate  $N$  bit**

**Output words limiting the throughput**

**It requires  $N$ -bit accurate DAC**


**It requires faster settling elements**

 


Strict timing is involved- transforming analog to digital each cycle

Comparator runs inside an open loop circuit  
therefore stability and closed loop Band width is not an issue.


## Flow chart of SAR ADC

 


## SAR ADC Details

 

## SAR ADC – Timing

 

## SAR design- determining full scale

 

How to find RD value


$$R_D \gg \frac{V_{in\_max}}{R_{in}} = \frac{V_{ref}}{R_D}$$

$$R_D = \left[ \frac{V_{in\_scale}}{V_{ref}} \right]^{-1} R_{in}$$

Time Continuous only means we use non switched C for dac

## Time continuous SAR block

- 1<sup>st</sup> step sample and hold

 


Covered already. Note the buffer

- We know the errors
- We know the speed needed
- We can proceed to build the block
 
## SAR analog Loop


- 2<sup>nd</sup> step the sampled voltage part is being converted to I



Next how to build IDAC
 
## SAR IDAC feedback generation

- 3<sup>rd</sup> step the  $I_{in}$  and  $I_{dac}$  is compared around the loop n times




## SAR DAC – use an another alternative to R-Ladder

- Go to DAC lecture pick another type ?
- We got transistors they are small
- Current is always easy to generate with transistors
 
## SAR DAC – another DAC – speed and area Improvement

$$-V_{in}(nT) \frac{R_f}{R_i} + I_{DAC} R_f$$



## SAR DAC – another DAC – speed and area Improvement

- ❑ We used “not so efficient design”
- ❑ Speed issues:
  - ❑ BW amplifier,
  - ❑ Subtraction with amplifier
  - ❑ S/H - or Track and Hold.
  - ❑ Area
- ❑ Can we do it other way?
- ❑ Lead to a simpler architecture
- ❑ No amplifiers !
- ❑ **With capacitors we can easily subtract**
- ❑ Speed per cycle may be faster

## SAR DAC – another DAC – speed and area Improvement


We want to generate

Vref/2....	1 <sup>st</sup> clock cycle
Vref/2 +/- Vref/4..	2 <sup>nd</sup> clock cycle
Vref/2 +/- Vref/4 +/-Vref/8	3 <sup>rd</sup> clock cycle
Etc..., ,	

So lets use capacitor DAC to do this.

 
## Charge Distribution SAR DAC Operation

Step 1.- clock n=1, reset everything to 0 point – “wasted state” but needed because capacitors plates are held at a “value” for DC



 
## Generate $V_{ref}/2$ to Compare

Step 2.- clock n=2, generate  $v_{ref}/2$  to compare with input




## Compare to $V_{ref}/2$ and Generate $V_{ref}/2 + V_{ref}/4$

still in time = "2"

 


in time = "3 " add  $\frac{1}{4} v_{ref}$

Re arrange C to units

 

## Generate $V_{ref}/2 + V_{ref}/4$

 

$$\Delta V_{out}(3T) = (0.25C / C) V_{ref}$$

$$\Delta V_{out}(3T) = 1/4 \text{ (time the signal delta)}$$


$$V_{out}(3T) = V_{ref}(2T) + 1/4 V_{ref}$$

$$\boxed{\mathbf{V_{out}(3T)= V_{ref}/2+V_{ref}/4}}$$

**Generate the Minus  $\rightarrow V_{ref}/2 - V_{ref}/4$**

in time = “3” add  $-1/4$  vref


**2 operations**

 

$$\Delta V_{out}(3T) = -0.5 + 0.25$$


$$V_{out}(3T) = V(2T) + -0.5 + 0.25$$

$$\Delta V_{out}(3T) = 1/4 V_{ref}$$

 


## Generate the Minus of the Input as well Easily

$T=1$

 


$T=2$

 

And on.. And on.. Until the number of bits  $M+1$




## .... Let's Look at complete C-DAC SAR

 

**5bit dac**
   
## Fring. Caps to improve area density (capacitors on IC)


$$C = C_o WL \longrightarrow C = C_o WL + 2C_{fr} (W + L)$$



**Accuracy in silicon is low ~ +/-20%**  
**Low temperature/V dependency**  
**Matched well** What about plate parasitic ?

Co= 1-2 ff/uu if Metal to Metal sandwitched  
 With Fringing effect into the picture:

## Fring. Capacitors-Parasitic Errors

 

C parasitic ~0.1-0.2C total! – how to design it out..

## Silicon Transistors as Capacitors

**Capacitors from MOS (transistor) → triki.- watch the plates potential.**

In accumulation (off) -----→  $V_{gs} < V_t$  ( n ch)


$$C = C_o WL$$

$C_O \sim 12fF$  if thin oxide is used ( 90nm)

Cap is to the substrate ( N well probably)

In depletion (on) -----→  $V_{gs} > V_t$

P can be in both


 


Cap is to the drain sources!

Next to  $V_t$  –  $C$  drops to ~ 0.3 its max value


It's a voltage dependent capacitor –

  doesn't work good with 0 volt across it (integrator and opamp)



## Silicon Transistors as Capacitors

Why not work here ? – ah.. Veractor..

 

The NMOS capacitor is in inversion for  $V > 0$ .

Giovanni Anelli, CERN

## Errors in SAR ADCs

- ❑ Its an accurate structure
- ❑ Subtraction using caps
- ❑ Low/average power: SH, one comparator, DAC, and Logic
- ❑ 8b-200msps is possible
- ❑ But: Need Accuracy in the DAC.
- ❑ Comparator offset < ~ 0.5 LSB – Easily calibrated

## ***ACCURACY : FUNCTION OF DAC (CAPACITORS) MATCHING***

## Matching

$$C \approx \epsilon \frac{WL}{t} \longrightarrow \left( \frac{\Delta C}{C} \right)^2 = \left( \frac{\Delta \epsilon_r}{\epsilon_r} \right)^2 + \left( \frac{\Delta t_{ox}}{t_{ox}} \right)^2 + \left( \frac{\Delta L}{L} \right)^2 + \left( \frac{\Delta W}{W} \right)^2$$

- Once again can correlate to area with good accuracy
- How is it given

1. A\_deltaC/C is based on sigma of (deltaC / C) vs. 1/sqrt(WL)  
 typ. number 2fF/micron square

## Matching

To get to the best matched number you need to :

- ❖ Use identical geometries
- ❖ Use large unity capacitance (minimize fringing)
- ❖ Use common centroid arrangement
- ❖ Use dummy capacitors
- ❖ Use shielding
- ❖ Account for the connections' contribution
- ❖ Don't run connections over capacitor
- ❖ Place capacitor in low stress areas
- ❖ Place capacitors far from power devices

## An Example

Find the LSB capacitor size (and total capacitors)  
 for a 12b SAR ADC Given that 10ff unit match to 0.8%. (to 1 sigma)

$$C_{unit} = 10fF \quad \left(\frac{\Delta C}{C}\right)_{unit} = 0.8\%$$

$$\Delta_{noise} = \sqrt{\frac{\Delta^2}{12} + [Distortions]^2 + \frac{KT}{C_T}}$$

$1pF \sim 64E^{-6} V/\sqrt{Hz}$

Let give  $[Distortions] \gg \frac{1}{3} LSB weight$

$$\left[\frac{\Delta C}{C}\right]_{Full\ scale} = \frac{1}{3} \left[ \frac{1}{2^n - 1} \right] = 0.0081\%$$

$$\left[\frac{\Delta C}{C}\right]_{LSB} = [0.0081] \sqrt{2^n - 1} = 0.518\%$$


$$C_{LSB} = [C_{unit}] \left[ \frac{0.8}{0.518} \right]^2 = 23.85fF$$

$$C_{total} = 97.67pF$$

Not to influency the converter

$$C_{LSB} = [C_{unit}] \frac{\left[ \left( \frac{\Delta C}{C} \right)_{Full\ scale} \sqrt{2^n - 1} \right]^2}{\left[ \left( \frac{\Delta C}{C} \right)_{unit} \right]^2}$$

 
## Example of Matching Requirement on F. Scale (MSBs)



$2 \text{ to the } n \times 2/3$


( $2/3$  only as example not to give all the error to the linearity)
 
## How to Build One – What is Needed to Look for



Source: B. P. Ginsburg sept. 2005

## Design Examples

 


## Word on the References

References issues:
 
### REFERENCE HOLDING BREF IS HARD TO DO:

During switching phase references  
has to settle every clock (fast) They are op amp  
driven therefore make the design almost as op-amp based

Also the comparator must settle every cycle. (faster)



## Summary – C or R DAC

- ❑ Most time absolute value can move  $=/-15\%$  to  $+/-20\%$  and does not significantly matter but ratio's do
- ❑ However, the bigger the area the better the matching
- ❑ Typical values 30ff can match 3-sigma to better  $\sim 0.5\%$
- ❑ Matching is area dependent generally by the root of  $(W \times L)$
- ❑ In SAR there is contradiction large is good for matching however speed is degraded a lot R switch  $\times$  C and its multiplied N bit for a complete cycle.

- ❑ Without amplifiers power is set by S/H, References, 1 comparator, and digital blocks+clocks
- ❑ Generally for lower number of bits – logic may be significant
- ❑ Area. For many bits analog set the power waist.
- ❑ Logic running multiple times for each conversion and capacitor size (forcing a large drive current)
- ❑ Power waist : S/H + Comparator + Reference + Switching/logic

### Good:

- ❑ Lowest possible power- FOM
- ❑ Fewer analog elements,
- ❑ T/H or S/H drive low capacitance

## SAR- Key Points

- ❑ The Feed Back ADC (SAR) offers significant hardware savings compared to flash ADCs because the coarse Quantizer (comparator) resolution  $m$  can be much smaller than the converter resolution.  $N$
- ❑ However, it suffers from drawbacks making it not suitable for many applications because:
  - ❑ It requires  $p = N/m$  passes to generate  $N$  bit output words limiting the throughput
  - ❑ It requires  $N$  bit accurate DAC
  - ❑ It requires faster settling elements
  - ❑ but No need amplifiers !
- ❑ So, if speed is a problem should we combine SARs in time ?– time interleaved 50gsps nice to do..

# End Lecture 7