



Welcome to
046188 Winter semester 2012
Mixed Signal Electronic Circuits
Instructor: Dr. M. Moyal

Lecture 7 part b. + 8

Comparator: Operation and Design

Agenda



Comparator Basics

Architectures

Error Sources

Comparator Examples



Comparator: Non Sampled, Sampled

Error in Comparators

Basic Analysis


Architectures

Special topics – Calibrated and differential

Basic Feed back to boost BW



“SLOW”

 


$$V_{out}(t) = V_{in} [1 - e^{-t/RC}]$$

$$\tau = R * C$$

DC gain=1

“FAST”

 


$$V_{out}(t) = V_{in} [1 - e^{-t(A+1)/RC}]$$

$$\tau(new) = R * C / (A + 1)$$

DC gain=1/1+A


But at v2 DC
gain=A/1+A ~ 1

Simulation: a=2 and a=10

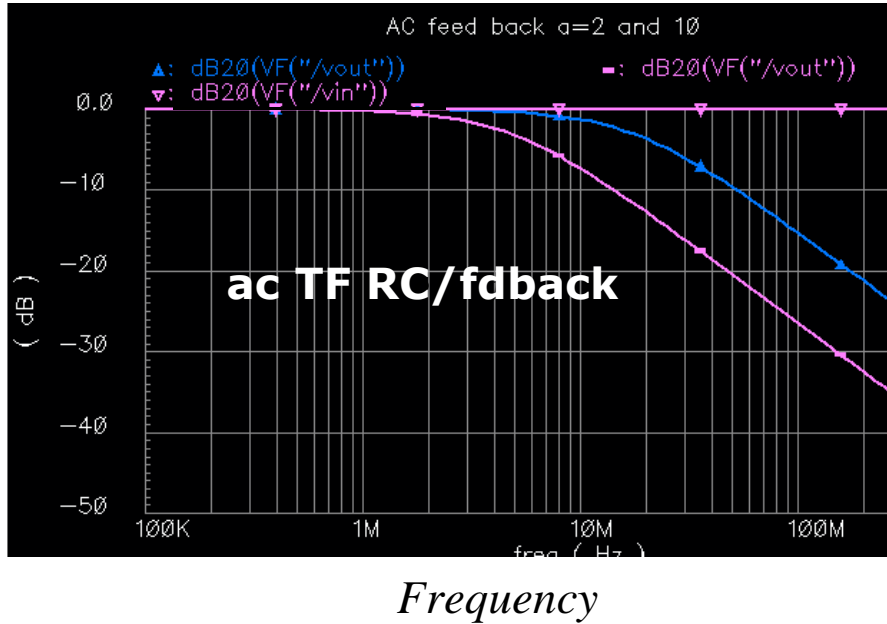

$$V_o / V_i(f)$$


Ac response

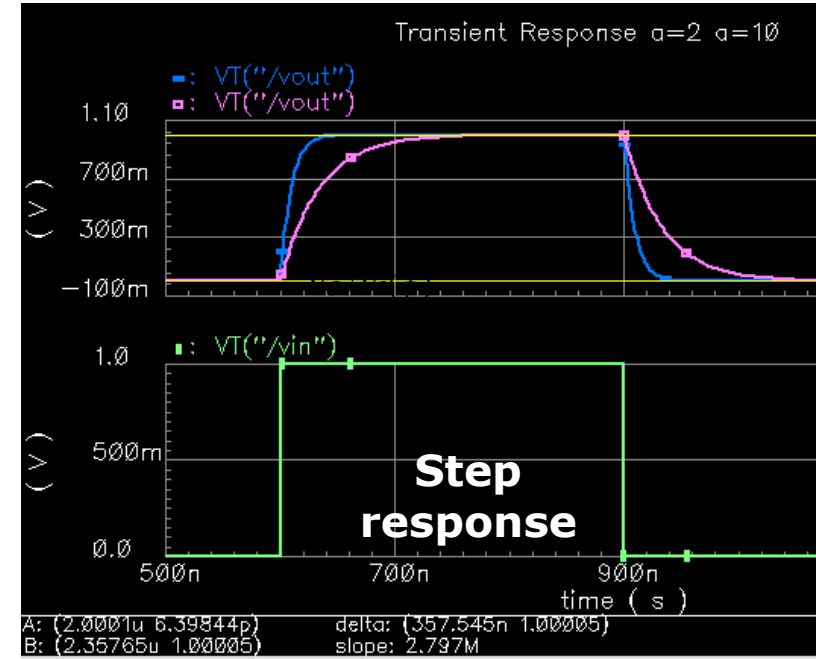


Time

Time domain

Speed and feed back basics

 

Feed _back

 

Removed all compensation



A Comparator:

LINK FROM ANALOG TO DIGITAL – QUANTIZER

Definition: Compare 2 or more input and produce a digital value high or low- “Its a 1 bit ADC !”

Structure:

A chain of gain stages (no feed back-unlike amplifier)


It is used in an “open Loop” configuration to achieve fast digital response (opamps are slow and big)



Basic Architecture1 of comparators

Non Sampled: Continuous Time (CT)

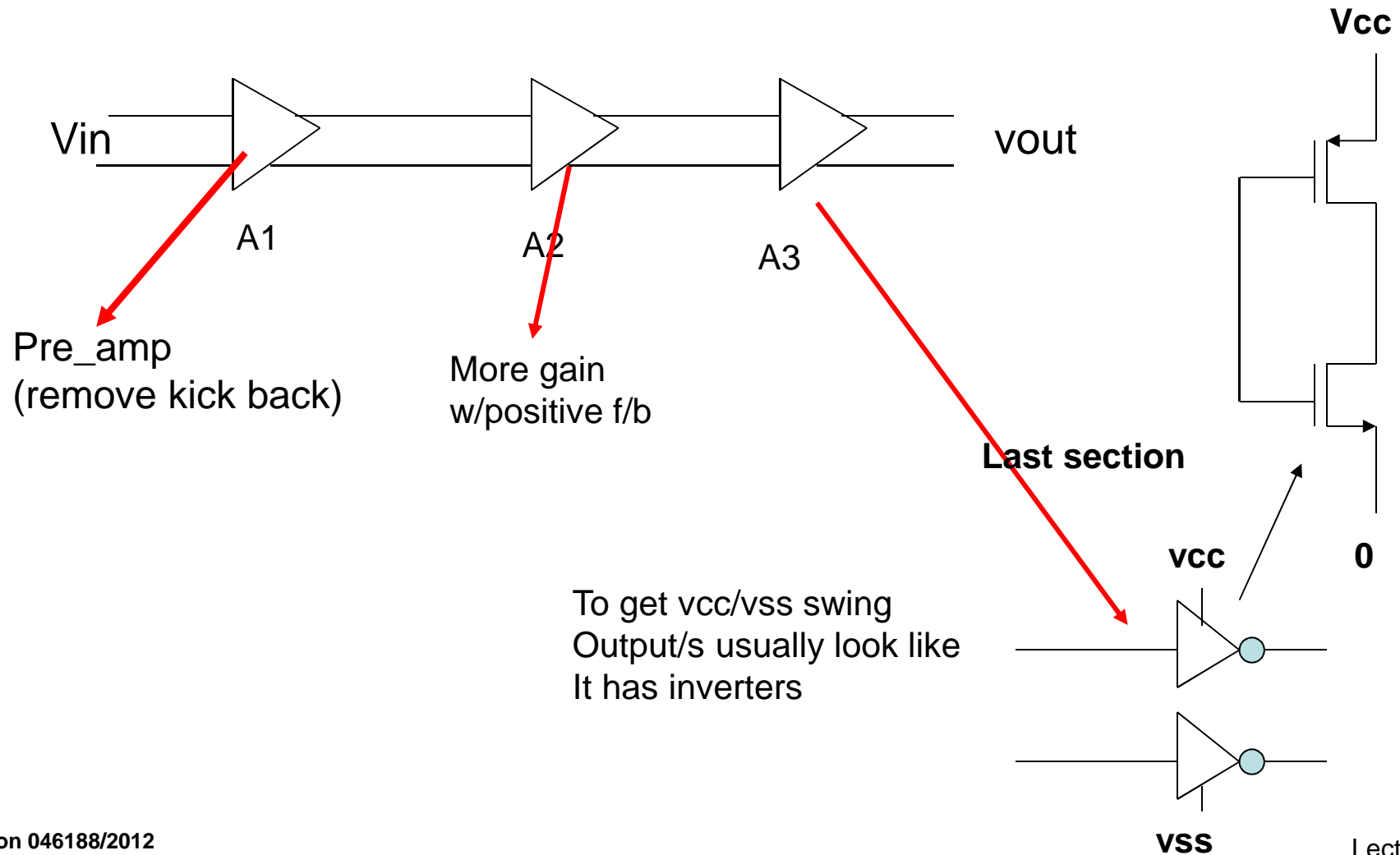Output is gain time input differences:
slow because internal nodes need to be recovered




Mathematical Descriptions (low frequency)



For small $V_{in1}-V_{in2}$

$$V_{out}=A(V_{in1}-V_{in2})$$

A is the gain of the combine structure

 

For all $V_{in1}-V_{in2}$

V_{out} =clamp at either supply

Ideal


$V_{out}=A(V_{in1}-V_{in2})$ results fall between supplies

(realistically its exponential)

$$V_{out}=V_{dd} \text{ if } A(V_{in1}-V_{in2}) > V_{dd}-V_{ss}$$

$$V_{out} = V_{ss} \text{ if } A(V_{in1}-V_{in2}) < V_{dd}-V_{ss}$$

Mathematical Descriptions with noise.

 

Important model in
Sigma delta ADCs

exact model if e is defined properly
ex. $y = \text{sgn}(x)$, then $e = y - x = \text{sgn}(x) - x$

becomes an approximation when we
claim noise is independent

Basic Architecture 2 type-Latched




Sampled Comparator:

Much faster

clamp high gain stages

Need clock or digital signal

Concept:

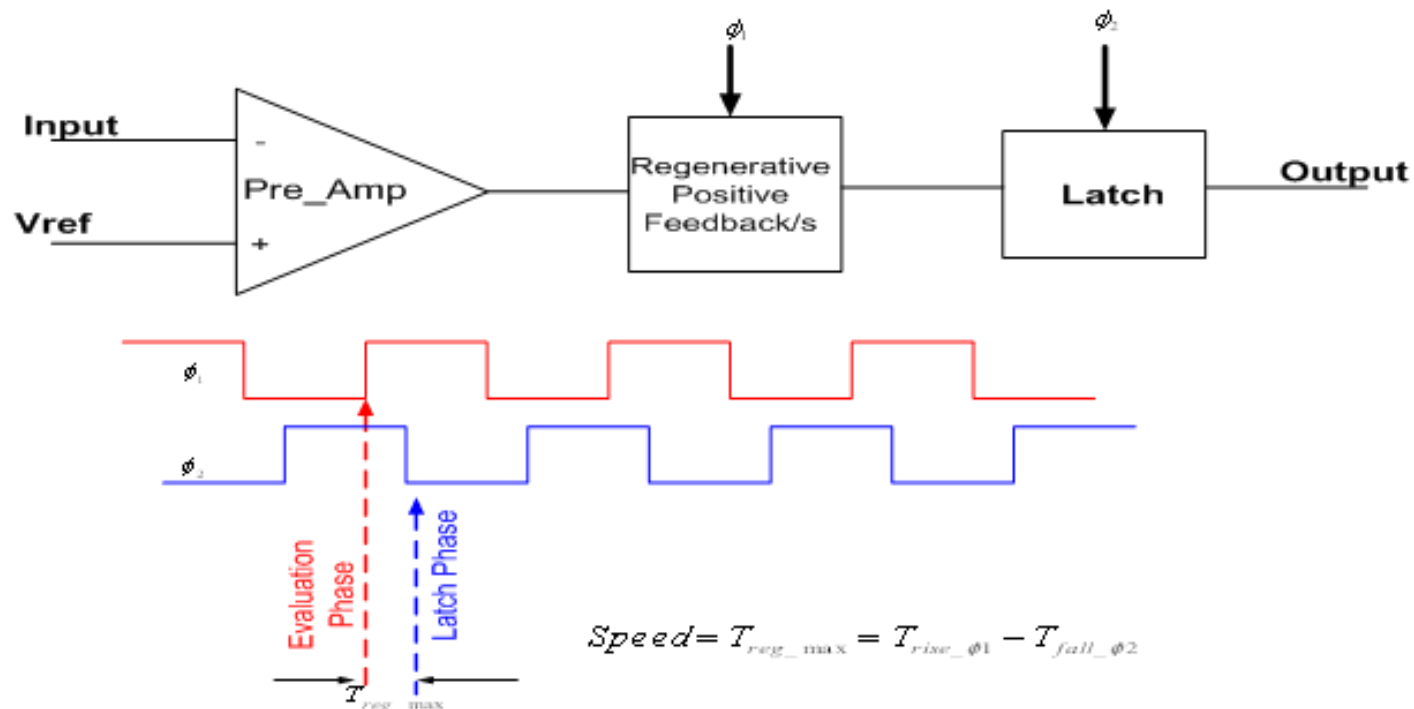

Error in Comparators:



Error in Comparators:

Gain

Offset

Meta State

Speed

Kick Back

Noises and supply noise

Main Parameters Definitions




- **Input Offset** – It is the voltage that must be applied to the input to obtain the crossing point between low and high logic level
- $V_{out} = A \times V_{indiff}$, $v_{ss} < V_{out} < V_{dd}$ $A=1000$, time is also a factor
- **Sensitivity**- It is the minimum voltage or current that produces a consistent output signal within the expected comparison time- **Meta state**
- **Comparator response time** – It is minimum time interval required to achieve the proper logic output as a response to the minimum input step
- **Overdrive recovery time** – When the input signal is pretty large the gain stage saturates to the positive or negative rails quickly. If the input stage become small, the gain stage takes some time to react and generates the voltage required to produce the output voltage
- **Kick back input noise** – Caused in evaluation state due to transition response: **Switching noise**

Offset and gain basics in comparator



Vos(total)

 

$$Vos(total)^2 = \sqrt{Vos1^2 + Vos2^2 / A1^2 + Vos3^2 / A1^2 A2^2}$$

Key: Vos is a statistic parameter
Further stages (A2 and A3) have larger offset
Using minimum sizes..

Example: 8 bit ADC 1GS/s (through put=2ns)

for 8 bit with Vfs=0.5v , Vdd=1v at 1/10LSB =

A1 x A2 X A3 required ~ 5000 → (1v/(0.5/255 x 10) in under 1ns

If

Vos1=2mv , vos2=10mv vos3=20mv

If we take : A1=10 A2=25 A3=20

$$Vos(total) = \sqrt{2^2 + 10^2 / 10^2 + 20^2 / 10^2 25^2 +}$$

$$Vos(total) = 2.23mV$$

Transistor as linear gain blocks




Gm Rout ... diff stage..



Basic Analysis- small signal

Non Sampled – Non Latched

 


$$V_{out}(t) = V_{in} \cdot g_m \cdot R_{out} \cdot (1 - e^{-t_{reg}/\tau})$$


$$\text{Where: } \tau = R_{out} \cdot C_{out}$$

$$g_m = i/v_{in}$$

With Positive feedback- sampled

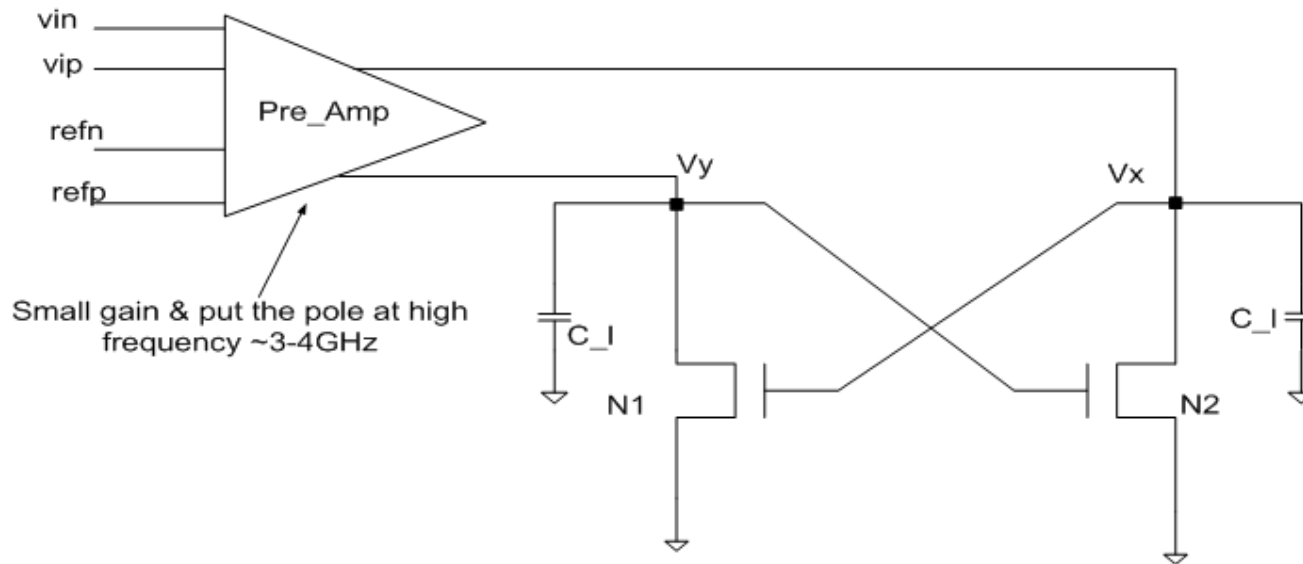

 Small gain & put the pole at high frequency ~3-4GHz



Small signal representation



Math- Positive feed back comparator latch

$$g_m \cdot V_y = -C_L \cdot \frac{dV_x}{dt} - \frac{V_x}{R_{out}} \quad g_m \cdot V_x = -C_L \cdot \frac{dV_y}{dt} - \frac{V_y}{R_{out}}$$


$$\begin{cases} \tau \cdot \frac{dV_x}{dt} + V_x = -A \cdot V_y \\ \tau \cdot \frac{dV_y}{dt} + V_y = -A \cdot V_x \end{cases} \rightarrow \text{where} \quad \begin{aligned} \tau &= R_{out} \cdot C_L \\ A &= g_m \cdot R_{out} \end{aligned}$$

$$\tau \cdot \frac{d(\Delta V)}{dt} = \Delta V(A-1)$$

Solution \rightarrow

$$\frac{\tau}{A-1} \cdot \frac{d(\Delta V)}{dt} = \Delta V$$

 
$$\Delta V = \Delta V_0 \cdot e^{\frac{A-1}{\tau} t} \approx \Delta V_0 \cdot e^{\frac{g_m \cdot t}{C_L}}$$
$$\frac{A-1}{\tau} = \frac{g_m \cdot R_{out} - 1}{R_{out} \cdot C_L} \approx \frac{g_m}{C_L}$$



Cascade stages:




Band width reduction

 

$$h(t) = h_1(t) * h_2(t) = \left(e^{\frac{g_m \cdot t}{C_L}} * e^{\frac{g_m \cdot t}{C_L}} \right) = t \cdot e^{\frac{g_m \cdot t}{C_L}}$$

 
$$\Delta V_{out}(t) \approx \Delta V_{in} \cdot K \cdot t \cdot e^{\frac{g_m \cdot t}{C_L}}$$



Note: if we have n-stages of the regenerative feedbacks then

$$h_n(t) = h_1(t) * h_2(t) \dots * h_{n-1} * h_n = \left(e^{\frac{g_m \cdot t}{C_L}} * e^{\frac{g_m \cdot t}{C_L}} \dots * e^{\frac{g_m \cdot t}{C_L}} * e^{\frac{g_m \cdot t}{C_L}} \right) = \frac{t^{n-1} \cdot e^{\frac{g_m \cdot t}{C_L}}}{(n-1)!}$$
 
$$v_{oN} = \frac{\omega_u^N}{s^N} v_{in}$$






Meta-Stability In Comparator

- Meta-stability is a potentially catastrophic event that can occur when asynchronous inputs and regenerative/flip-flops are used
- Meta-stable outputs are not logic high or logic low and cause delays and system failures
- Meta-Stability is a probabilistic event, because the difference between the input signal and the reference voltage is a random variable
- The smaller the difference between the input signal and reference voltage, the longer the decision time required. On the limit the decision time can approach infinity

Not defined place

Example in class

 



Analytical Derivation of Meta-Stability & Mean Time To Failure (MTF)

- The probability event given following: where t is the actual comparison time, T is the allowed time

$$\Pr(t > T) = e^{\left(-\frac{A}{\tau} \cdot T\right)} = e^{-\frac{g_m \cdot T}{C_{out}}}$$


- If one can have a collection of N such comparators all clocking at a frequency f_s , then one can find MTF following

$$MTF \approx \frac{e^{\frac{A}{\tau} \cdot T}}{N \cdot f_s} = \frac{e^{\frac{g_m \cdot T}{C_{out}}}}{N \cdot f_s}$$

~ Set it for > month

example in class

The 'CML'

 

$$I_B = I_1 + I_2$$

$$I_O = I_1 - I_2$$

$$I_B^2 - I_O^2 = 4I_1I_2$$

$$I_1 = k(V_1 - V_X - V_T)^2$$

$$I_2 = k(V_2 - V_X - V_T)^2$$


$$V_i = V_1 - V_2 = \sqrt{\frac{I_1}{k}} - \sqrt{\frac{I_2}{k}}$$

$$kV_i^2 = I_1 + I_2 - 2\sqrt{I_1I_2} = I_B - 2\sqrt{I_1I_2} = I_B - \sqrt{I_B^2 - I_O^2}$$

$$I_O = \sqrt{2I_Bk} \cdot V_i \sqrt{1 - \frac{k}{2I_B} V_i^2}$$


large signal transfer: assuming square law devices in saturation region.

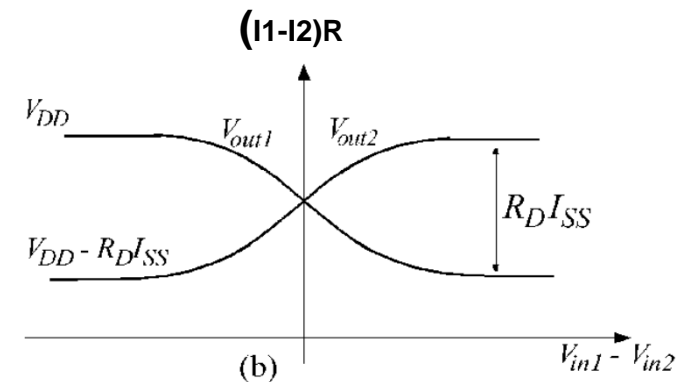Express I_{out} as a function of differential V_i.



Resulting expression is a linear term multiplied by a non-linear square root function.

The 'CML'

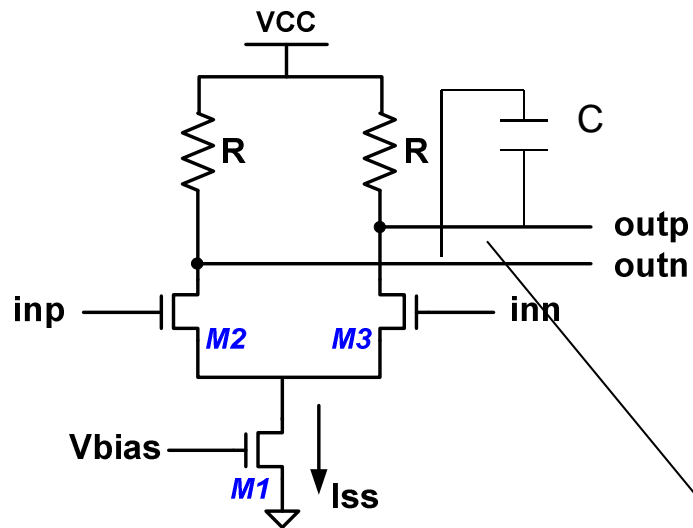

● CML (current mode logic) is a differential structure

- **Basic block in Analog/Mixed signal**
- **Less sensitive to supply noises and noise from aggressors**
 - Less noise (AC current) injected to supply -> less supply noises in analog portion
- **Good for high speed operation**
 - No PMOS devices (slower)
 - Differential switching is faster than single ended rail-to-rail
 - Noninverting cells are just as fast as inverting cells (unlike CMOS: inverter vs. buffer)
- **Drawback: Static current consumption**

- The output load (CL) and the operation speed (BW) determine the value of R*
- CL must include the capacitance of the next stages and all parasitic capacitances of wires and Cgd of switching transistors in differential pair
- f must be taken higher than target frequency for margin (10% higher)
- When used in large signal inputs !
- The typical CML swing for 1.2V process is 400mV -> this determines Iss, Iss = 400mV/R

1. P. Heydari & R. Mohanavelu, "Design of Ultrahigh-speed Low-V CMOS CML Buffers..", 2004

$$f_{3dB} = \frac{1}{2\pi RC}$$

$$R = \frac{1}{2\pi C f_{3dB}}$$


$$G_{m_avg} = \frac{g_{m_ss}}{\sqrt{2}}$$



Front stage Architectures- with resistors

 1. Use small values of R_1

- Minimizes swing
- Shortens time constant




$$V_{out}(t) = V_{in} \cdot g_m \cdot R_{out} \cdot (1 - e^{-t_{reg}/\tau})$$

Where: $\tau = R_{out} \cdot C_{out}$

2. Use Passive Clamps


- Limits Swing
- Adds parasitics

 

$$BW = 1 / 2\pi(R_{out}C)$$

 3. Use active nulling clamps

- Good in principle
- Tough clock generation problem




Source: P Gray

Summary:
 Number of stages and gain needed
 is process and project dependent no fixed analytical solution.


Best empirical gmR=4-8 number of stages ~ 2-4

 Input stage: Architectures options- using P cmos




$g_m \times \text{what}$

A

 

$G_m \times R_{op}/R_{on}$
Kickback
Large gain


B

 

$G_m \times 1/g_{mp}$
Low gain



C

Added feed back to load

 

positive feedback to raise R_{out}


Effective rout =infinite

  



Values close to ∞ !

Source: Willy Snasen 2005

Input stage: Architectures options

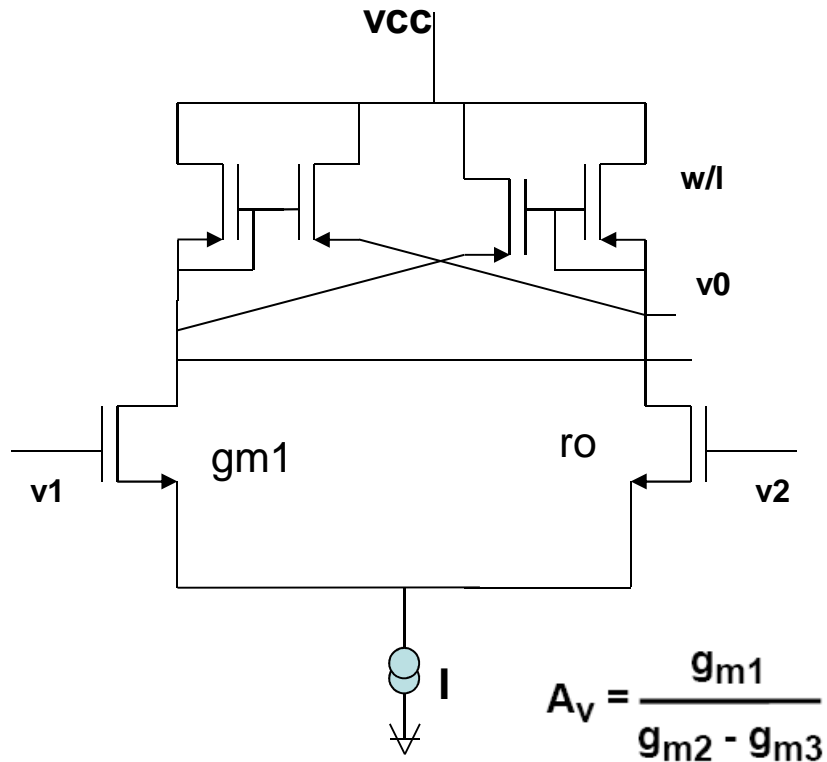


$AV \sim g_{m1} \times r_o$

 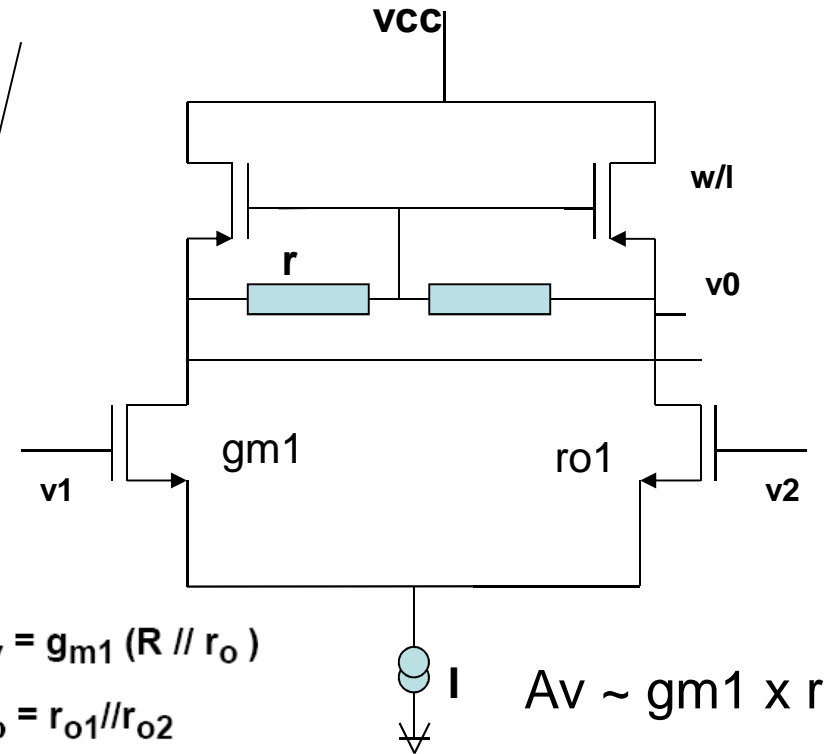

Source: Willy Snasen 2005



Comparator Examples

 

Simple


Good for low supply

Reset switch to ground

Kick back

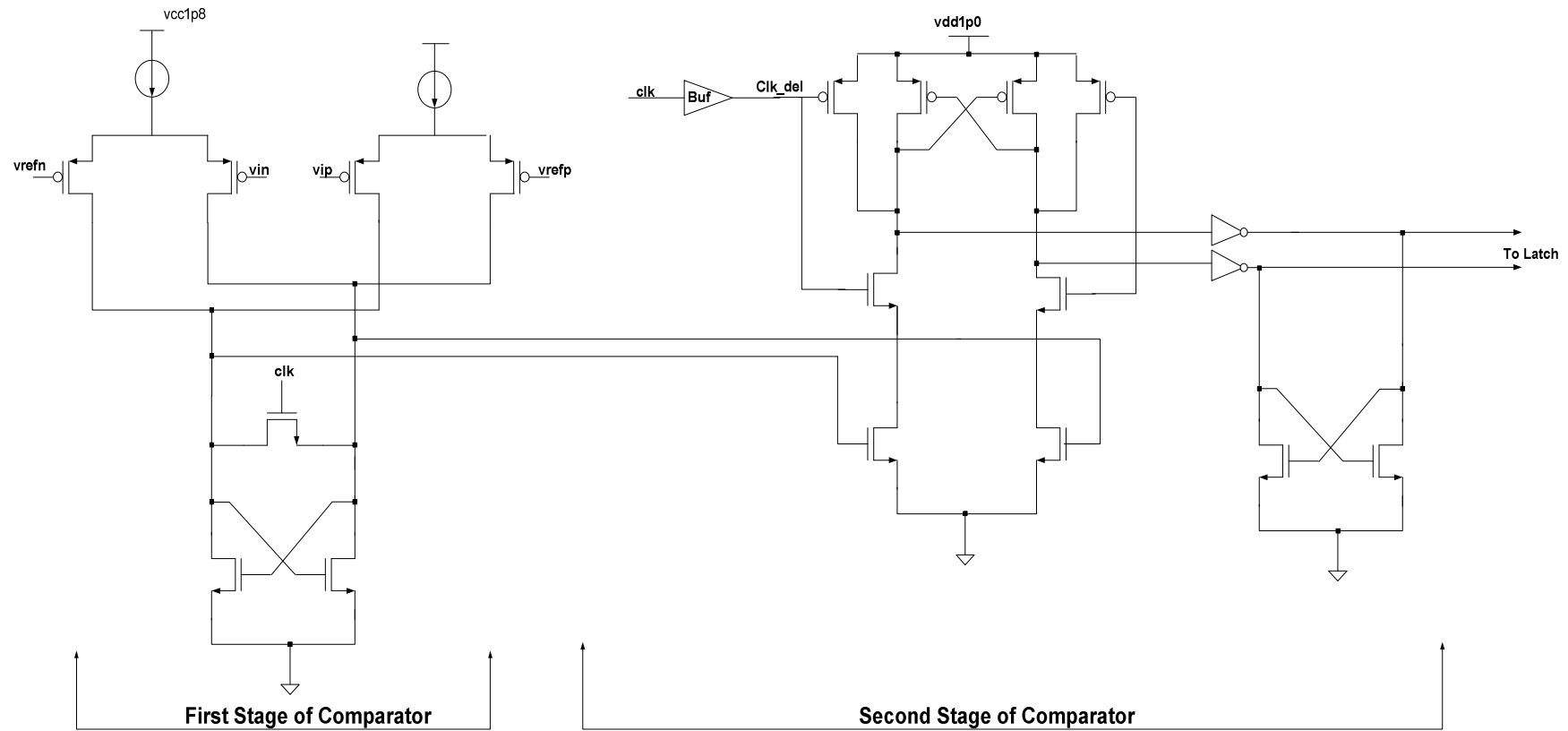Question can the outputs (inverter) swing to Vss ?

Differential input Two Stage Comparator Option (no pre_amp)



More Example of comparators

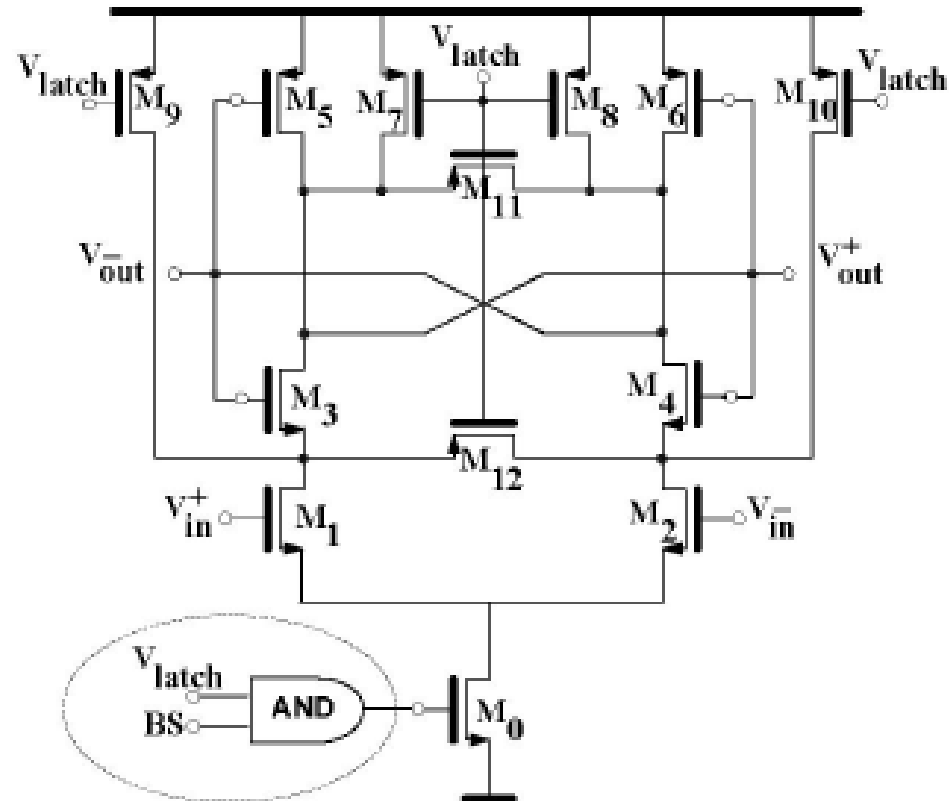


Fig. 5: High speed comparator and its switching circuit


A Power-Efficient 1.056 GS/s Resolution-Switchable
5-bit/6-bit Flash ADC for UWB Applications

Jun-Xia Ma, Sai-Weng Sin, Seng-Pan U¹, R.P.Martins²



More Example of comparators

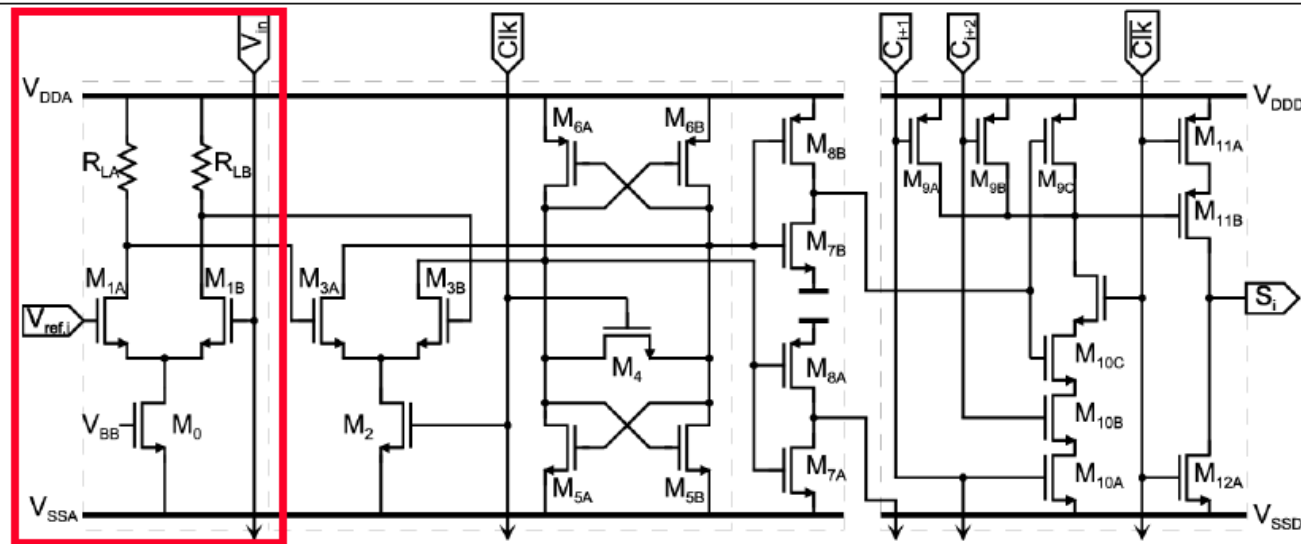Special Topics – Calibrated and differential Architectures examples



- ◆ **Pre-amplifier [M1a,M1b]**
 - Differential Pair with resistive load
 - Reduce Kick-back noise
 - Reduce Input Referred Offset Comparator

Source: Esat-Micas essirc00




Offset calibration of Comparators:

Why : Main reason lower input capacitance




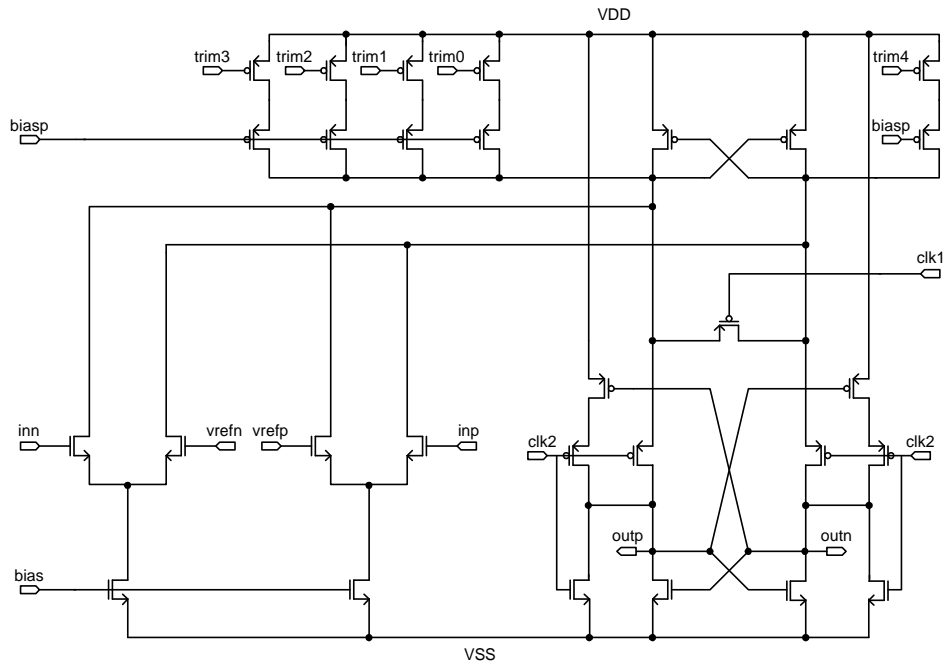DIFFERENTIAL: LATCHED With CALIBRATION AND DIFFERENTIAL!



A 10.3GS/s 6bit (5.1 ENOB at Nyquist) Time-Interleaved/Pipelined ADC Using Open-Loop Amplifiers and Digital Calibration in 90nm CMOS

Ali Nazemi¹, Carl Grace¹, Lanny Lewyn¹, Bilal Kobeissy¹, Oscar Agazzi^{1,2}, Paul Voois¹, Cindra Abidin¹, George Eaton¹, Mahyar Kargar¹, Cesar Marquez¹, Sumant Ramprasad¹, Federico Bollo², Vladimir A. Posse¹, Stephen Wang¹, Georgios Asmanis¹
ClariPhy Communications, Inc., 16 Technology Drive, Suite 165, Irvine, CA 92618, USA, E-mail: ali.nazemi@clariPHY.com
²ClariPhy Argentina S.A., Cordoba, Argentina

 

Comparator schematic with digital offset calibration.



End Lecture 7b + 8