



Welcome to  
046188 Winter semester 2012  
Mixed Signal Electronic Circuits  
Instructor: Dr. M. Moyal

## **Lecture 9**

**SUCCESSIVE APPROXIMATION ADC: Operation**

**Design of Time Continuous SARs**

**Design of Switch C SAR**

**Error sources**

EXAM DAY 23/6/09 14 pm ! Available question on project

[www.gigalogchip.com](http://www.gigalogchip.com)




ADC Architectures


SAR ADCs

Error Sources


# Common Data Acquisition Architectures

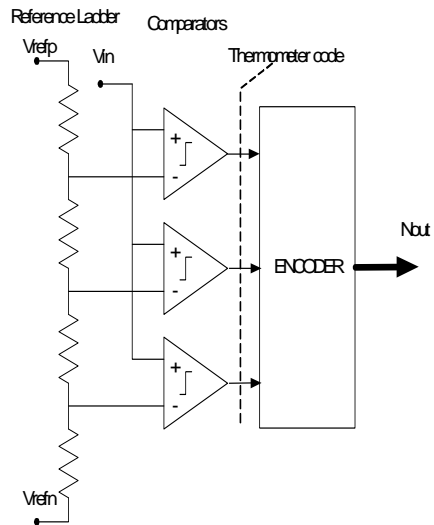

FLASH ADC

 


Sub ranging

 


With S/H


SAR

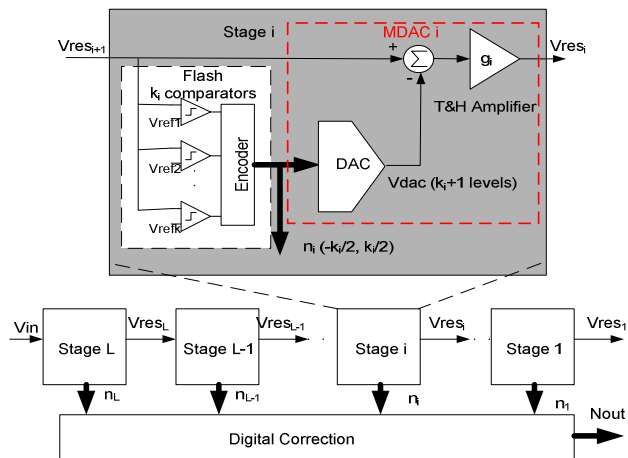

Pipe Line

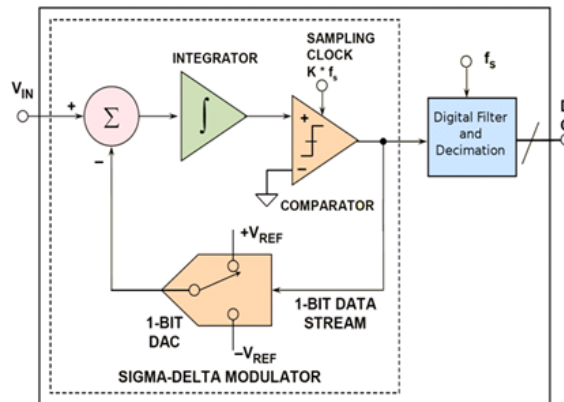

Sigma Delta

 


SD multi bits

 
# Short summary/review of lect 8- s/h..



$$\Delta V = \alpha \frac{C_{ov}}{C_{ov} + C_h} V_{swing} + \frac{q_{inj}}{C_h} + \sqrt{\frac{kT}{C_h}} + \frac{I_{leak} T_h}{C_h}$$




Slow clock Charge almost 0

 

Cp=Ch  
Fast clock Charge split

$$q_{inj} = C_{ox} \times W \times L \times (V_H - V_{in} - V_T)$$

 Cp=Ch reduced charge injection  
Fast clock add short w/2



Source: C. Temes


# Which ADC to use and why




miki

Technion

## ADC Architectures

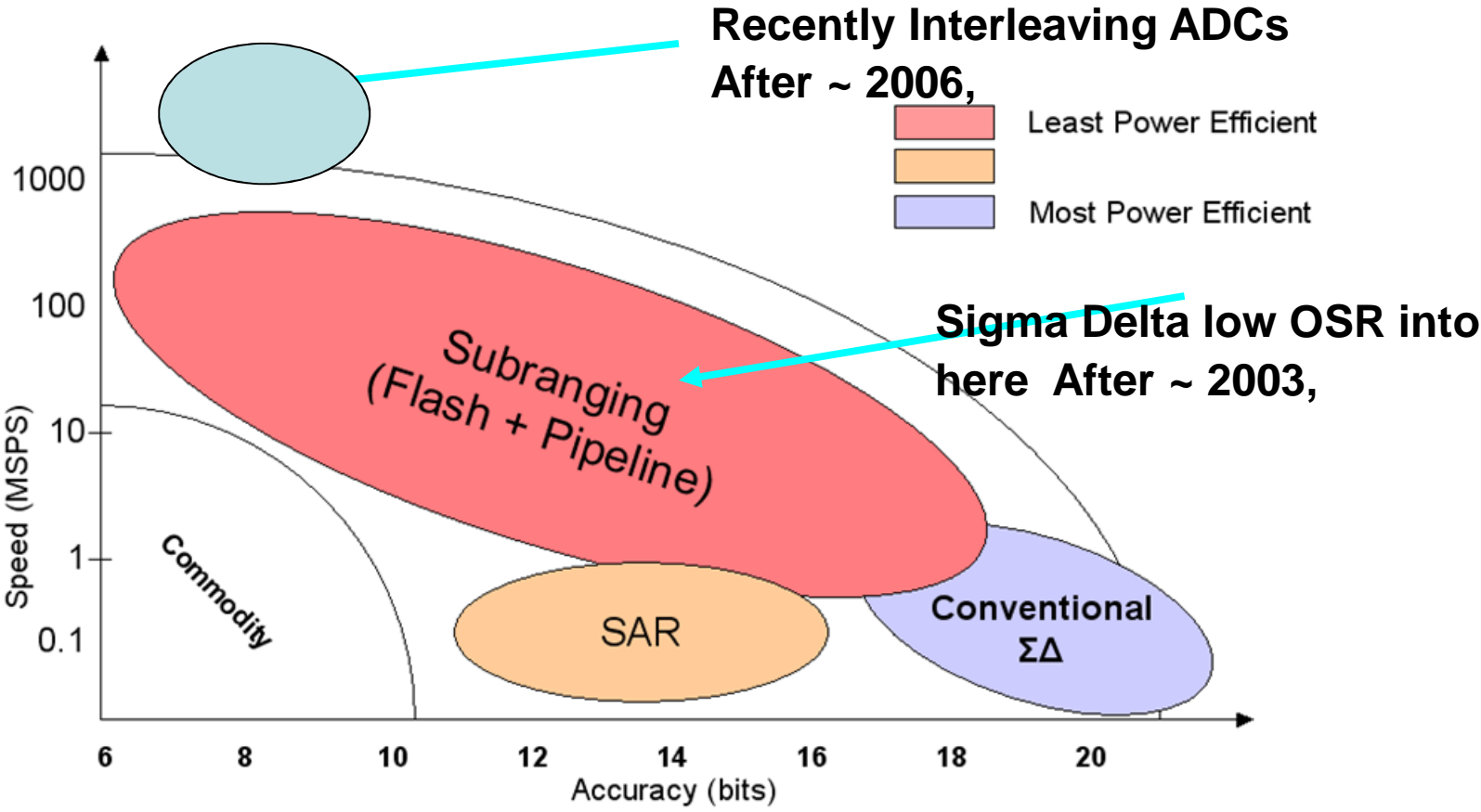

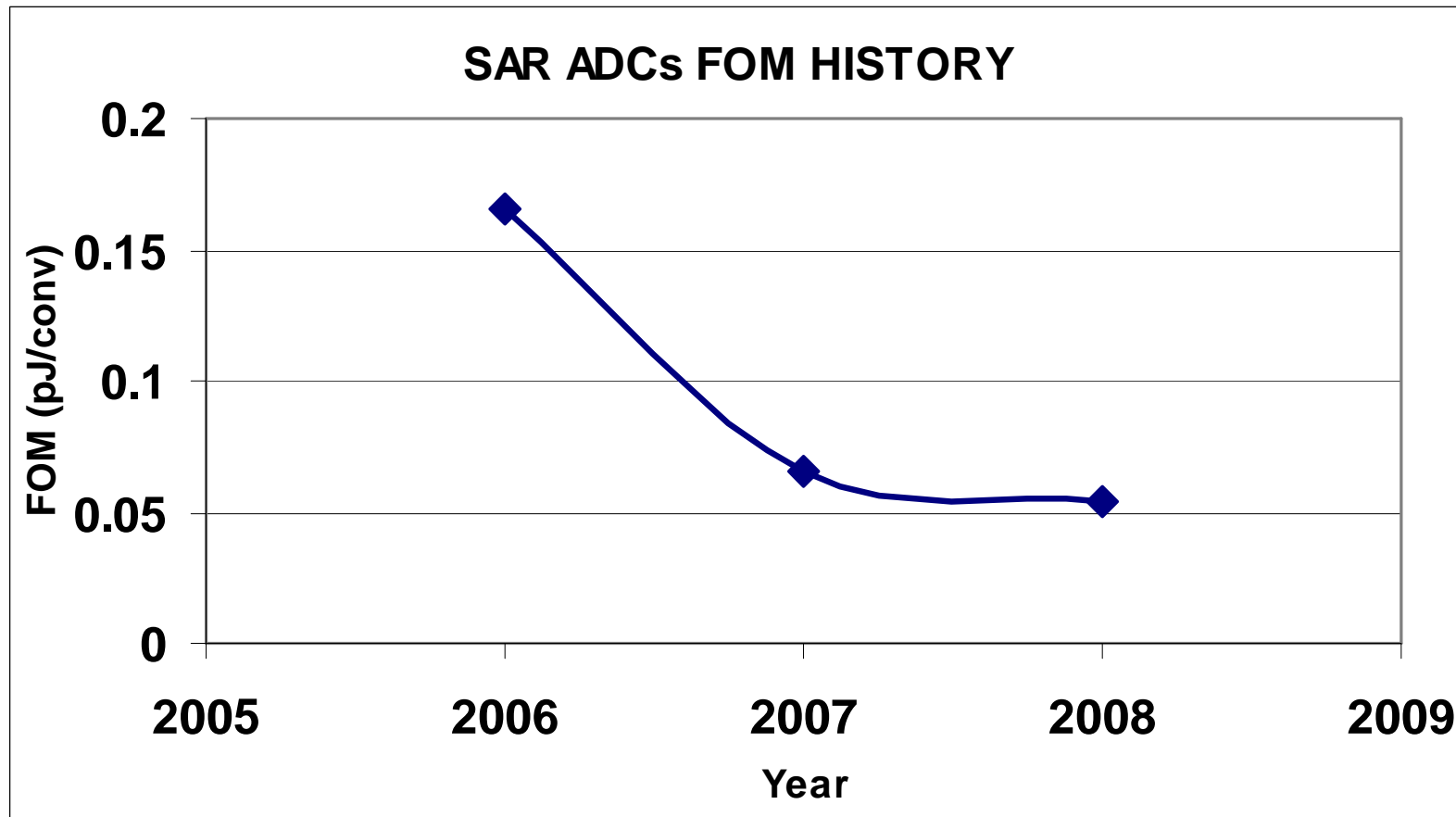


**2006 → 12b & 100Ks/s (180nm CMOS)**

**2007 → 9b & 50Ms/s (90nm CMOS)**

**2008 → 9b & 40Ms/s (90nm CMOS)**

$$\text{Energy/Decision} = \frac{\text{Power}}{\text{SamplingRate} \cdot 2^{N_{bit}}}$$

# Generic ADC:

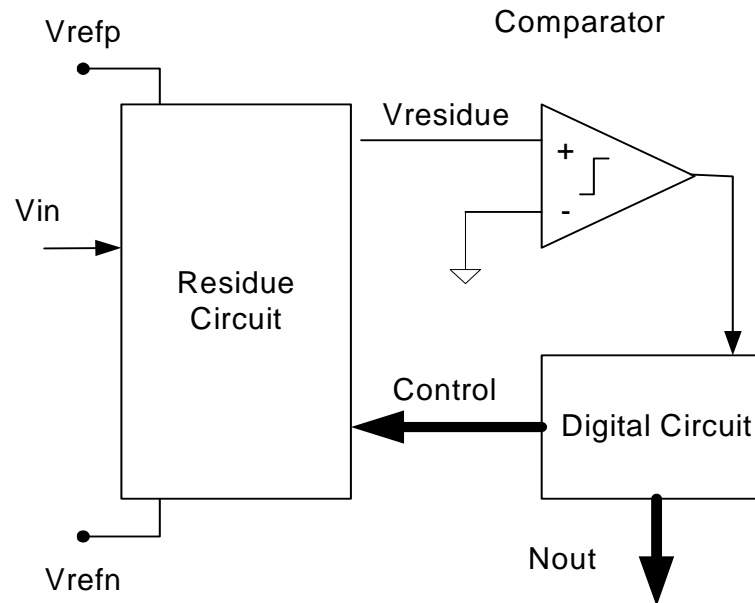

$V$  residue is a function of  $V_{in} - V_{ref}$  .

THE RESIDUE SETS THE SOURCE OF LINEARITY ERRORS

THE COMPARATOR SET THE SOURCE OF SPEED (Offset may be a problem )

Must check always:

Distortion (non linearity's) and ckt noise.

Speed and Power


# Successive approximation ADC



If  $T_s$  is twice maximum BW

And if  $N$  =desired bits

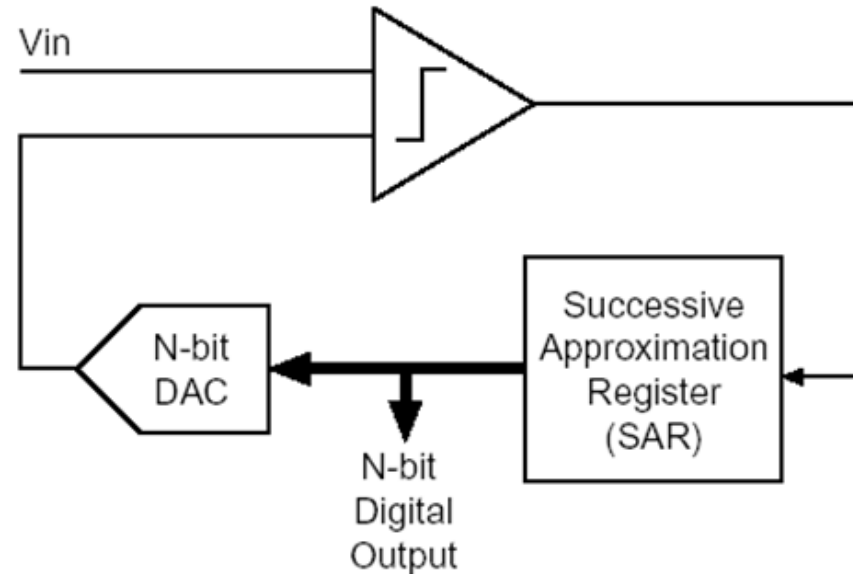**It requires minimum of  $p = N \times T_s$   
passes to generate  $N$  bit  
Output words limiting the through put  
It requires  $N$ -bit accurate DAC  
It requires faster settling elements**




Strict timing is involved- transforming analog to digital each cycle


Comparator runs inside an open loop circuit  
therefore stability and closed loop Band width is not an issue.



# FLOW GRAPH OF SAR ADC

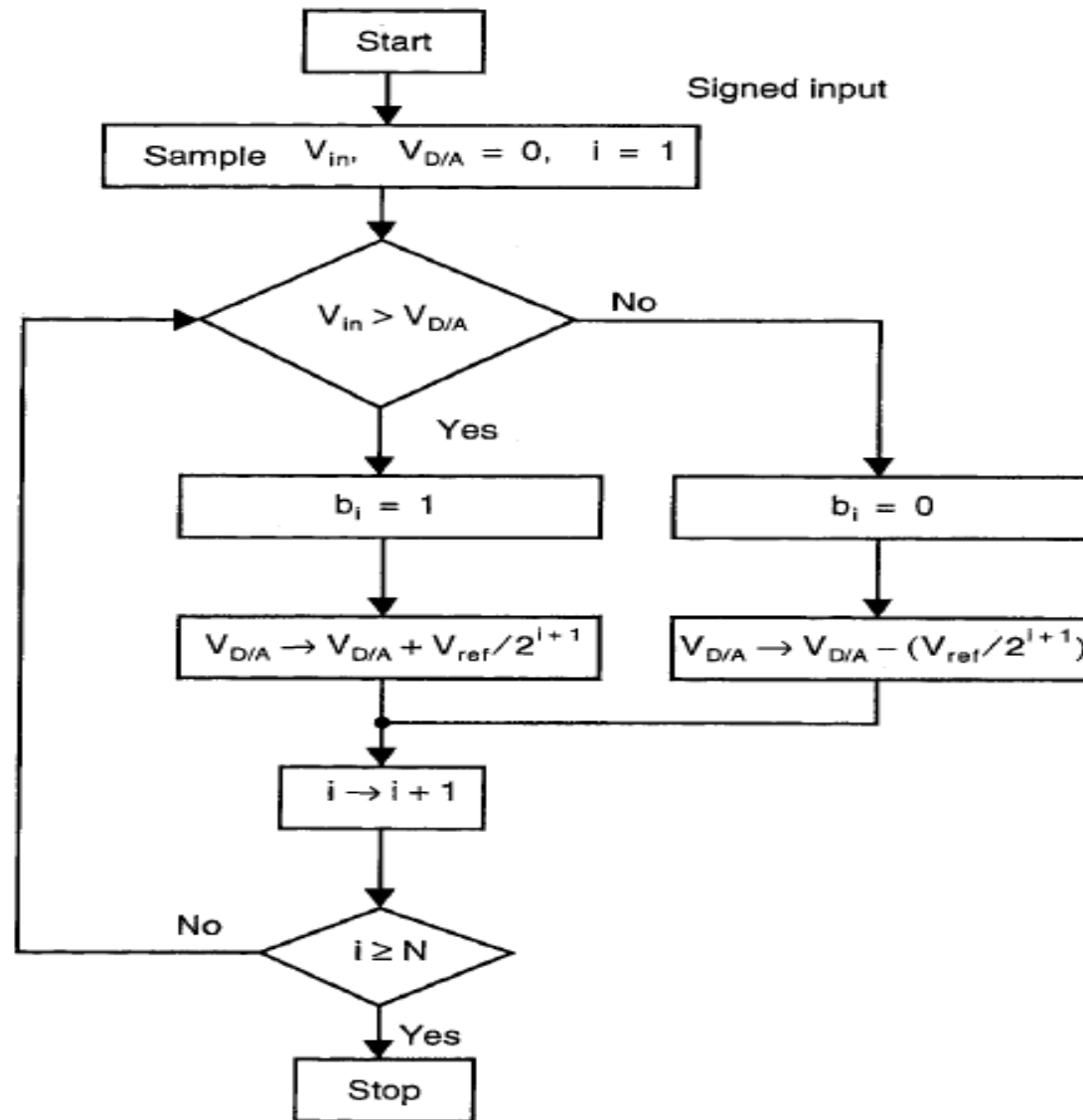


# SAR ADC details

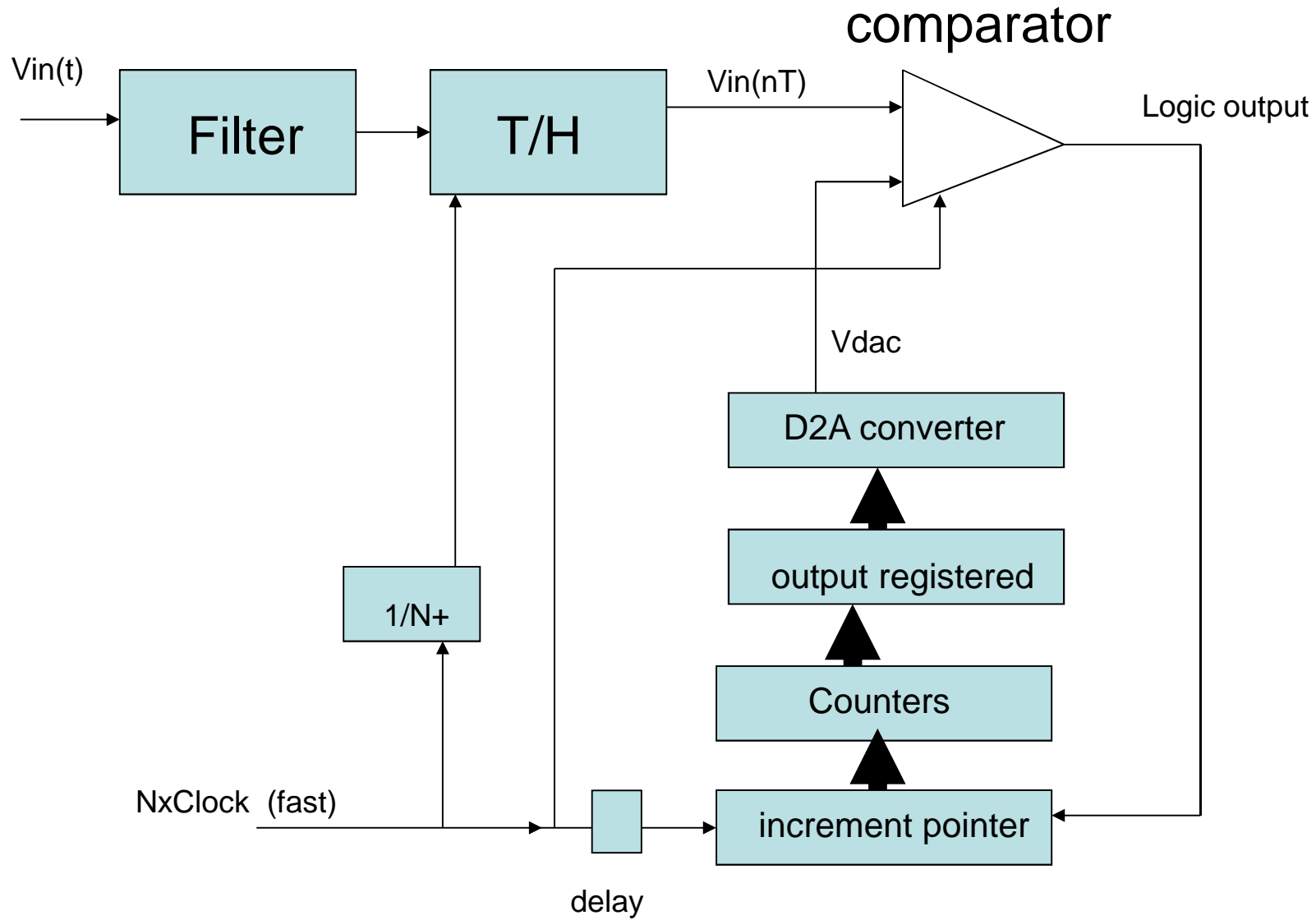




# SAR ADC timing look

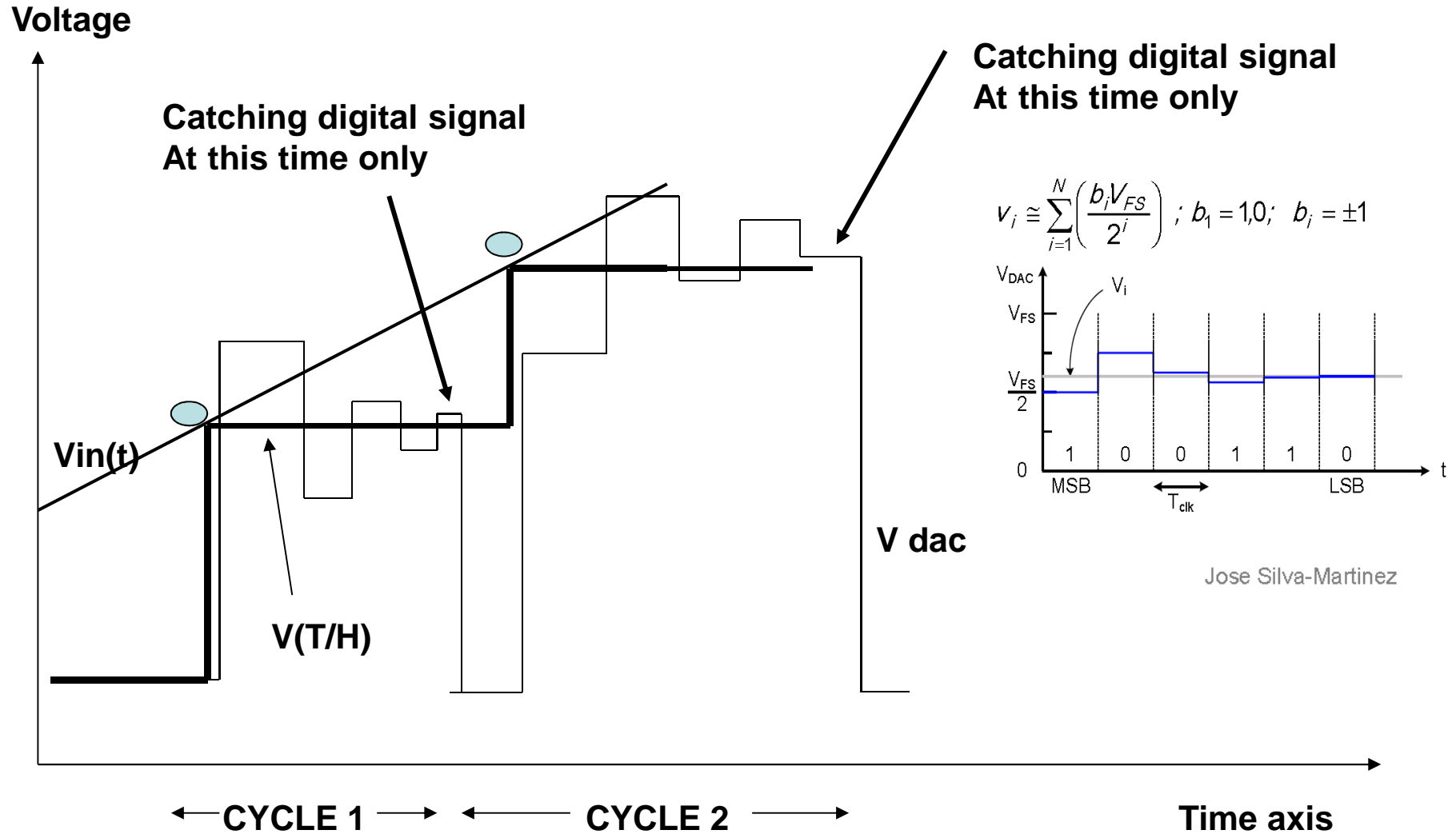

# SAR Operation/Design

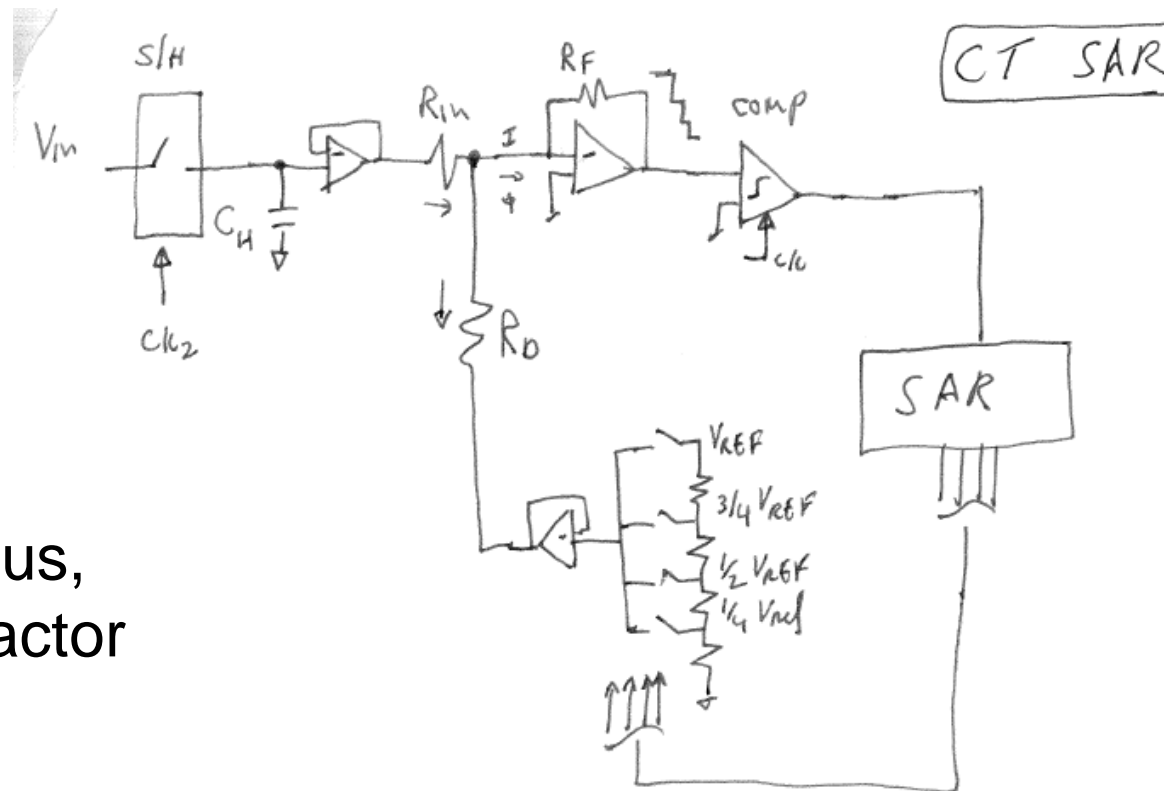


Continuous,  
w. sub tractor

① AT FULL SCALE Figure out  $R_D \Rightarrow \frac{V_{in\ max}}{R_{in}} = \frac{V_{REF}}{R_D}$

$$R_D = \left[ \frac{V_{in\ scale}}{V_{REF}} \right]^{-1} \cdot R_{in}$$



## 1<sup>st</sup> step sample and hold

 


Covered in lecture 8

We know the errors,  
We know the speed needed  
We can proceed to build the block
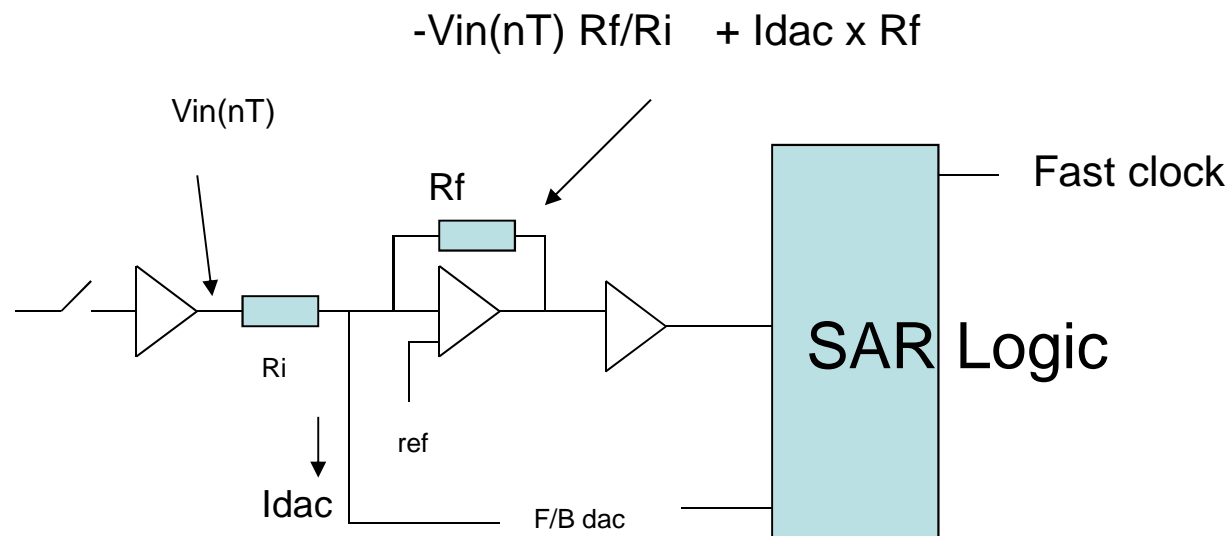
# Example, SAR Analog loop



2<sup>nd</sup> step the sampled voltage part is being converted to I




Next how to build  $I_{dac}$
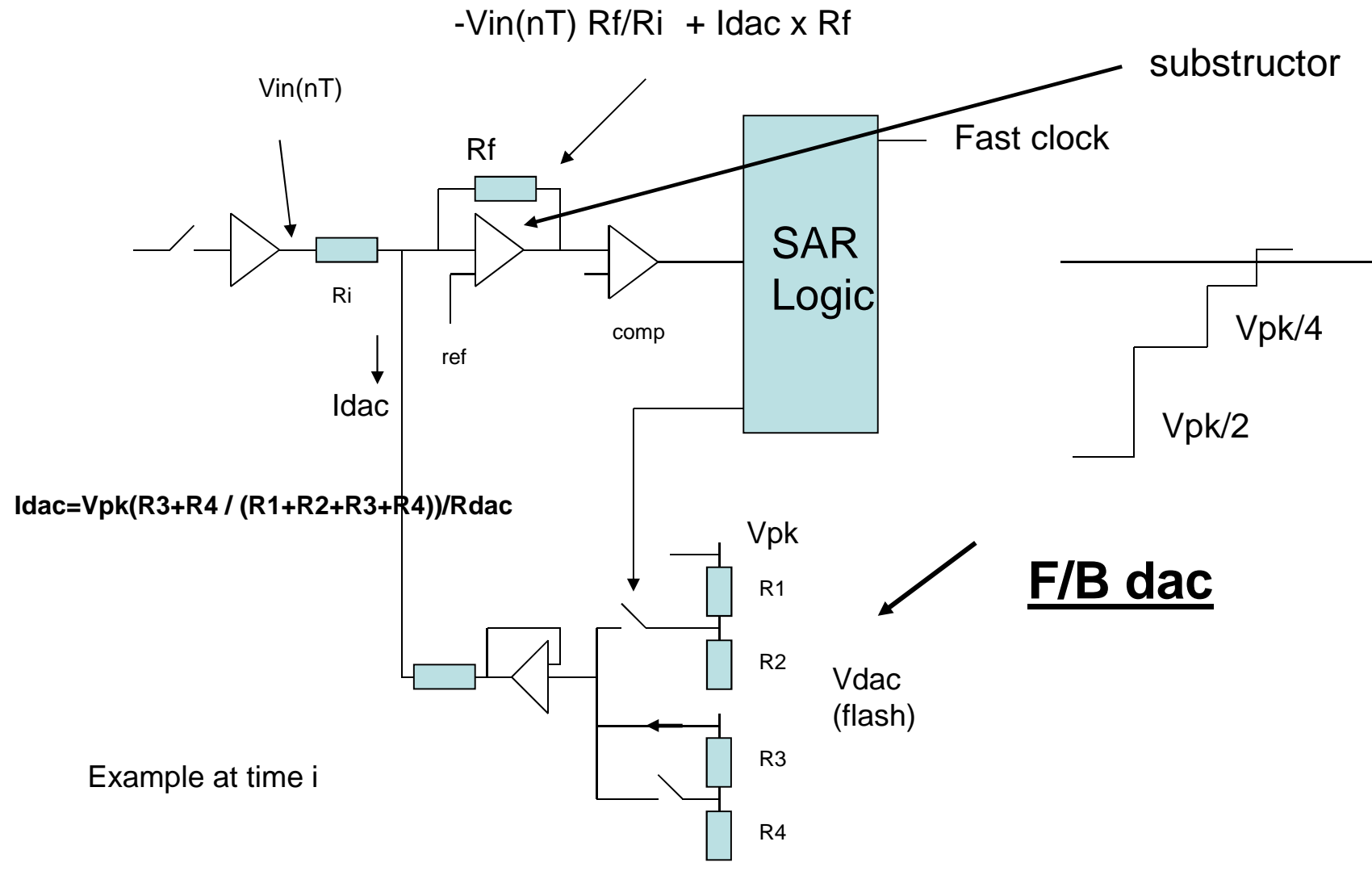
# Example cont, SAR Idac feed back generation



3<sup>rd</sup> step the lin and Idac is compared around the loop n times



## SAR DAC – use another alternative to R-Ladder




Go to DAC lecture pick another type ?

We got transistors they are small

Current is always easy to generate with transistors


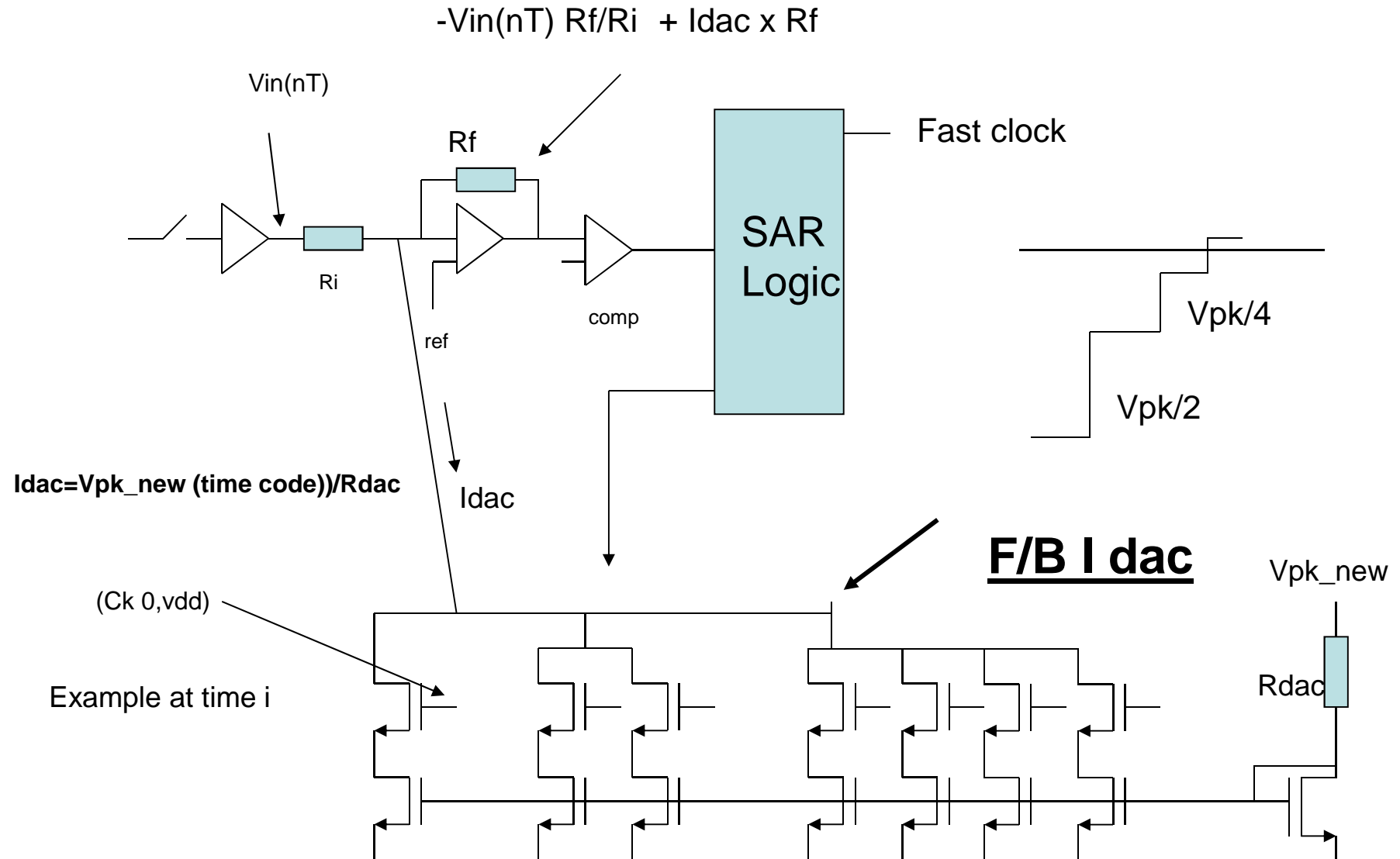
# SAR DAC – another dac – speed and area improvement





Lets look at other DAC in SAR approach.

Speed issues: BW amplifier,  
Subtraction with amplifier  
s/h- or track and hold.  
Area

**Can we do it other way ?**

Lead to a simpler architecture  
No amplifiers !!

**With capacitors we can easily subtract**  
Speed per cycle may be faster



We want to generate


$V_{ref}/2.....$	1 <sup>st</sup> clock cycle
$V_{ref}/2 +/- V_{ref}/4..$	2 <sup>nd</sup> clock cycle
$V_{ref}/2 +/- V_{ref}/4 +/-V_{ref}/8$	3 <sup>rd</sup> clock cycle
.. Etc..., ,	

So lets use capacitor DAC to do this.
 
# Charge distribution SAR DAC operation



Step 1.- clock n=1, reset everything to 0 point – “wasted state” but needed because capacitors plates are held at a “value” for DC





$V_{out} = 0v$  all capacitors plates are shorted to 0  
In reality after  $nR_{on}C/2$  time ( $R_{on} = 1/\mu_{ox}(v_{gs}-v_t)(w/l)$ )
  
# Generate $V_{ref}/2$ to compare



Step 2.- clock  $n=2$ , generate  $v_{ref}/2$  to compare with input



$$V_{out}(2T) = 0 + \frac{1/S0.5C}{(1/S0.5C + 1/S0.5C)} V_{ref}$$


$$V_{out}(2T) = \frac{1/0.5}{(1/0.5 + 1/0.5)} V_{ref}$$

## $V_{out}(2T) = V_{ref}/2$

# Compare to $V_{ref}/2$ and generate $V_{ref}/2 + V_{ref}/4$




still in time = "2"

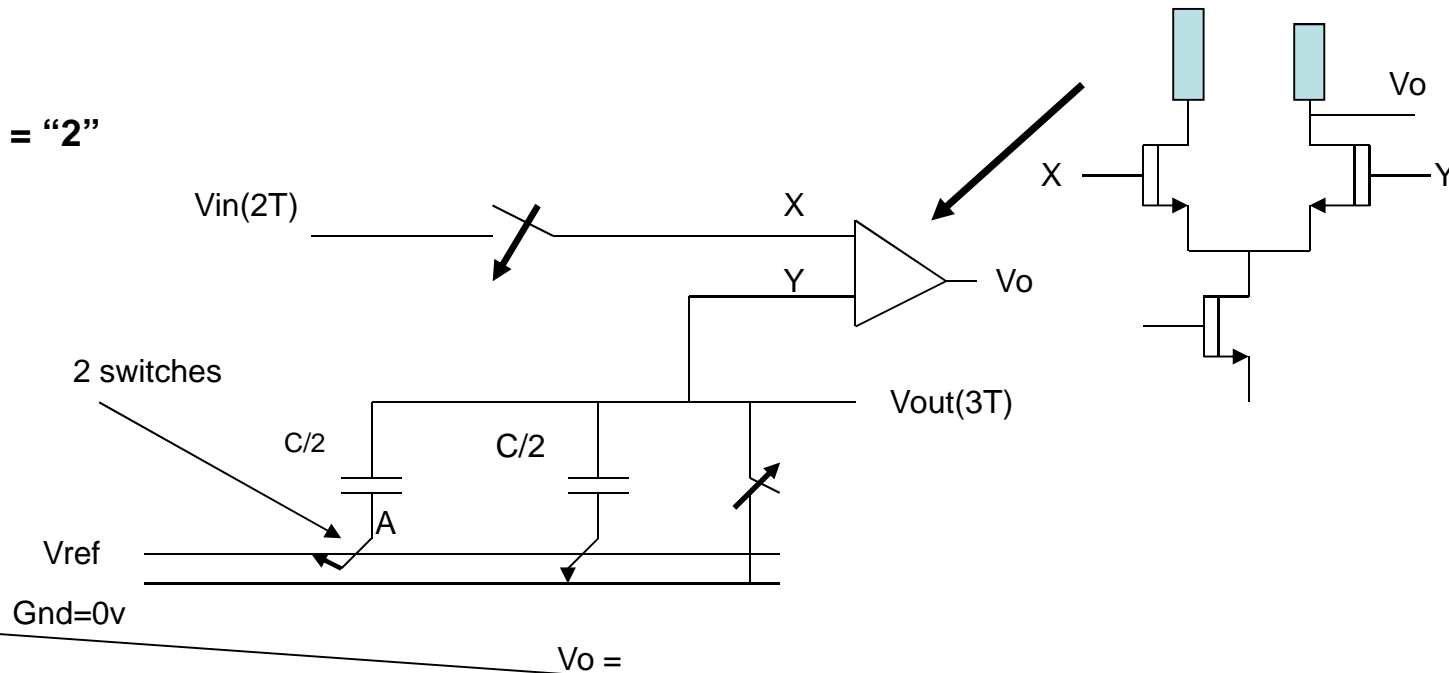


in time = "3" add  $\frac{1}{4} v_{ref}$

Re arrange C to units

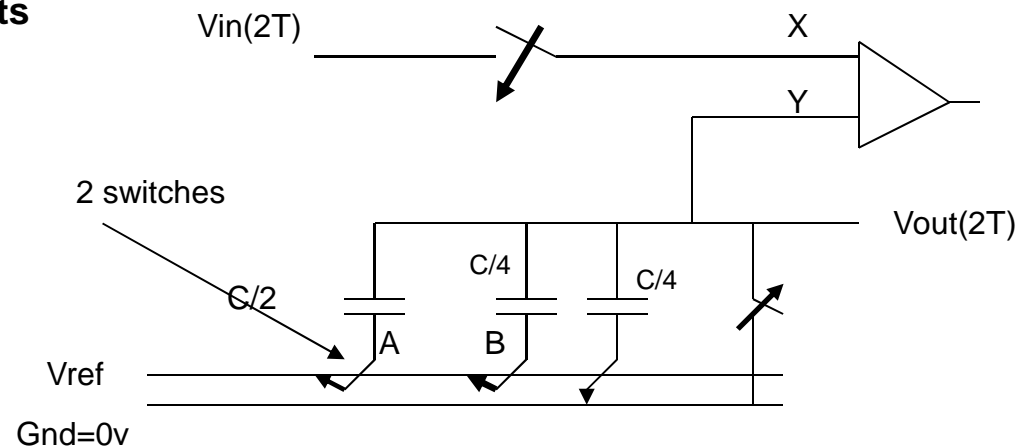
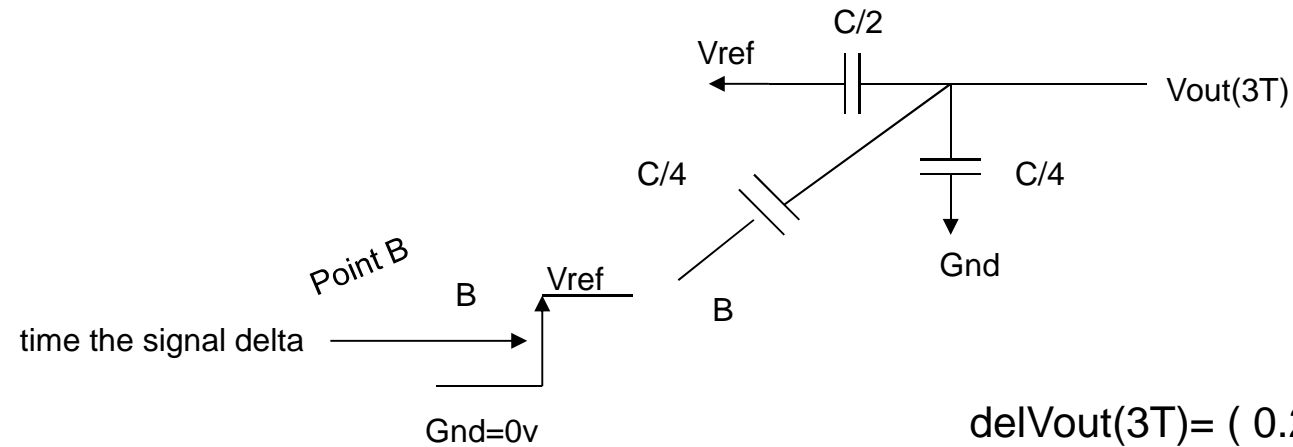
# Time "3" Generate $V_{ref}/2 + V_{ref}/4$



$$\Delta V_{out(3T)} = (0.25C / C) V_{ref}$$

$$\Delta V_{out(3T)} = 1/4 (\text{time the signal delta})$$

$$V_{out(3T)} = V_{ref(2T)} + 1/4 V_{ref}$$


$$\mathbf{V_{out(3T)} = V_{ref}/2 + V_{ref}/4}$$

# Generate the minus $\rightarrow V_{ref}/2 - V_{ref}/4$



in time = "3" let say we want to add  $-1/4 v_{ref}$


2 operations

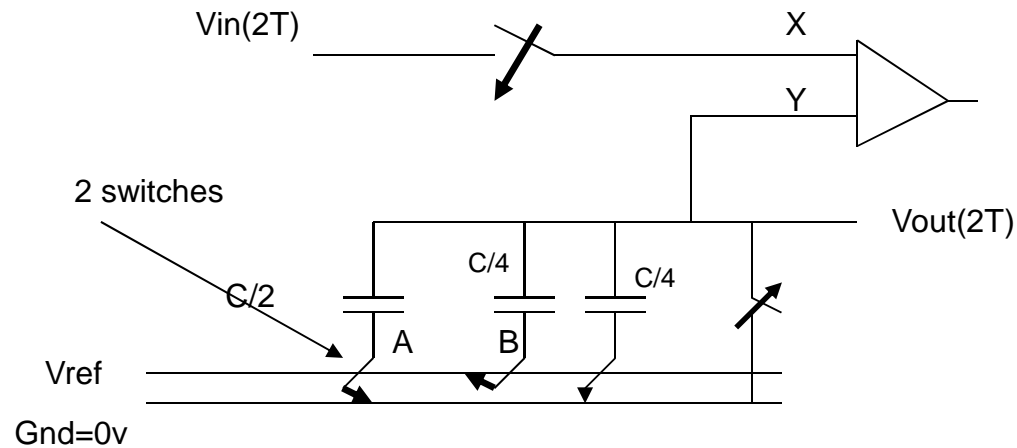

$$\Delta V_{out}(3T) = -0.5 + 0.25$$

$$V_{out}(3T) = V(2T) + -0.5 + 0.25$$

$$\Delta V_{out}(3T) = 1/4 V_{ref}$$

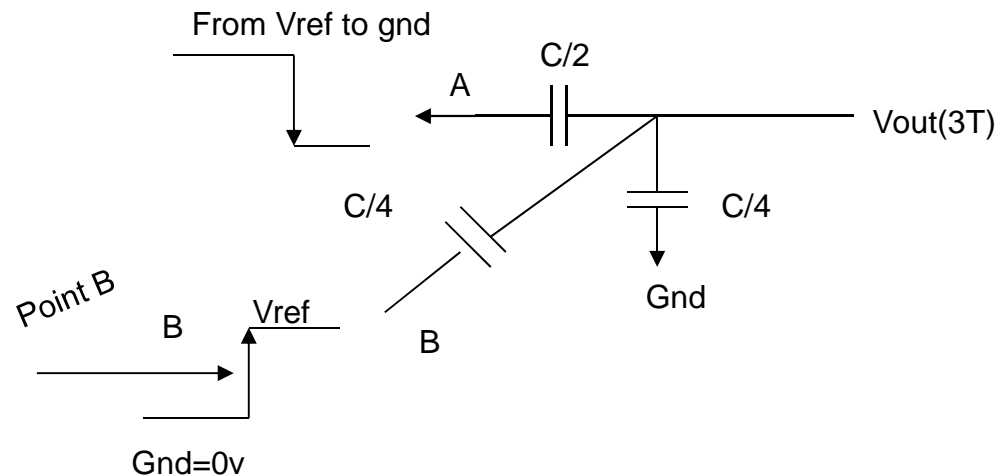





# Generate the minus of the input as well easily



$T=1$

 


$T=2$

 

And on.. And on.. Until the number of bits  $M+1$

# .... Let look at Charges SAR



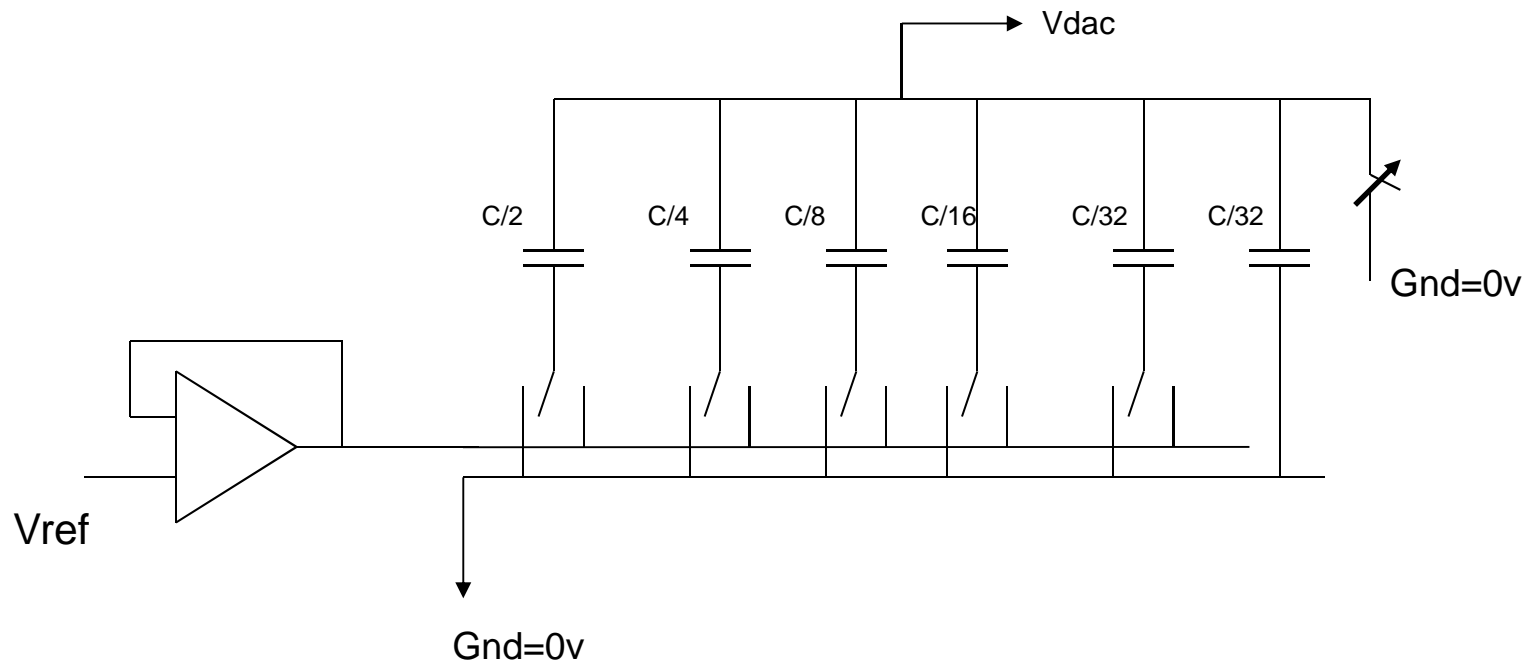


**5bit dac**


   
## Fring. caps-to improve area density..)

$$C = C_o WL \longrightarrow \bar{C} = C_o WL + 2C_{fr} (W + L)$$



Accuracy in silicon is low ~ +/-20%  
Low temperature/V dependency  
Matched well. What about plate parasitic ?

$C_o = 1-2 \text{ ff/}\mu\mu$  if Metal to Metal sandwiched  
With Fringing effect into the picture:



# Example: How low can the cap value be ?

 


Fig. 3. 0.5fF unit capacitor implementation.

## PERFORMANCE COMPARISON.

	[1]	[5]	[6]	This work
Technology	90nm	130nm	65nm	90nm
Power supply	1V	1.2V	1.2V	1V
Power	69 μW	0.92mW	1.13mW	26.3 μW
Sampling rate	10.24MS/s	50MS/s	100MS/s	10.24MS/s
Resolution	8bit	10bit	10bit	8bit
ENOB	7.8bit	8.5bit	9.5bit	7.7bit
FoM	30fJ/step	52fJ/step	15.5fJ/step	12fJ/step


 


Fig. 4. High-speed, low-leakage dynamic comparator.

## A 12fJ/Conversion-Step 8bit 10MS/s Asynchronous SAR ADC for Low Energy Radios

Pieter Harpe, Cui Zhou, Xiaoyan Wang, Guido Dolmans, Harmke de Groot  
 Holst Centre - IMEC, High Tech Campus 31, 5656AE Eindhoven, The Netherlands  
 tel.: +31 40 277 4408, fax: +31 40 274 6400, pieter.harpe@imec-nl.nl

# Fring. capacitors-parasitic errors..

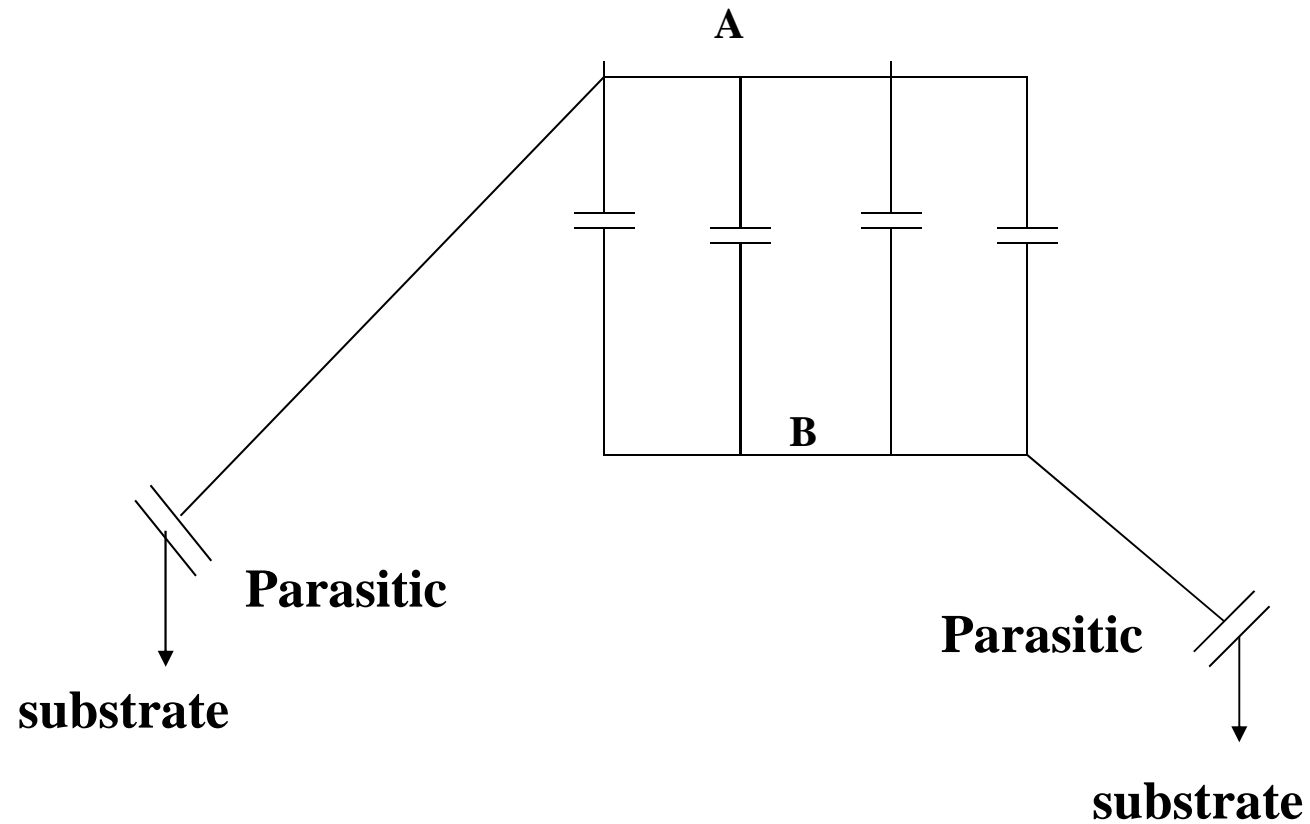

**C parasitic ~0.1-0.05C total! – how to design it out..**



# Silicon transistors as Capacitors


## Capacitors from MOS (transistor) → be careful - watch the plates potential.

In accumulation (off) →  $V_{gs} < V_t$  (n ch)



$$C = C_o WL$$

$C_o \sim 12\text{ff}$  if thin oxide is used (90nm)  
Cap is to the substrate (N well probably)  
In depletion (on) →  $V_{gs} > V_t$


P can be in both

 

NMOS  
Inversion Region

  


$$C = C_{ox}$$

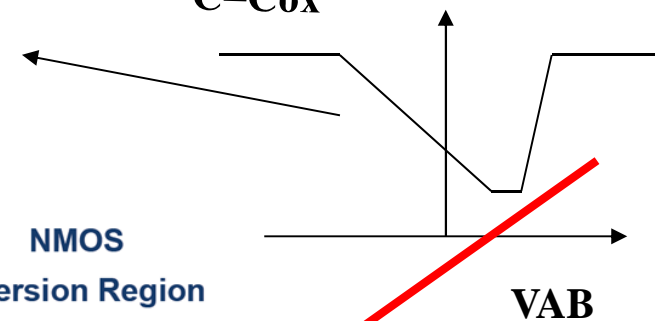

Cap is to the drain sources!  
Next to  $V_t$  – C drops to  $\sim 0.3$  its max value  
It's a voltage dependent capacitor –  
doesn't work good with 0 volt across it (integrator and opamp)

# Silicon transistors as Capacitors

 

The NMOS in an N well capacitor is in accumulation for  $V > 0$  V.

The NMOS capacitor is in inversion for  $V > 0$ .

Giovanni Anelli, CERN

Oh.. We got cap variable.. ? – ah.. Veractor..

# ERRORS IN SAR ADCs



Its an accurate structure

Subtraction using caps

Low/average power: SH, one comparator, DAC, and Logic

8b-200msps is possible

But: Need Accuracy in the DAC.

Comparator offset <  $\sim 0.5$  LSB – Easily calibrated

## ACCURACY : FUNCTION OF DAC (CAPACITORS) MATCHING



# MATCHING



$$C \approx \varepsilon \frac{WL}{t} \longrightarrow \left(\frac{\Delta C}{C}\right)^2 = \left(\frac{\Delta \varepsilon_r}{\varepsilon_r}\right)^2 + \left(\frac{\Delta t_{\text{ox}}}{t_{\text{ox}}}\right)^2 + \left(\frac{\Delta L}{L}\right)^2 + \left(\frac{\Delta W}{W}\right)^2$$

**Once again can correlate to area with good accuracy  
How is it given**

- 1. A\_ΔC/C is based on sigma of (ΔC / C) vs. 1/sqrt(WL)  
typ. number 2fF/micron square**



## To get to the best matched number you need to :

- ❖ Use identical geometries
- ❖ Use large unity capacitance (minimize fringing)
- ❖ Use common centroid arrangement
- ❖ Use dummy capacitors
- ❖ Use shielding
- ❖ Account for the connections' contribution
- ❖ Don't run connections over capacitor
- ❖ Place capacitor in low stress areas
- ❖ Place capacitors far from power devices

## ON BOARD EXAMLE



Find the LSB capacitor size ( and total capacitors)  
for a 12b SAR ADC Given that 10ff unit match to 0.8%. (to 1 sigma)

$$C_{unit} = 10ff, \left(\frac{\Delta C}{C}\right)_{unit} = 0.8\%$$

$$\Delta_{noise} = \sqrt{\frac{\Delta^2}{12} + \{DISTORTIONS\}^2 + \frac{1kT}{C_r}}$$

1pF ~ 64e-6V/sqrtHz

Let give {DISTORTIONS} - 1/3 LSB weight.

$$\left\{\frac{\Delta C}{C}\right\}_{F.scale} = \frac{1}{3} \left[ \frac{1}{2^n - 1} \right] = 0.0081\%$$

LSB can be a lot worst, its scale  
by  $\frac{1}{\sqrt{A}} - \frac{1}{\sqrt{V}}$

$$\left\{\frac{\Delta C}{C}\right\}_{LSB} = [0.0081] \cdot \sqrt{2^n - 1} = 0.518\%$$


$$C_{LSB} = [C_{unit}] \cdot \left[ \frac{0.8}{0.518} \right]^2 = 23.85ff$$

$$C_{TOTAL} = 97.67pF$$

NOT TO INFLUENCY THE CONVERTER. !


$$C_{LSB} = [C_{unit}] \cdot \left[ \frac{\left(\frac{\Delta C}{C}\right)_{F.scale} \sqrt{2^n - 1}}{\left(\frac{\Delta C}{C}\right)_{unit}} \right]^2$$
 
## Example of matching requirement on F. Scale (MSBs)




**2 to the n x 2/3**  
**(2/3 only as example not to give all the error to the linearity)**

# HOW TO BUILD ONE – WHAT TO LOOK FOR

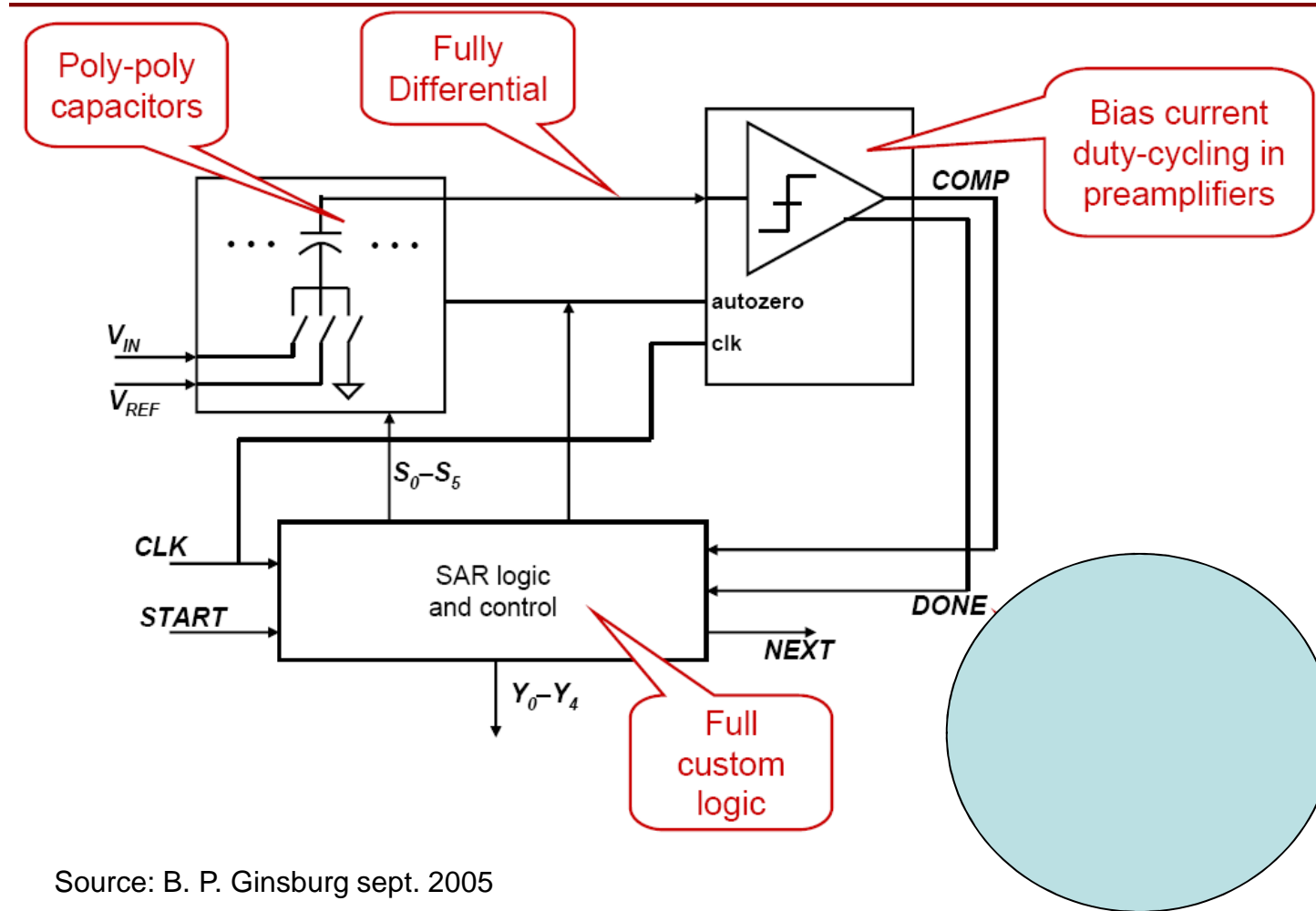

Source: B. P. Ginsburg sept. 2005

# Design Examples:

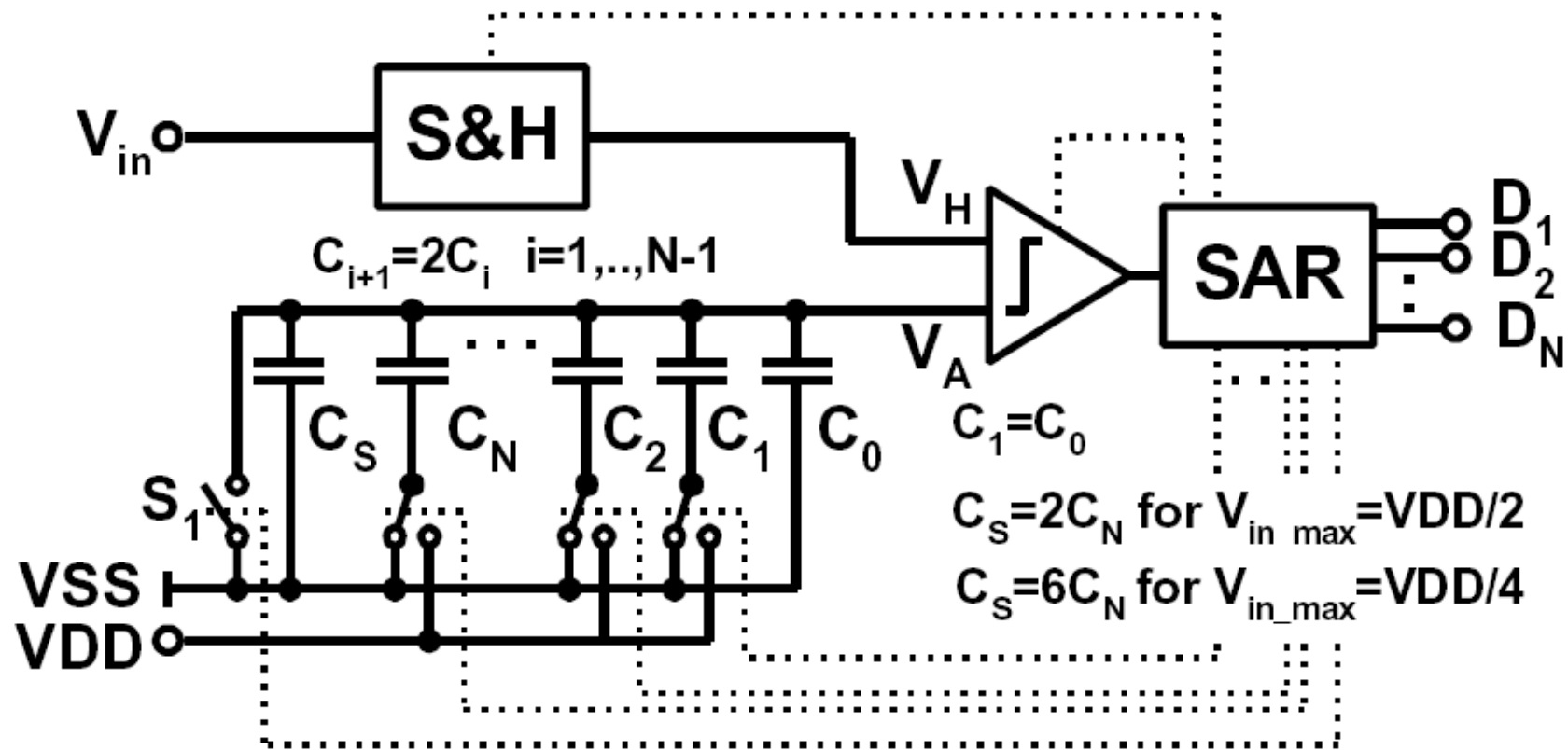

## Key: Word on the references




References issues:
 
### **REFERENCE HOLDING BREF IS HARD TO DO:**

During switching phase references  
has to settle every clock (fast) They are op amp  
driven therefore make the design almost as op-amp based

Also the comparator must settle every cycle. (faster)



## Summary- C or R dac



Most time absolute value can move = $\pm 15\%$  to  $\pm 20\%$   
and does not significantly matter but ratio's do

However, the bigger the area the better the matching  
Typical values 30ff can match 3-sigma to better  $\sim 0.5\%$   
Matching is area dependent generally by the root of (W x L)

In SAR there is contradiction large is good for matching however  
speed is degraded a lot R switch x C and its multiplied N bit for a  
complete cycle.





## POWER/Analog componets

Without amplifiers power is set by S/H, References, 1 comparator, and digital blocks+clocks

Generally for lower number of bits – logic may be significant Area. For many bits analog set the power waist.

Logic running multiple times for each conversion and capacitor size (forcing a large drive current)

Power waist : S/H + Comparator + Refes+switching/logic

**Good:**

**Lowest possible power- FOM**

**Fewer analog elements,**

**T/H or S/H drive low capacitance**

# SAR- Key Points



The Feed Back ADC (SAR) offers significant hardware savings compared to flash ADCs because the coarse quantizer (comparator) resolution  $m$  can be much smaller than the converter resolution.  $N$

However, it suffers from drawbacks making it not suitable for many applications because:  
It requires  $p = N/m$  passes to generate  $N$  bit output words limiting the throughput  
It requires  $N$ ; bit accurate DAC

It requires faster settling elements

but No need amplifiers !

**So if speed is a problem should we combine SARs in time ??**



# End Lecture 9

[www.gigalogchip.com](http://www.gigalogchip.com)