

Welcome to
0510.7720.01 Winter semester 2021
Mixed Signal Electronic Circuits
Instructor: Dr. M. Moyal

Lecture 10 at 18:10 26/05/2021

- Over Sampling ADCs:**
 - Sigma Delta - Loops and Architectures**


- SNR Calculations**

- ❑ Sigma Delta – System Non Nyquist Converters
- ❑ Why Over sample
- ❑ Basic Loops, Z transform
- ❑ Noise Transfer
- ❑ Multi-Loops
- ❑ Multi Bit Multi Loops


ADC Architectures



Parallel ADC's (SARs/Flash)

 

ADC Architectures

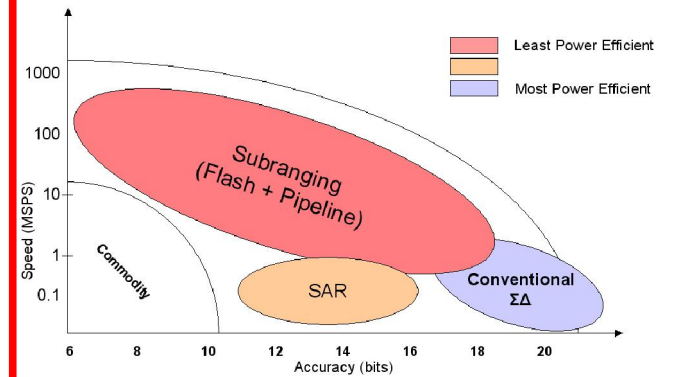

Lecture 9 ADC's 'before 2002'

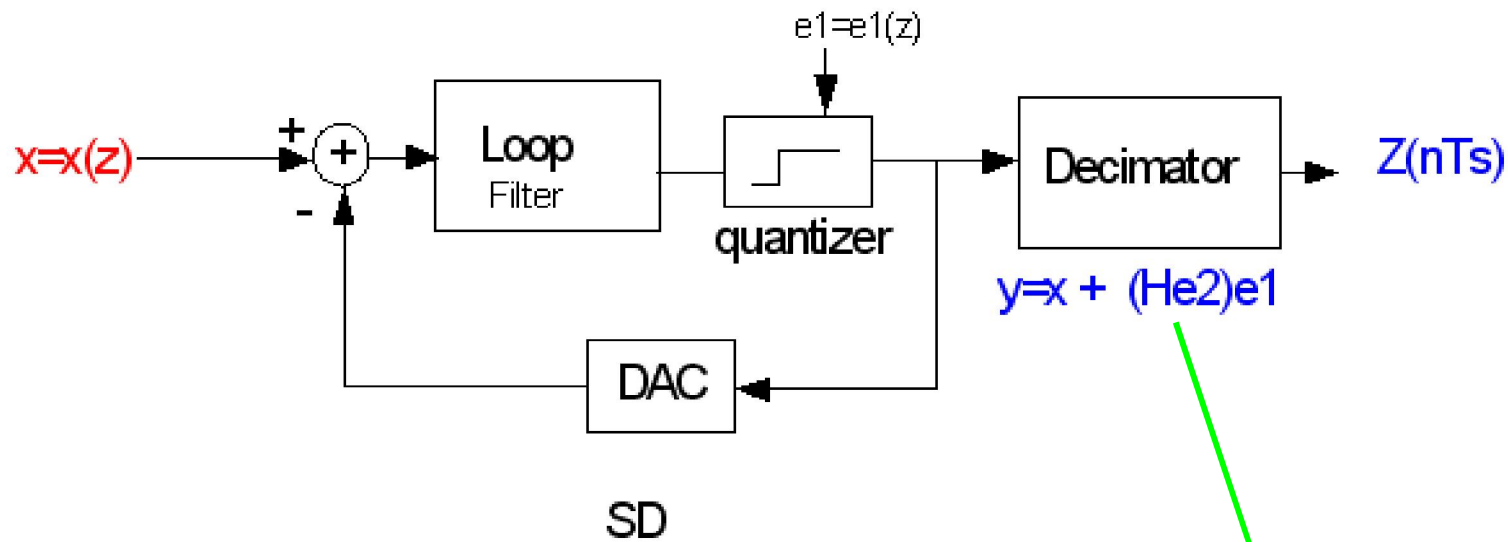



Figure out H_e2

Main Old Reason – Linearity is Infinite!

Why ?

Quantization Noise

Nyquist vs Over-sampling Operation

 

Σ -Delta architectures use oversampling; Normally, pipeline architectures do not

Trading Digitizing Rate for Bits to Get Equal Quantization Noise in a Fixed Band

$$SNR \text{ Increase} \gg f\left(10 \log \frac{f_{s1}}{f_{s2}}\right)$$

$$2x \gg 10 \log 2 = 3dB$$

When the noise is shaped equally (quantization noise)

2 x f_s – Half noise power increase in SNR by 3dB

4 x f_s – Same as 1 bit performance increase

N x f_s – $10\log(n)$ increase in performance

Example:

Use 8 bit converter over sample by 16 get 10 bit SNR


But is it the best we can do?

Poor return on investment

(clock frequency increased - if noise spread equally)

Can we shape the noise in band ?

Can we shape the noise ?

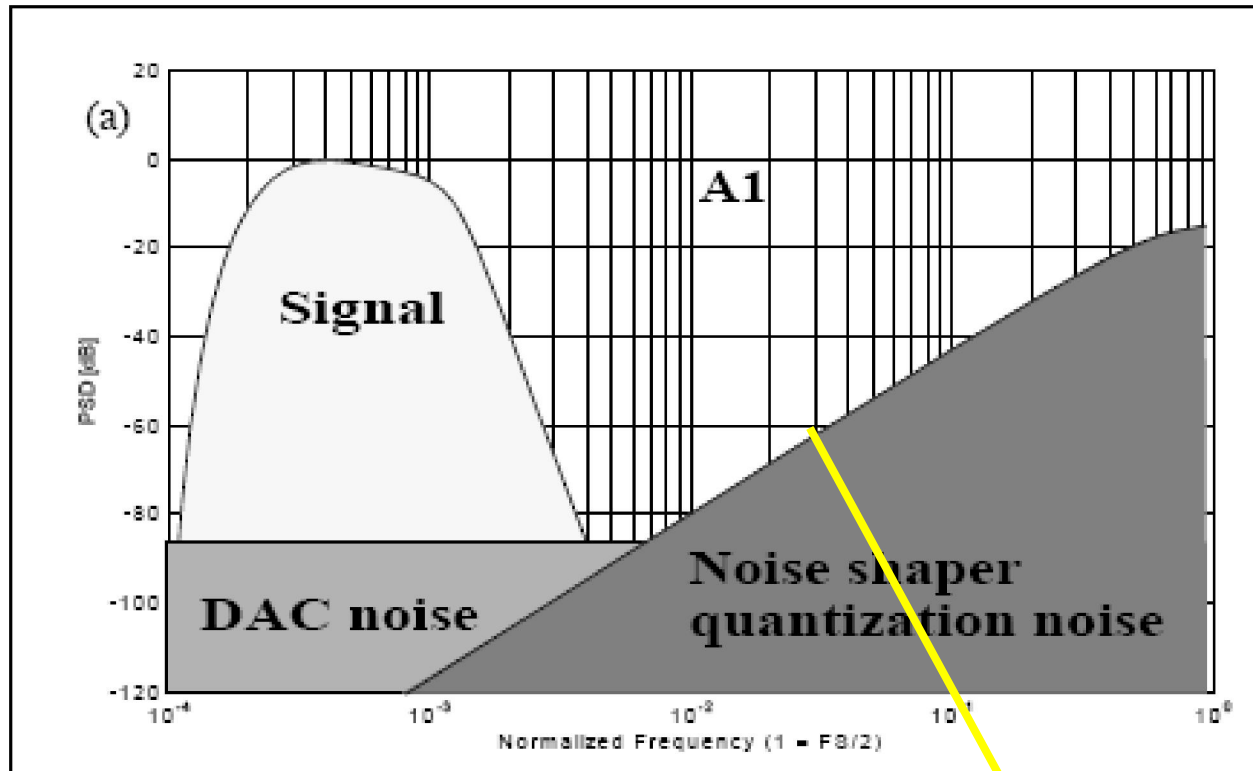


*DAC output with shaped noise
(same for adc shaped digital noise)*

We may need analog filter..



Quantization Noise

The benefits of Noise Shaping

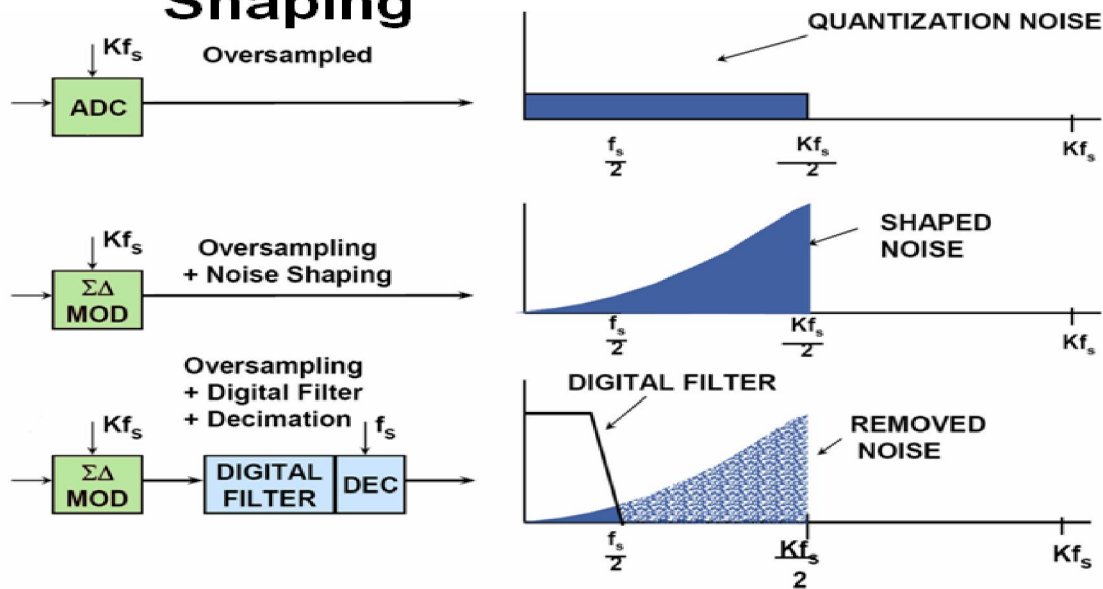


We will need digital filter..

Additional why's...


Sigma Delta Converter “love digital noise”..

- Anti-alias filter relaxed
- No S/H – Reduced analog block requirements
- Easy re-design for new technology
- Low Voltage design
- Low power- Good FOM
- Fewer DAC bits

 ***DONT FORGET WE CAN GET INFINITE LINEARITY !
But... Need much faster sampling clock***




Basic Loop – How Does it Work

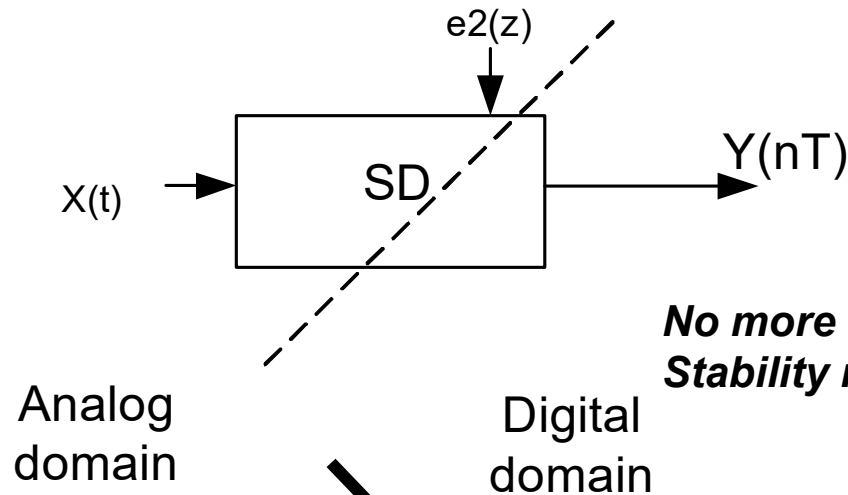

**No more open loop:
Stability must be watched for Clocked at 2 places at least.**


Place the Quantizer with filtering inside the ADC loop. What is a good loop filter? why?

BASIC SD LOOP

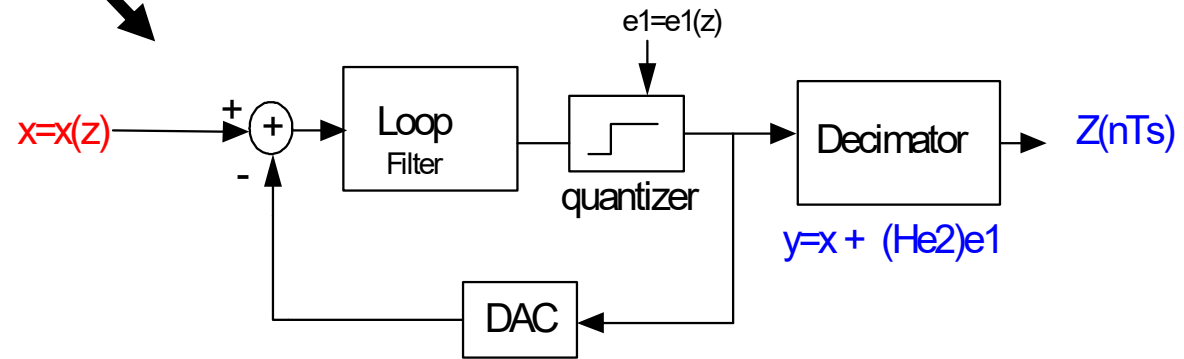

SD


Example Simulation

 

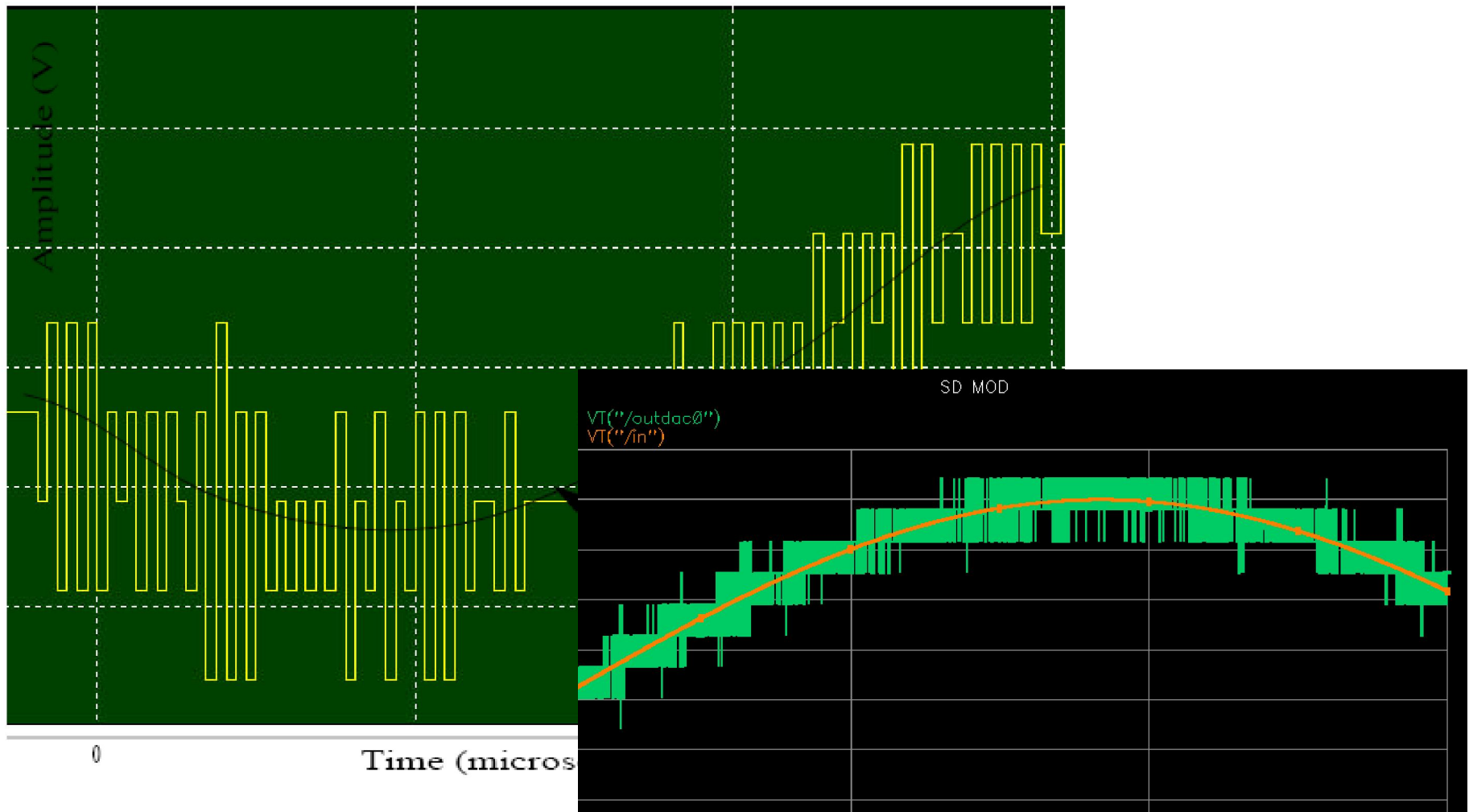Example 2 - Multi bit SD – ADC




Time domain multi bit over sample converter
(converting digital bits to levels..)



NEXT :


- Analyze SD Structures, Review few Loops and..**

- How to Calculate Loop Quality: SNR**

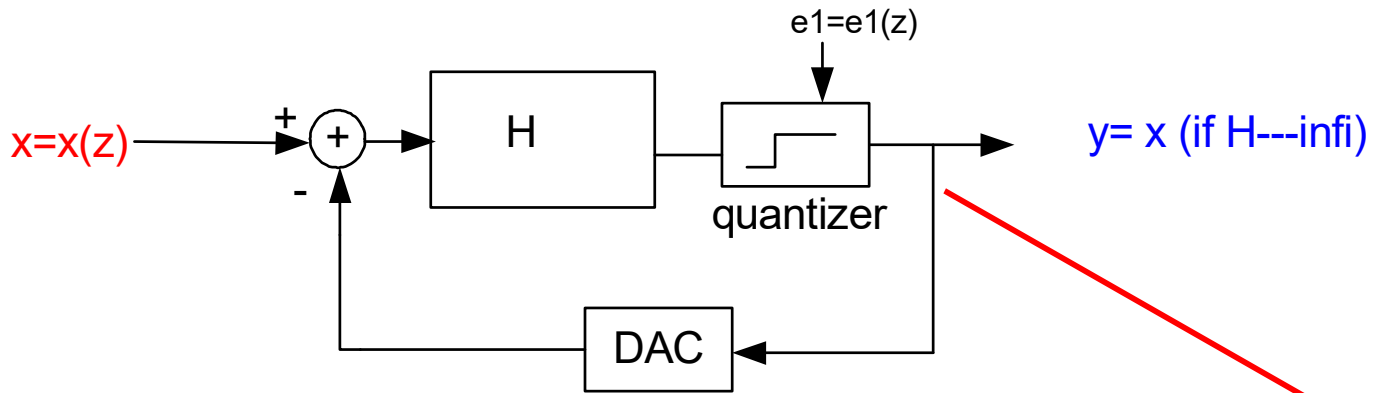

SD


Signal TF

 

Can be 1 comparator (covered Lecture 8)
 Can be set of comparators- Flash ADCs

$$V_{out}/V_{in} = H / 1 + H$$

if H (v. large) goes to infinite T.F = 1

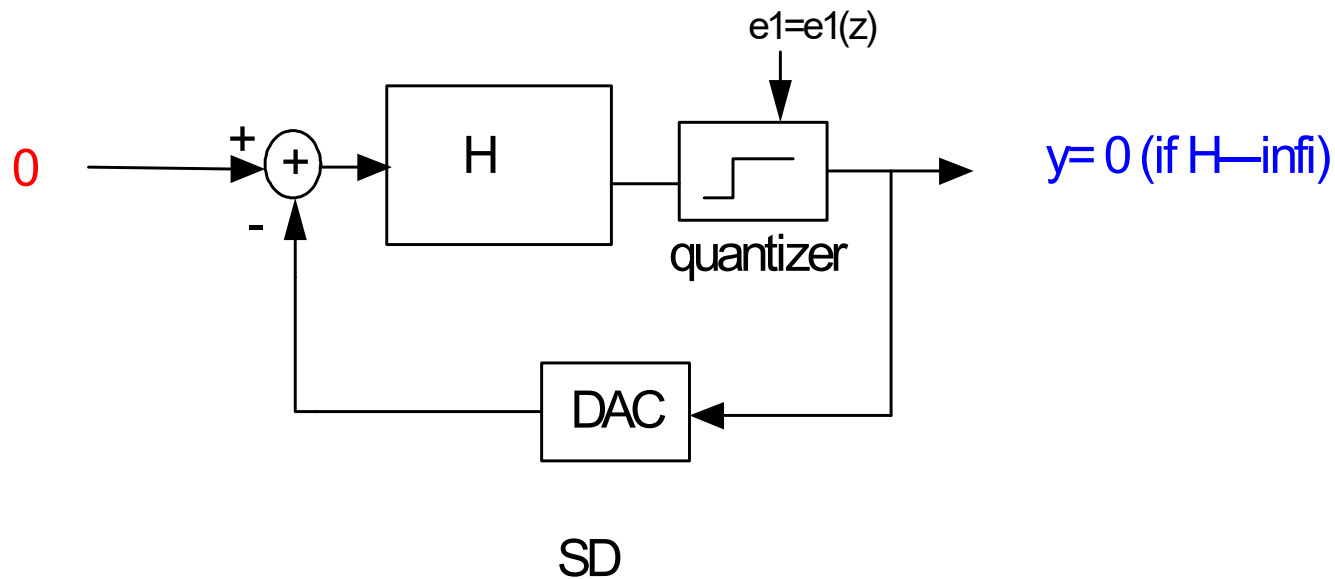

Noise (quant) TF

$$V_{out}/V_{in} = 1 / 1 + H$$

- ❑ Let's assume its good to use an integrator in the loop
- ❑ SD can be implemented using time continuous filters (integrators) but also using switch capacitor- discrete time..
- ❑ For further study of SD, I will switch back and force from time domain to Discrete domain- some calculations are easier to explain in one domain or the other.


So lets switch no analog domain..

**Look first at analog sigma delta
simple 1 loop**


CT- $\Sigma\Delta$ ADC

Simple filter here

Block diagram

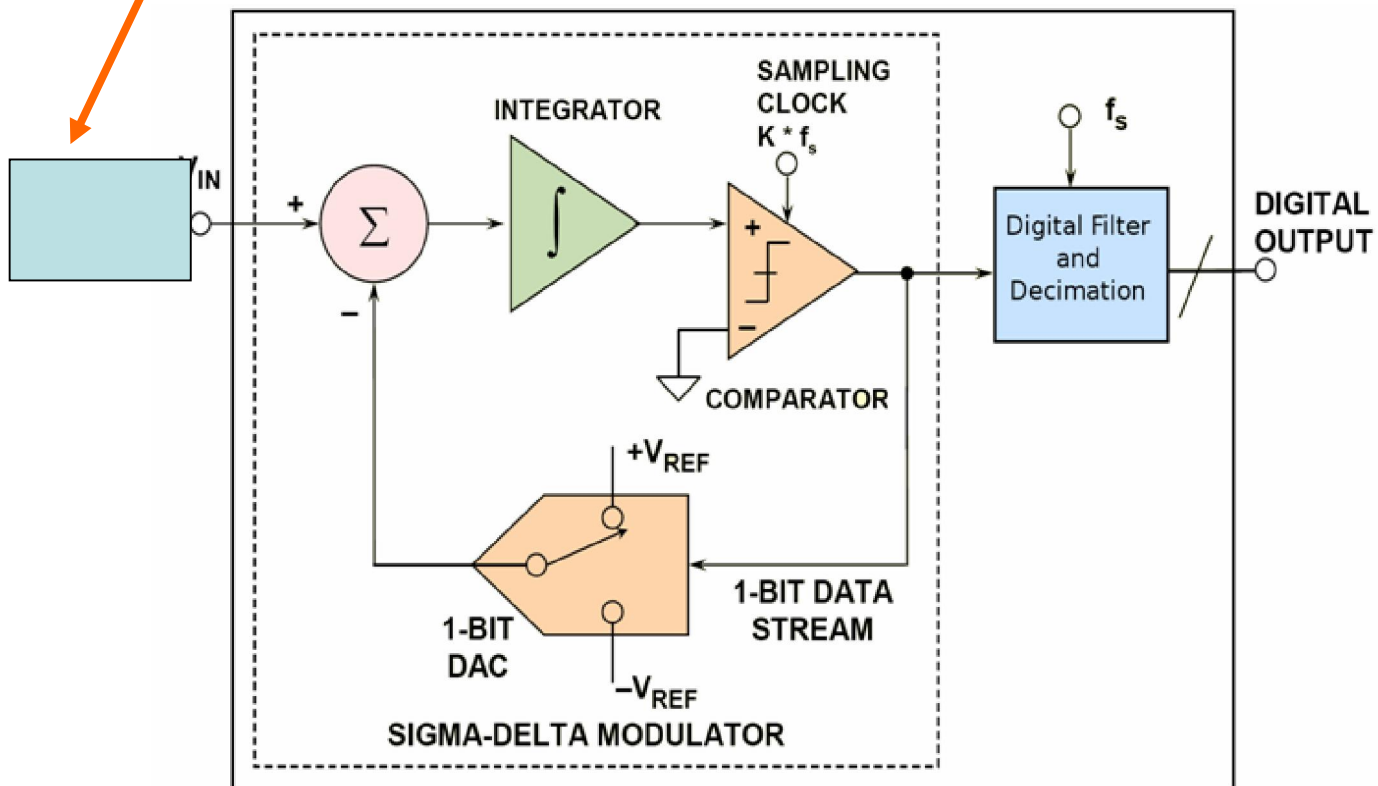

SD Analog Model for TF

 


Signal Transfer Function:
(when $N(s) = 0$)

$$Y(s) = [X(s) - Y(s)] \frac{1}{s}$$

$$\frac{Y(s)}{X(s)} = \frac{\frac{1}{s}}{1 + \frac{1}{s}} = \frac{1}{s + 1} \quad \text{: lowpass filter}$$

 
Integrator in open loop is LPF
In closed loop



Noise Transfer Function:
(when $X(s) = 0$)

$$Y(s) = -Y(s) \frac{1}{s} + N(s)$$
 
$$\frac{Y(s)}{N(s)} = \frac{1}{1 + \frac{1}{s}} = \frac{s}{s + 1} \quad \text{: highpass filter}$$




But the story is a bit more complicated:
Loop delay, DAC TF is not constant

Noise is H passed shaped



SD Continuous Analog Blocks – implementation



Detail design example in lect11

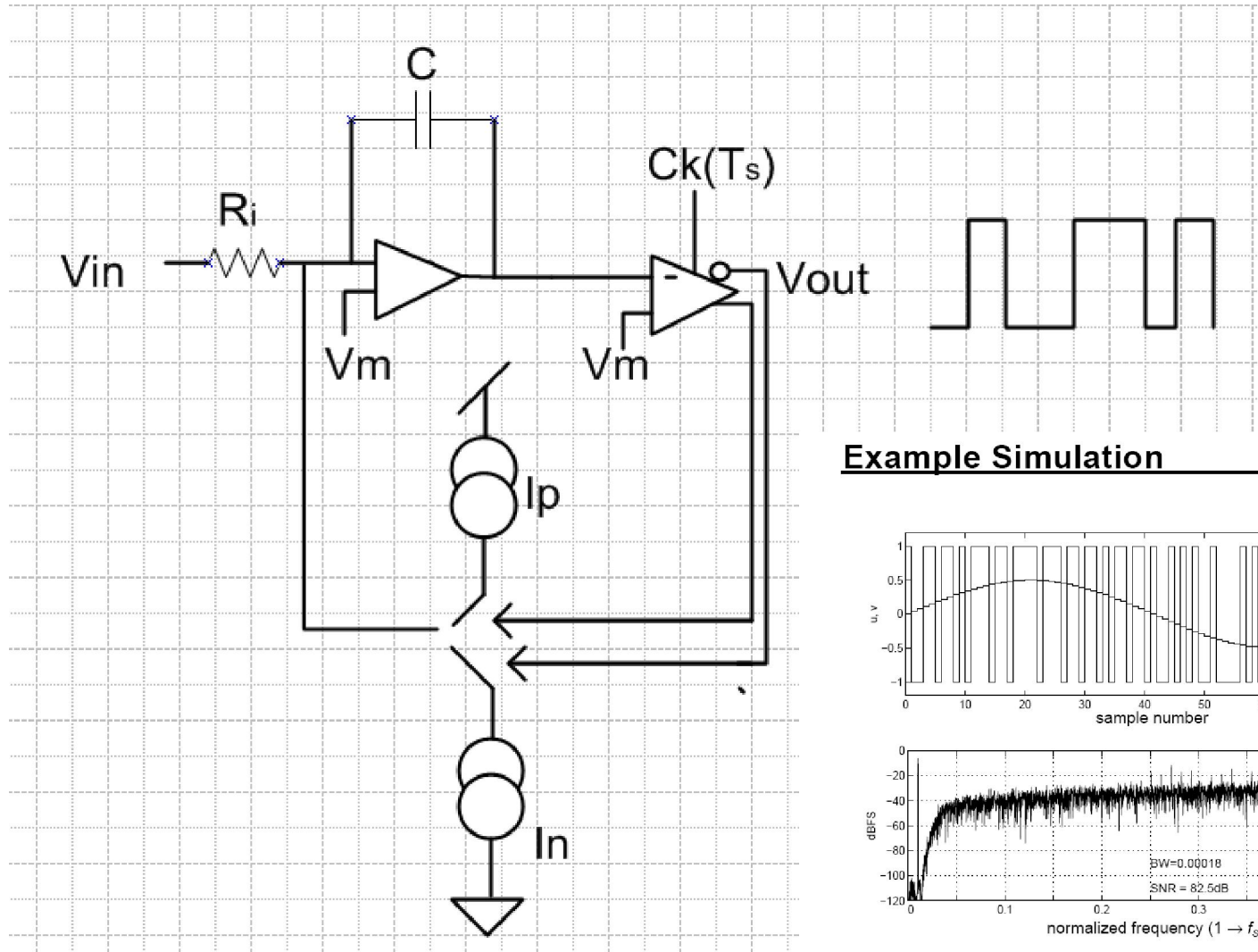

Example Simulation

  


SD - Noise analysis vs. Loop order


Now lets switch to discrete time...

Summary >> Z Transformation

1) Take $f(t)$

 

2) Create $f^*(t)$

 

$$f^*(t) = f(t) \sum_{k=0}^{\infty} \delta(t - kT)$$

3) Take Laplace Transform of

$$f^*(t) = F^*(s) = \sum_{k=0}^{\infty} f(kT) e^{-kT}$$

4) Replace s by $\frac{1}{T} \ln(Z)$

$$\text{If } Z \triangleq e^{Ts} = e^{j\omega T} \gg F(Z) = Z[f(f)] \triangleq F^*(s) \int_{s=\frac{1}{T} \ln Z} = \sum_{k=0}^{\infty} f(kT) Z^{-k}$$

Transfer to distinct values - $X(nT)$

Differences eq. can be easily described:

$$Y(n) = X(n-1) + Y(n-1)$$

Quick Overview at Z Domain



$f(t)$	$F(s)$	$F(z)$
$\delta(t)$	1	1
$u(t)$	$\frac{1}{s}$	$\frac{1}{1-z^{-1}}$
t	$\frac{1}{s^2}$	$T \frac{z}{(z-1)^2}$
t^2	$\frac{2}{s^3}$	$T \frac{z(z+1)}{(z-1)^3}$
e^{-at}	$\frac{1}{s+a}$	$\frac{z}{z-e^{-aT}}$
$1 - e^{at}$	$\frac{a}{s(s+a)}$	$\frac{z(1-e^{aT})}{(z-1)(z-e^{aT})}$
a^t	$\frac{1}{s-\ln a}$	$\frac{z}{z-a}$

$$s = \frac{1}{T} \ln Z$$

← **Integrator:
Most Important for SD**

$$X(z) \rightarrow Z^{-m} \rightarrow Y(z) = Z^{-m} \times X(z)$$

$$X(k) \xrightarrow{Z} X(z)$$

$$X(k-m) \xrightarrow{Z} Z^{-m} \times X(z)$$

$$a^k X(k) \xrightarrow{Z} X\left(\frac{z}{a}\right)$$

$$k X(k) \xrightarrow{Z} -Z \frac{dx(z)}{dz} \{k < 0; X(k) \neq 0\}$$

From Z to Difference Equations

$$\begin{array}{l}
 X(z) \rightarrow \boxed{z^{-m}} \rightarrow Y(z) = z^{-m} \cdot X(z) \\
 x[k] \xrightarrow{z} X(z) \\
 x[k+m] \xrightarrow{z} z^{-m} \cdot X(z)
 \end{array}$$

Linearity Property

Given $x[k]$, $y[k]$, which are all zero for $k < 0$.

Then:

$$\begin{array}{l}
 x[k] \xrightarrow{z} X(z) \\
 y[k] \xrightarrow{z} Y(z)
 \end{array}$$

and:

$$\boxed{a \cdot x[k] + b \cdot y[k] \xrightarrow{z} a \cdot X(z) + b \cdot Y(z)}$$

"Multiplication by a^k " Property.

Given $x[k]$ where $x[k] = 0$ for $k < 0$ and $a = \text{constant}$

Then:

$$\boxed{a^k \cdot x[k] \xrightarrow{z} X\left(\frac{z}{a}\right)} \quad \dots \text{ corresponds to scaling by 'a' in the z-domain.}$$


"Multiplication with k " Property

Given $x[k] = 0$ for $k < 0$

Then:

$$\boxed{k \cdot x[k] \xrightarrow{z} -z \cdot \frac{dX(z)}{dz}}$$

From "z" to difference equations

 

Discrete time integrator

$$H = \frac{Z^{-1}}{1 - Z^{-1}}$$

Differences eq:


$$Y(n) = X(n-1) + Y(n-1)$$

**Now one more time switch to analog but
compare to discrete—**

**But I want to look also at time domain not
only s domain...**

Lets look at sd integrator

 Example: Z domain Vs. Time domain integrator ?





$$V_o = -\frac{1}{RC_2} \int_{-\infty}^t V_{in}(t) dt$$

$$H(j\omega) = -\frac{1}{RC_2} \left(\frac{1}{j\omega} \right)$$

$$A_0 = \infty, \quad BW = \infty, \quad V_{off} = 0$$
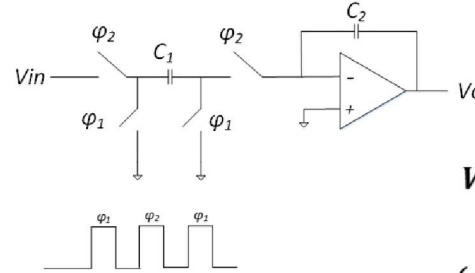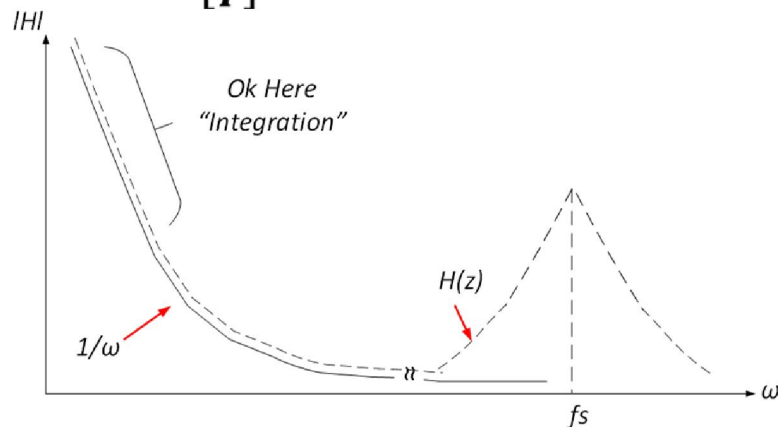
$$R \approx \left[\frac{C}{T} \right]^{-1}, \quad C = C_2$$



Gain

$$V_o = V_o(n-1) + \left(-\frac{C_1}{C_2} \right) V_{in}(n)$$

$$(1 - Z^{-1})V_o = -\left(\frac{C_1}{C_2} \right) V_{in}(n)$$

$$H(z) = \frac{-C_1/C_2}{1 - Z^{-1}}$$

$$Z^{-1} = e^{-j\omega t}$$

$$\text{If } \omega t \ll 1, \quad e^x \sim (1 + x + \frac{x^2}{2} + \dots)$$

$$H(j\omega) \cong \frac{-C_1/C_2}{1 - 1 - j\omega t + \omega^2 t^2} =$$

$$= -\frac{C_1/C_2}{1} \times \frac{1}{j\omega - \frac{\omega^2 t}{2}} =$$

$\underbrace{\hspace{1.5cm}}_{\frac{1}{RC_2}} \quad \underbrace{\hspace{1.5cm}}_{\text{Integrator}}$


"0" Intersect is process independent → Matching

If $\omega t \ll \ll 1$, all $\omega^2 \dots = 0$

$1/j\omega$ exactly ωt


**Next lets build the switch C discrete SD and calculate
SNR**

 Build the SD: Lets put the Integrator in the Loop/s




$$H = Z^{-1} / 1 - Z^{-1}$$

Discrete time integrator

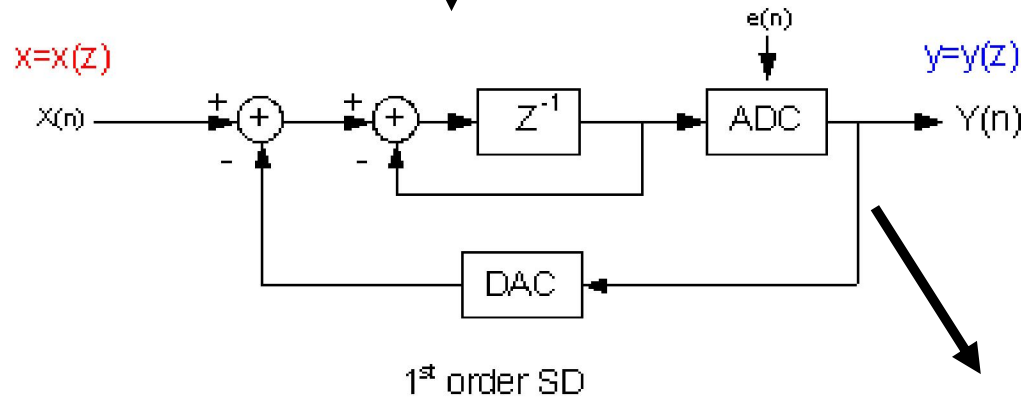


1st order SD

 

1st order SD model

Build the SD: TF Calculations 1 Loop

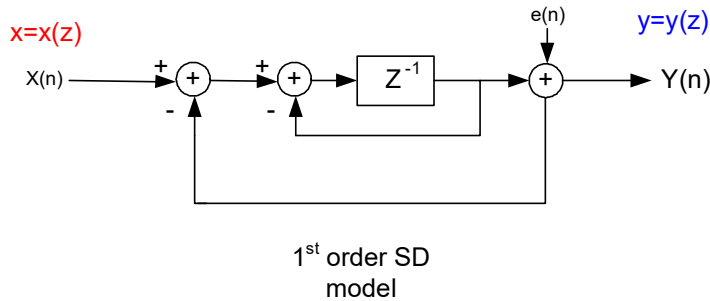


$$Y(z) = z^{-1}X(z) + (1 - z^{-1})E(z)$$

$$Y(z) = H_x(z)X(z) + H_e(z)E(z)$$

with $H_x(z) = z^{-1}$ and $H_e(z) = (1 - z^{-1})$

First-Order Modulator

 

- Noise Transfer Function (NTF):

$$\rightarrow H(z) = \frac{V(z)}{E(z)} = \frac{1}{1 - L(z)} = \frac{1}{1 + \left(\frac{z^{-1}}{1 - z^{-1}}\right)} = 1 - z^{-1}$$

- Signal Transfer Function (STF):

$$\rightarrow (z) = \frac{V(z)}{U(z)} = \frac{\left(\frac{z^{-1}}{1 - z^{-1}}\right)}{1 + \left(\frac{z^{-1}}{1 - z^{-1}}\right)} = z^{-1}$$




Same way

in discrete time domain (n)

$$y[n] = x[n - 1] + e[n] - e[n - 1]$$

output is delayed input and High passed the error e.

Build the SD: 2 Loops

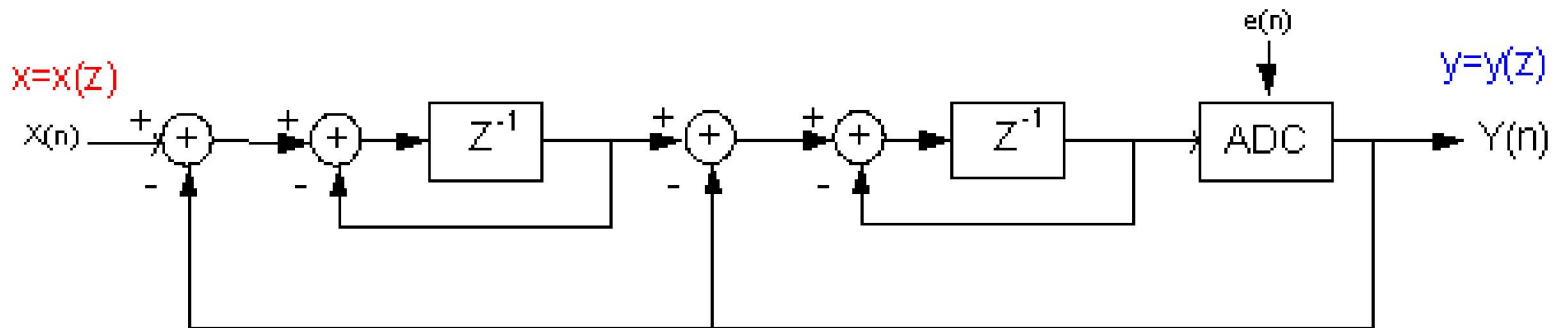 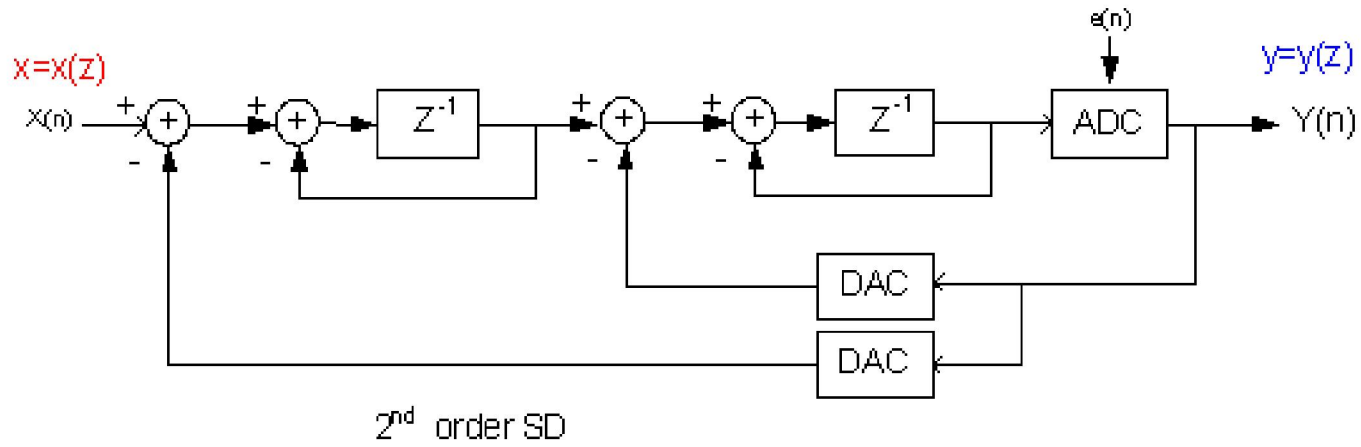

HOW TO CALCULATE LOOP SNR

$$Y(z) = z^{-1}X(z) + (1 - z^{-1})E(z)$$

$$Y(z) = H_x(z)X(z) + H_e(z)E(z)$$

with $H_x(z) = z^{-1}$ and $H_e(z) = (1 - z^{-1})$

Another look at 1 – Z-1 (high pass noise filter)



$$NTF(z) = 1 - z^{-1} \quad (5.17)$$

For *DC* values, the noise transfer function is zero, thereby exactly producing $X(z)$. The shaping function, $1 - z^{-1}$, is analyzed using the transformation from the z domain to the s domain given by: $Z = e^{sT_s} = e^{j\omega T_s}$, where T_s is the sampling rate. The magnitude of the shaping function on $e(z)$ is written as $|1 - z^{-1}|$, and is calculated as

$$: \left| 1 - e^{-j\omega T_s} \right| = \sqrt{[1 - \cos(\omega T_s) + j \sin(\omega T_s)][1 - \cos(\omega T_s) - j \sin(\omega T_s)]} \quad (5.18)$$


Combining the geometric terms of Eq. (5.18) yields,

$$|NTF(f)| = \sqrt{2 - 2 \cos(2\pi f T_s)} \quad (5.19)$$

For a first order noise shaper, the noise power level improvement between any two frequencies, f and $2f$ is given by squaring and integrating Eq. (5.19) from f to $2f$

$$\int_f^{2f} NTF(f)^2 df = 2 - \frac{2 \sin(2\pi T_s)}{2\pi T_s} = 8.8 \text{ dB/octave} \quad (5.20)$$

 Uniform Distribution of Noise- no integrator--- old case..from last lectures..



$$\sigma_e^2 = \frac{\Delta^2}{12} = \frac{1}{12} \left(\frac{2V}{2^N - 1} \right)^2 \approx \frac{1}{12} \left(\frac{2V}{2^N} \right)^2$$

$$SNR = 10 \log \left(\frac{\sigma_x^2}{\sigma_e^2} \right)$$

The noise density power spectra density is


$$N(f) = \frac{\Delta^2}{12} * \frac{1}{fs}$$

$$\sigma_{ey}^2 = \int_{-fb}^{fb} P_{ey}(f) df = 2 \int_0^{fb} P_{ey}(f) df = \int_0^{fb} \frac{2\sigma_e^2}{fs} df = \sigma_e^2 \left(\frac{2fb}{fs} \right)$$

$M = \frac{fs}{2fb}$ is called the OverSampling Ratio (OSR) ←

noise improvements: 3 dB/ octave

 SNR Calculations for 1st order SD with Integrator in the loop



1st order SD model

$$Y(z) = z^{-1}X(z) + (1 - z^{-1})E(z)$$

$$Y(z) = H_x(z)X(z) + H_e(z)E(z)$$

with $H_x(z) = z^{-1}$ and $H_e(z) = (1 - z^{-1})$

SNR calculations $Z = \exp(ST)$
Look only at the magnitude

$$\sigma_{ey}^2 = \int_{-fb}^{fb} P_{ey}(f) df = 2 \int_0^{fb} P_{ey}(f) df = \int_0^{fb} P_e(f) \cdot |H_e(f)|^2 df = \int_0^{fb} \frac{\sigma_e^2}{fs} |1 - e^{-j\omega T}|^2 df$$

$$\sigma_{ey}^2 = \sigma_e^2 \frac{\pi^2}{3} \left(\frac{2fb}{fs} \right)^3$$

Cont: SNR for 1st order SD with Integrator in the loop





$$SNR = 10 \log(\sigma_x^2) - 10 \log(\sigma_e^2) - 10 \log\left(\frac{\pi^2}{3}\right) + 9.03r$$

~9db/ octave : doubling the sampling frequency reference to twice the maximum signal BW.

Remember DAC and ADC in the loop makes the delta LSB noise $6.02 \times$ number of bits

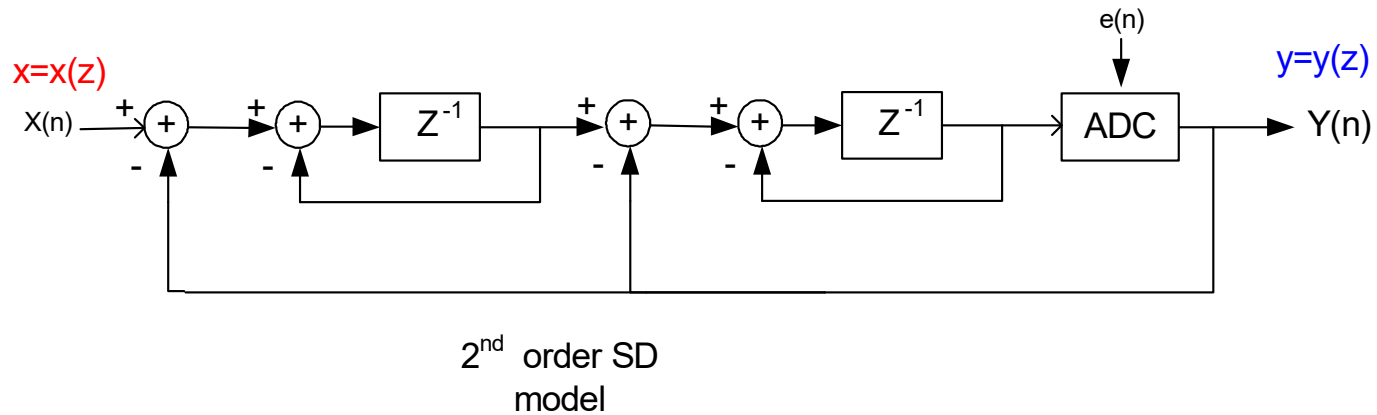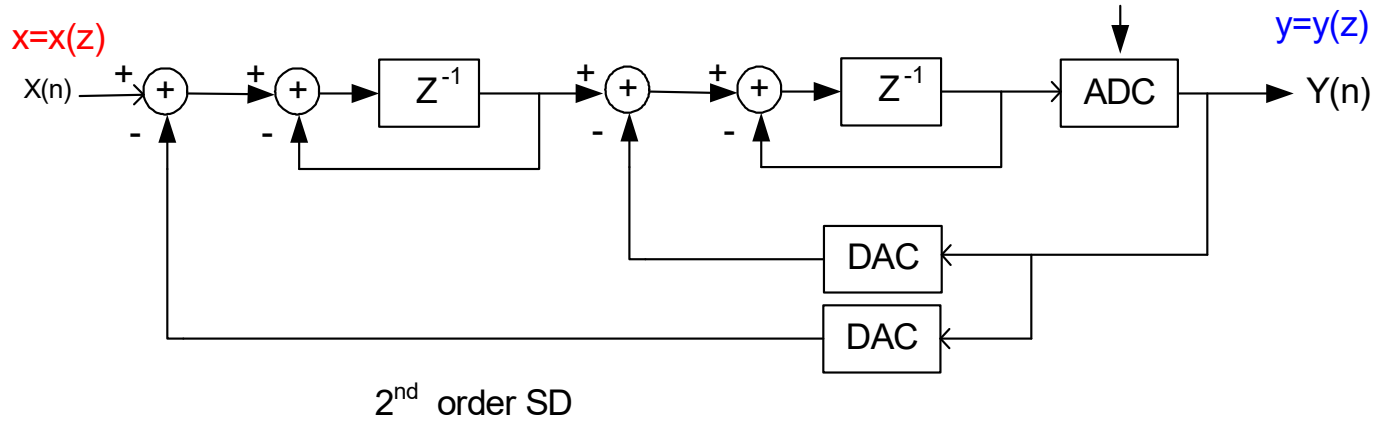SNR for 2nd order SD with Integrator in the Loop



$$Y(z) = z^{-1}X(z) + (1 - z^{-1})^2 E(z)$$

$$Y(z) = H_x(z)X(z) + H_e(z)E(z)$$

with $H_x(z) = z^{-1}$ and $H_e(z) = (1 - z^{-1})^2$




$$y[n] = x[n - 1] + e[n] - 2e[n - 1] + e[n - 2]$$

$$\sigma_{ey}^2 = \int_{-fb}^{fb} P_{ey}(f) df = 2 \int_0^{fb} P_{ey}(f) df = \int_0^{fb} P_e(f) \cdot |H_e(f)|^2 df = \int_0^{fb} \frac{\sigma_e^2}{fs} |1 - 2e^{-j\omega T} + e^{-j2\omega T}|^2 df$$

$$\sigma_{ey}^2 = \sigma_e^2 \frac{\pi^4}{5} \left(\frac{2fb}{fs}\right)^5$$

if r is the number of octaves
 
$$SNR = 10 \log(\sigma_x^2) - 10 \log(\sigma_e^2) - 10 \log\left(\frac{\pi^4}{5}\right) + \underline{15.05r}$$



For every doubling of the OSR, SNR improves by 15dB

(1 - 1/Z) for Multi Loop



Source : miki thesis

The advantage of the NS is that the noise is spread out to the higher frequencies to a location where the signal band is not used. The general form of the $NTF(z)$ is given by

$$NTF(z) = (1 - z^{-1})^p \tag{5.24}$$

where p is the shaping order. For a second order NS, $p = 2$, and for a third order, $p = 3$.

The $NTF(f)$ magnitude is plotted in Fig. 27 for three noise shapers at a sampling frequency, f_s , of $25MHz$. The noise portion is much lower for higher order NS at a low frequency. At about $4.3 MHz$, the noise error crosses at the same point for all the noise shapers. The higher the order, the higher the noise at frequencies closer to $f_s/2$.

 


Figure 27: Simulation plot of NS truncated error coefficient

- 1st-order modulator:
 - 1st-order highpass NTF
 - 9-dB SNR increase per octave OSR
 - i.e. 1.5 bits/octave!
(compared with 0.5-bit/octave for white noise)
- 2nd-order modulator:
 - 2nd-order highpass NTF
 - 15-dB SNR increase per octave OSR
 - i.e. 2.5 bits/octave!
- N th-order modulator:
 - N th-order highpass NTF
 - $6N+3$ dB SNR increase per octave OSR
 - i.e. $N+0.5$ bits/octave!


$$SNR_{\max} = 10 \log \left[\frac{3}{2} (2^B - 1)^2 \frac{(2L + 1) M^{2L + 1}}{\pi^{2L}} \right]$$

$M = \frac{f_s}{2f_B}$ = Oversampling Ratio

L = Modulator Order

B = Internal Quantizer Resolution

Frequency Responses

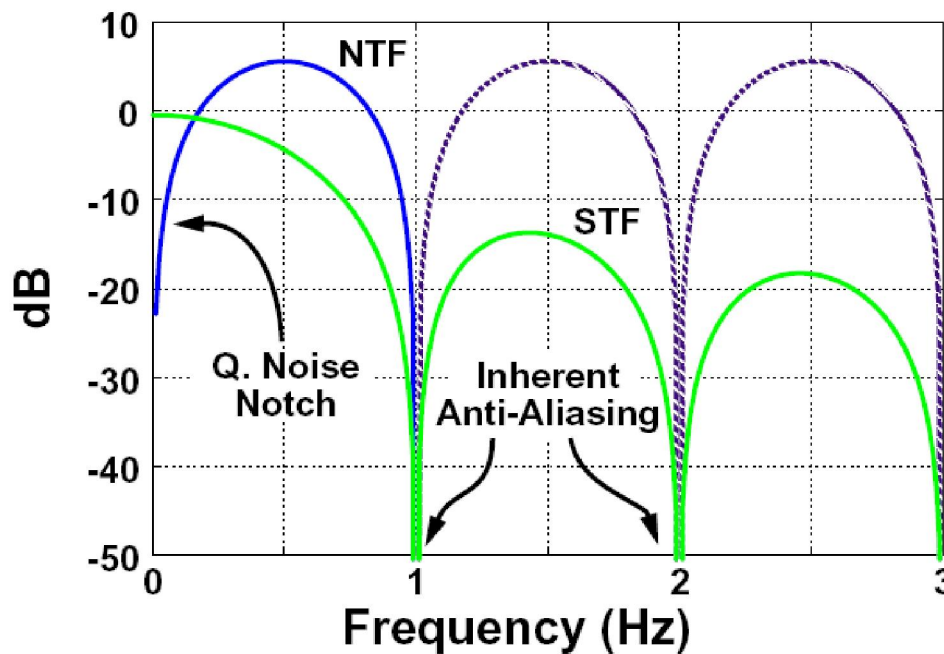

What is really going on:

For 1st order the integrator become LPF and the $1-z^{-1}$ is $2-\cos\omega T$ to the N

Design Example



(assume a's all 1)

Spec: VFs=1v,
Design an ADC for : SNR>86dB, (>14b), fin=0-8KHz,
Extra constrain: Power <2ma, Vdd=3.3v.

Objective:

We need to determin: Loop Order , DAC number of bits, smf Fclock

Option I SigmaD ADC SNR(quantization) CALCULATION miki

DACs Number of Bits []				Oversampling Ratio []	ADC Order []	Overload Voltage []	
B := 5.0				R := 128	n := 1	V := 0.75	
Integrator loop coefficients[]				Fin maximum	Boltzman cond and Temp[]		
a0 := 1.0	a1 := 1.0	a2 := 1.0	a3 := 1	Fin := 8 × 10³	Kh := 1.38 × 10⁻²³	Temp := 293	

1. 1st-order SDM, 5-bit -Quantizer, fs=2.048 MHz, Fin=8 KHz

SNR- Equation

Maximum SNR $SNR_{pk} := \left[(2^B - 1) \right]^2 \cdot (2n + 1) \cdot \left(\frac{R}{\pi} \right)^{(2n+1)} \cdot a_0 \cdot a_1 \cdot a_2 \cdot a_3 \cdot \left(\frac{3 \cdot \pi}{2} \right) \cdot V$ $SNR_{pk} = 6.892 \times 10^8$

In dB

$SNR_{dBpk} := 10 \cdot \log(SNR_{pk})$ $SNR_{dBpk} = 88.383$

Thermal Noise Requirements



If we make the converter with switch cap then the noise...

$$C_{in} := 1 \times 10^{-12}$$

$$V_{nqcap} := \left(\frac{Kb}{C_{in}} \right)^{0.5} \left[\left(\frac{Temp}{F_{in}} \right)^{0.5} \right] \cdot \frac{1}{1}$$

$$V_{nqcap} = 7.109 \times 10^{-7}$$

$$V_{nqcap} := \left(\frac{Kb}{C_{in}} \right)^{0.5} \left[\left(\frac{Temp}{1} \right)^{0.5} \right] \cdot \frac{1}{1}$$

$$V_{nqcap} = 6.359 \times 10^{-5}$$

$$SNR_{dBcap} := 20 \cdot \log \left(\frac{V}{V_{nqcap}} \right)$$

$$SNR_{dBcap} = 81.434 \quad \text{dB}$$

$$F_{ck} := 2 \cdot R \cdot F_{in} \quad F_{ck} = 2.048 \times 10^6$$

$$SNR_{dBcap} := 20 \cdot \log \left[\left(\frac{V}{V_{nqcap}} \right) \left[\left(\frac{F_{ck}}{2 \cdot F_{in}} \right)^{0.5} \right] \cdot \frac{1}{1} \right]$$

$$SNR_{dBcap} = 102.506 \quad \text{dB}$$

The capacitance noise concern to 8 KHz so we get 102dB



Option II SigmaD ADC SNR(quantization) CALCULATION

miki

DACS Number of Bits []

B := 1.0

Oversampling Ratio []

R := 1024

ADC Order []

n := 1

Overload Voltage []

V := 0.75

Integrator loop coefficients[]

a0 := 1.0 **a1** := 1.0 **a2** := 1.0 **a3** := 1

Fin maximum

Fin := 8×10^3

Boltzman cond and Temp[]

Kb := 1.38×10^{-23}

Temp := 293

1st-order SDM, 1-bit -Quantizer, fs=16.138 MHz, Fin=8 KHz

SNR- Equation

Maximum SNR

$$\text{SNRpk} := \left[(2^B - 1) \right]^2 \cdot (2n + 1) \cdot \left(\frac{R}{\pi} \right)^{(2n+1)} \cdot a0 \cdot a1 \cdot a2 \cdot a3 \cdot \left(\frac{3 \cdot \pi}{2} \right) \cdot V$$

SNRpk = 3.672×10^8

In dB

$$\text{SNRdBpk} := 10 \cdot \log(\text{SNRpk})$$

SNRdBpk = 85.649

Option III SigmaD ADC SNR(quantization) CALCULATION

miki

DACS Number of Bits []

$$\mathbf{B} := 1.0$$

Oversampling Ratio []

$$\mathbf{R} := 128$$

ADC Order []

$$\mathbf{n} := 2$$

Overload Voltage []

$$\mathbf{V} := 0.75$$

Integrator loop coefficients[]

$$\mathbf{a0} := 1.0 \quad \mathbf{a1} := 1.0 \quad \mathbf{a2} := 1.0 \quad \mathbf{a3} := 1$$

Fin maximum

$$\mathbf{Fin} := 8 \times 10^3$$

Boltzman condit and Temp[]

$$\mathbf{Kb} := 1.38 \times 10^{-23}$$

$$\mathbf{Temp} := 293$$

2nd order SDM, 1-bit -Quantizer, fs=2.048 MHz, Fin=8 KHz

SNR- Equation

Maximum SNR

$$\mathbf{SNRpk} := \left[(2^{\mathbf{B}} - 1) \right]^2 \cdot (2\mathbf{n} + 1) \cdot \left(\frac{\mathbf{R}}{\pi} \right)^{(2\mathbf{n}+1)} \cdot \mathbf{a0} \cdot \mathbf{a1} \cdot \mathbf{a2} \cdot \mathbf{a3} \cdot \left(\frac{3 \cdot \pi}{2} \right) \cdot \mathbf{V}$$

$$\mathbf{SNRpk} = 1.984 \times 10^9$$

In dB

$$\mathbf{SNRdBpk} := 10 \cdot \log(\mathbf{SNRpk})$$

$$\mathbf{SNRdBpk} = 92.976$$

End Lecture 10