

Welcome to  
7718 semester 1 2022  
Mixed Signal Electronic Circuits

Instructor: Dr. Miki Moyal



Lectures

<http://www.gigalogchip.com/lectures.html>

Lecture 10

*High Speed SerDes Basics*  
*As a Serial link*

Its your grade..

Project/assignments deadline: 1.5 mo. from now end of 2/2023

If you cant please send me e mail few days prior.


[miki@gigalogchip.com](mailto:miki@gigalogchip.com)

Why do we care ?

## CPU Performance Trends

Performance of microprocessor systems has scaled aggressively in the past

– Trend expected to continue

 

CPU freq. goes up  
Everything increases..

But we are blocked.... on speed in and out  
Memory2cpu, chip2chip..data2, data centers,  
I clouds...++

# SerDes


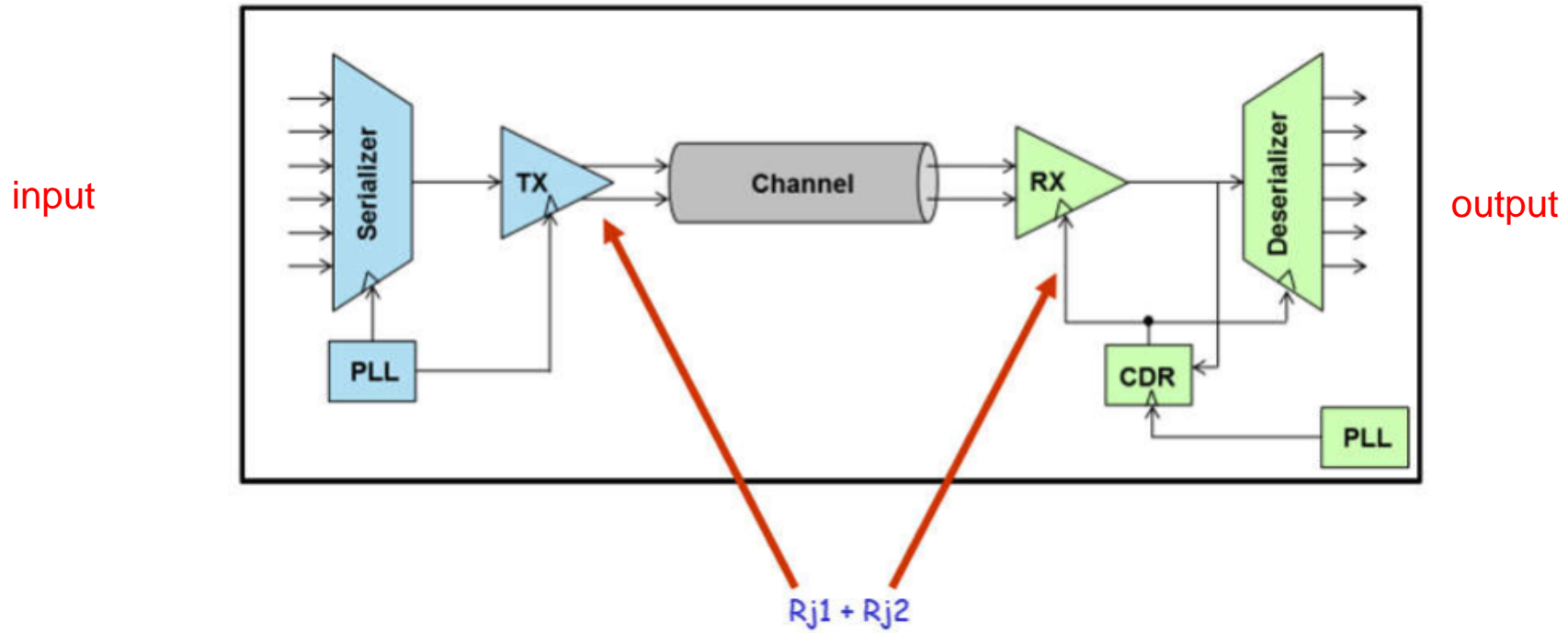


Figure 44: SerDes for simplified jitter places

Want Transfer function = 1

Wireline link


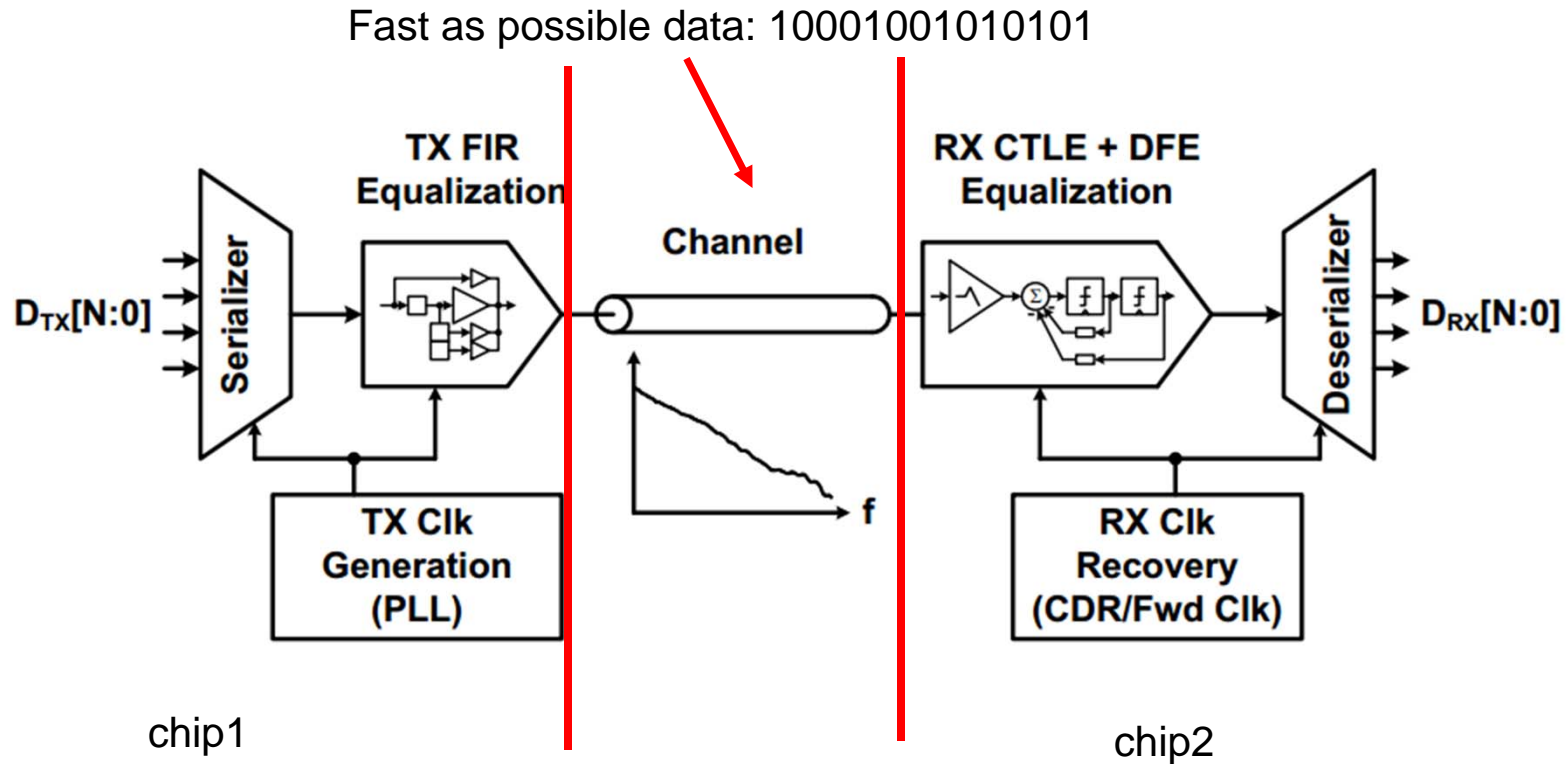


Want Transfer function = 1

Few millimeters to few km ( mostly few cm to 1 meter)


The line and BW.

## Microprocessor/Chipset Interface

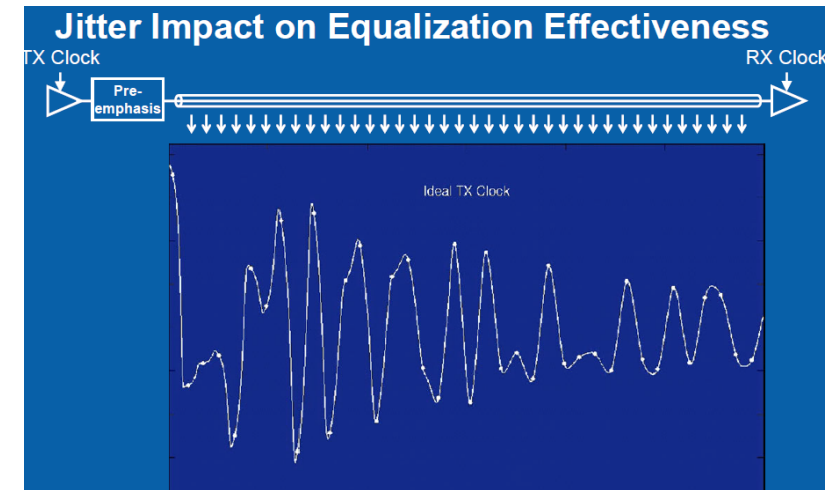 

## Optical link

# High-Speed Optical Link System

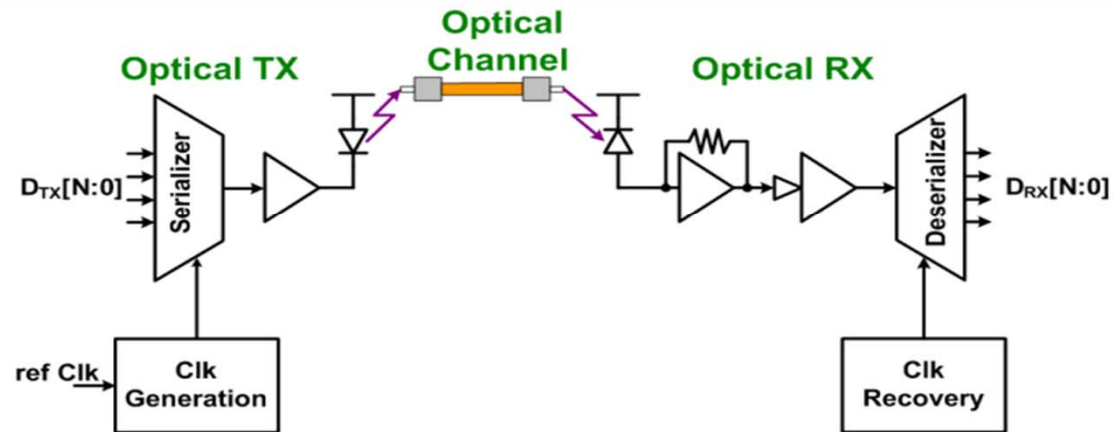


- Optical interconnects remove many channel limitations




## Options to deal with the data and clock...


Easy way out..-

 

Next way out- send clock..

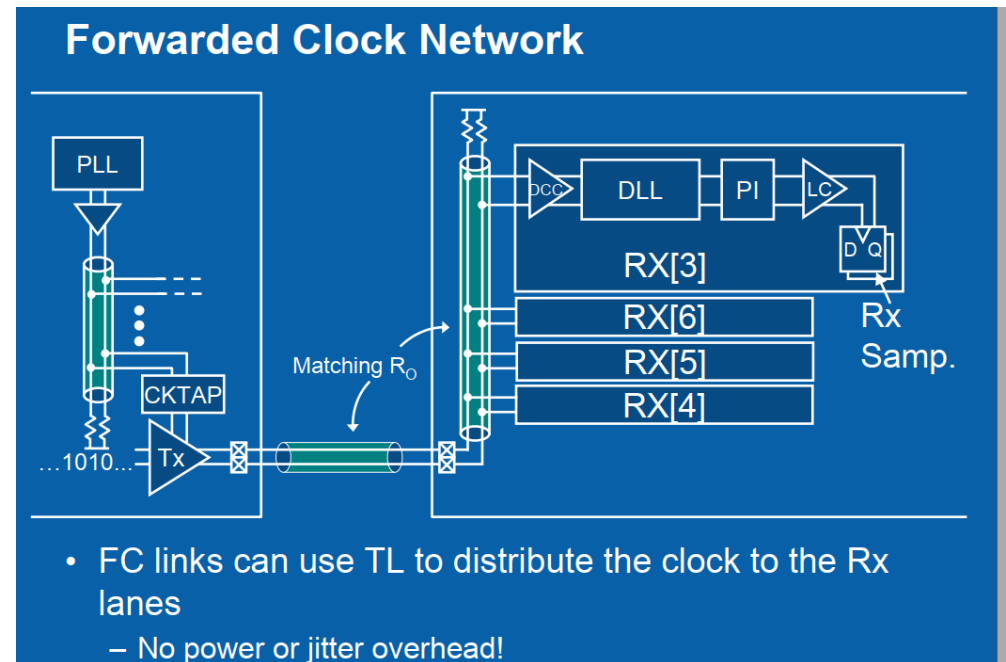

Most do this...

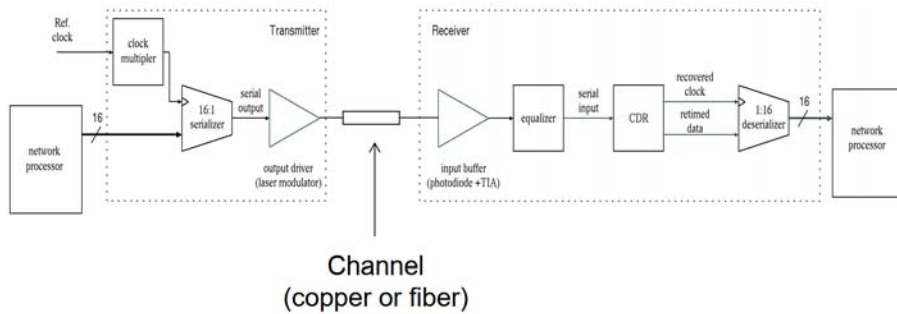



# ISI- How does the line look like when data at different rate passes.


## Inter-Symbol Interference (ISI)

Enclosed is a line with considerably low band with: BW=1.7GHz  
Enclosed is complete simulated Tx. pass

Let's assume a line (from transmitter to the end (beginning of the receiver of about -15dB (equivalent and close to 20cm line).

- Previous bits residual state can distort the current bit, resulting in inter-symbol interference (ISI)
- ISI is caused by
  - Reflections, Channel resonances, Channel loss (dispersion)
- Pulse Response

$$y^{(1)}(t) = c^{(1)}(t) * h(t)$$

 

100ps=5MHz max, data bits and 1.7Mhz BW



 



Figure 31: Loss in a 20cm line using simple RC filter: AC analysis

 


Input green  
Output yellow  
10gb/s

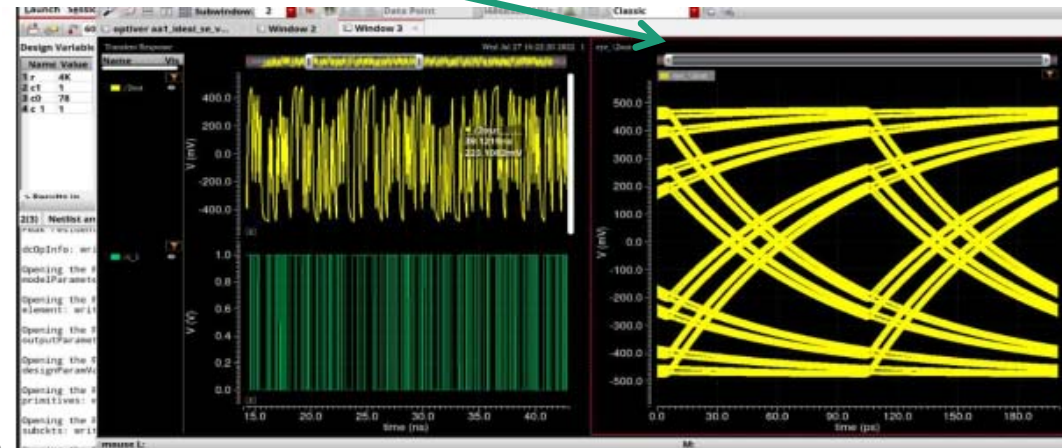

This is what we need.

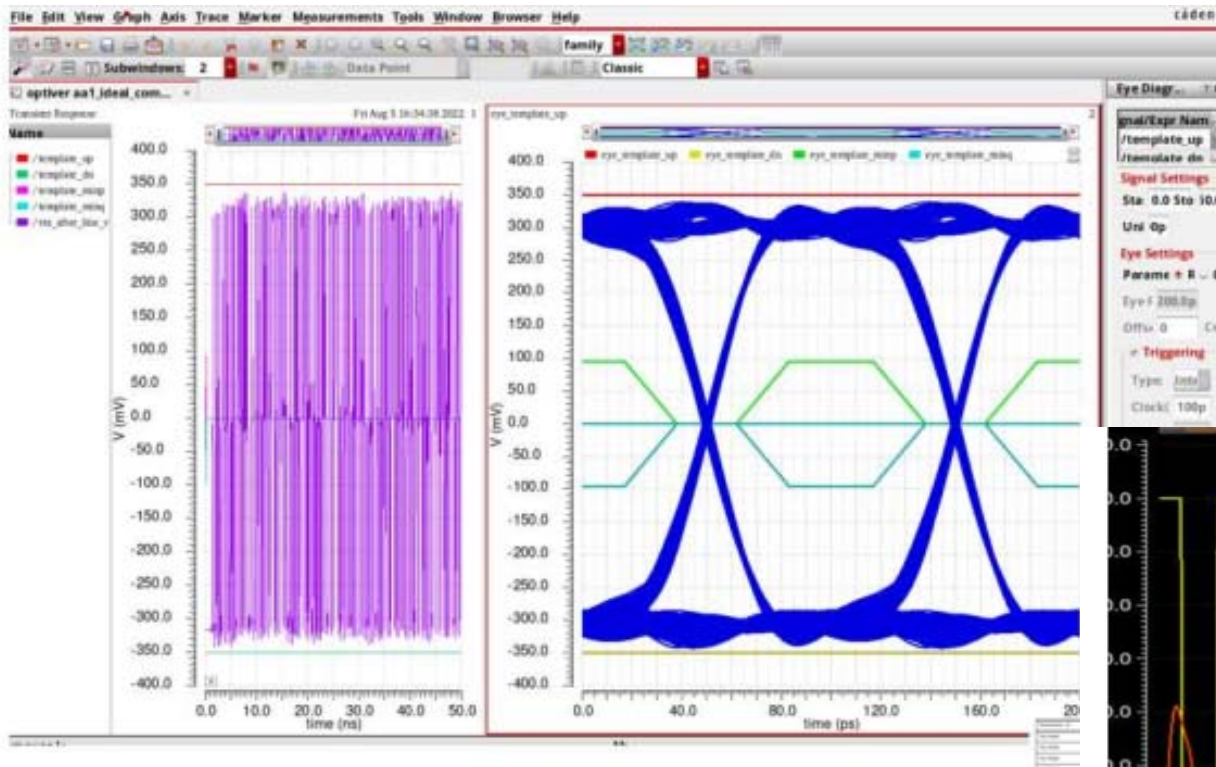

 Want line transfer = 1  
 Impulse response is a way  
 to see the problem..






Frequency to time

- Perform the inverse Fourier transform on the s-parameter of interest

$$h(t) = F^{-1}\{S(\omega)\}$$

 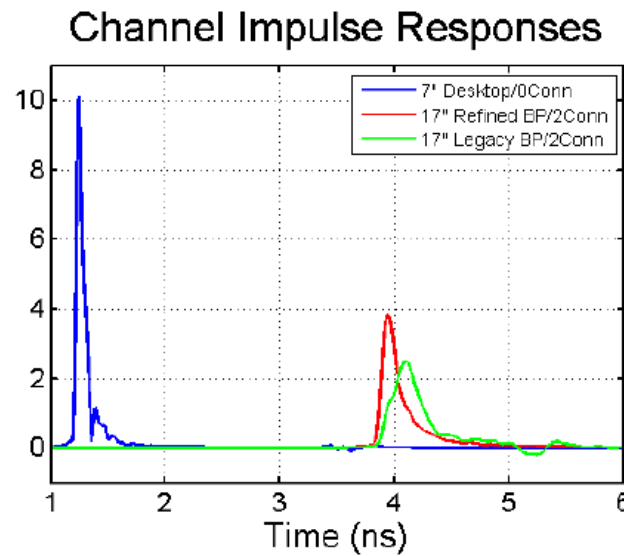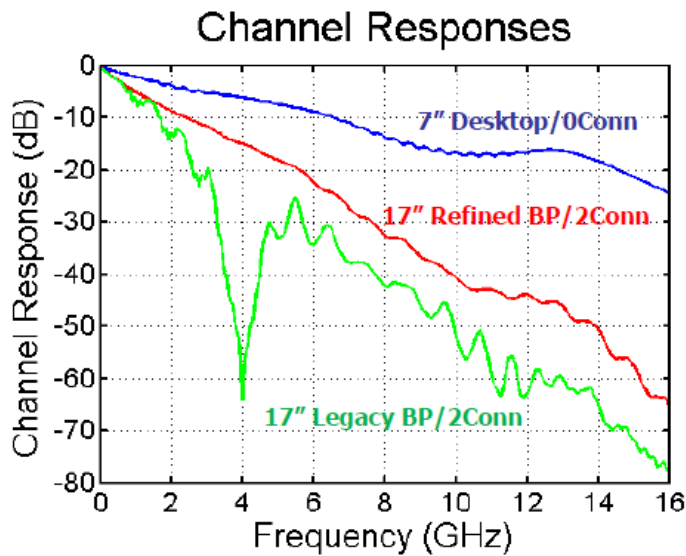
## Impulse Response of Different Channels



Sam Palermo  
 Analog & Mixed-Signal Center  
 Texas A&M University

Example...  
 Look at points in  
 1ui,2ui,3ui..  
 Bad channel can **\*\*last\*\***  
 30 UIs...

# Channel Transient Response

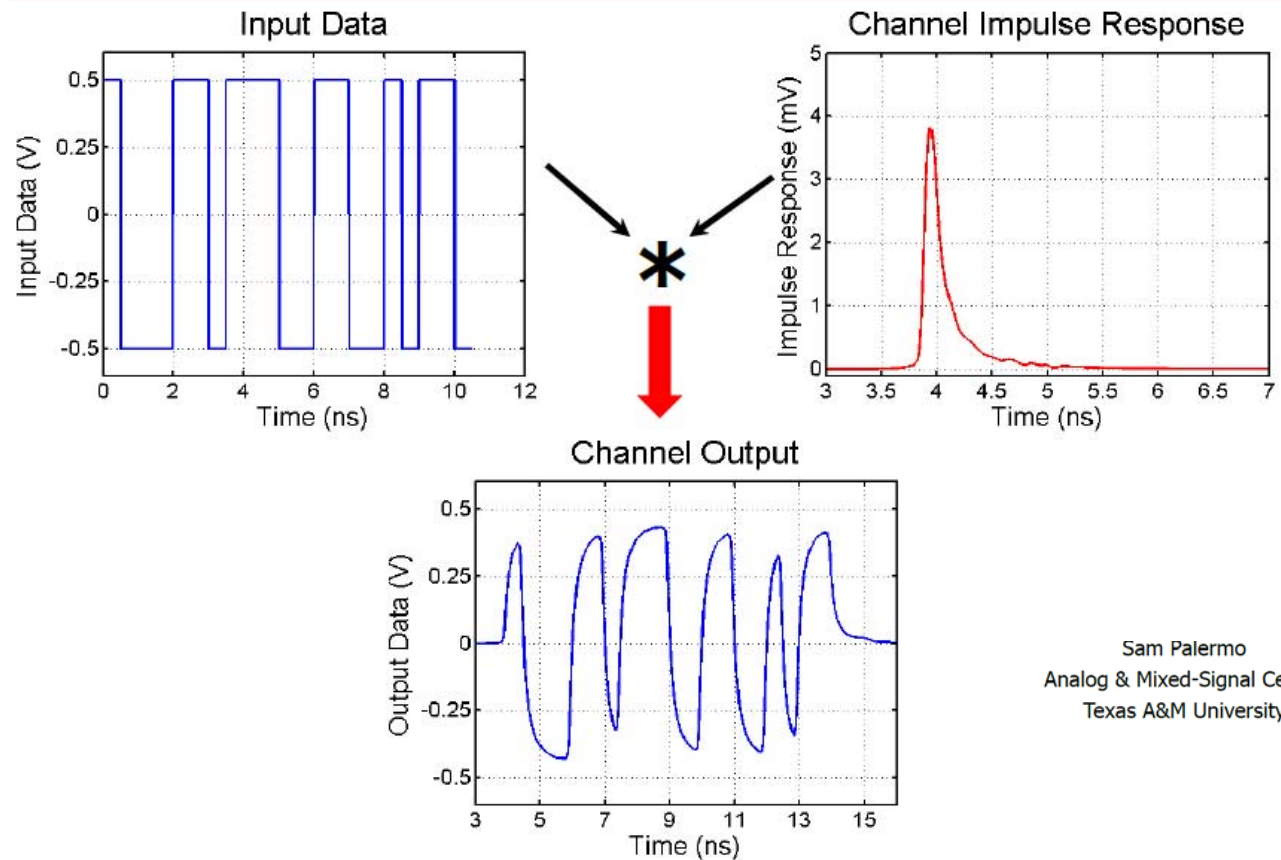

Sam Palermo  
 Analog & Mixed-Signal Center  
 Texas A&M University

What blocks are needed to do the job.

Paralell2serial  
Transmitter buffer and equalization  
Line  
Receiver input (Rx.)  
More equalization in Rx. - active CTLE  
CDR  
Serial2Parallel

# Transmitter.

Paralell-2-serial



# Option 1: Load the group and put them fast 1 by 1..

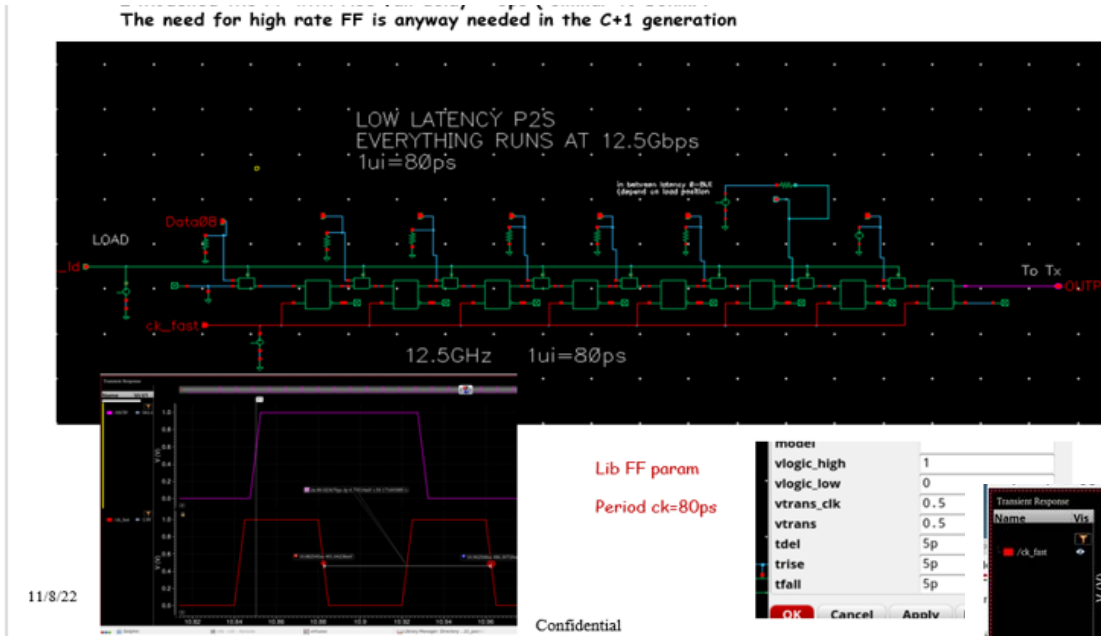


Figure 13: P2S (8:1) low latency design.


 


Figure 14: Mux concept for high level modeling

 

Option 2: cascade ...

# Tree-Type MUX


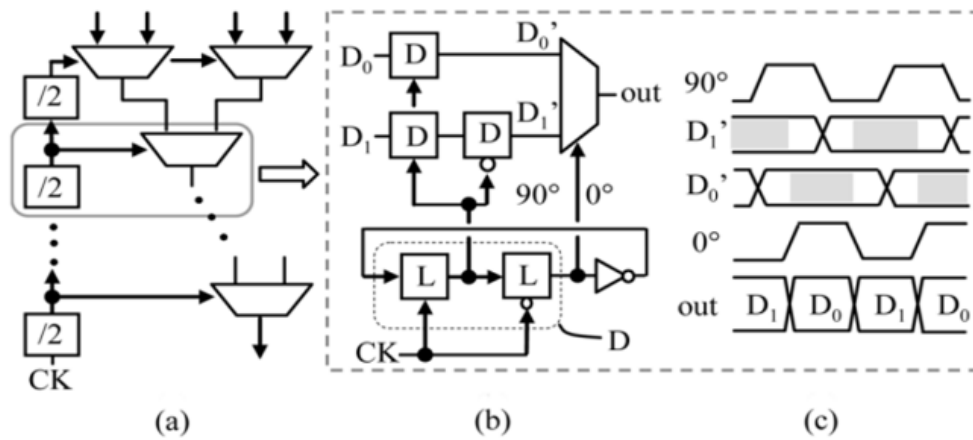


Figure 7 : The basics principle of P2S

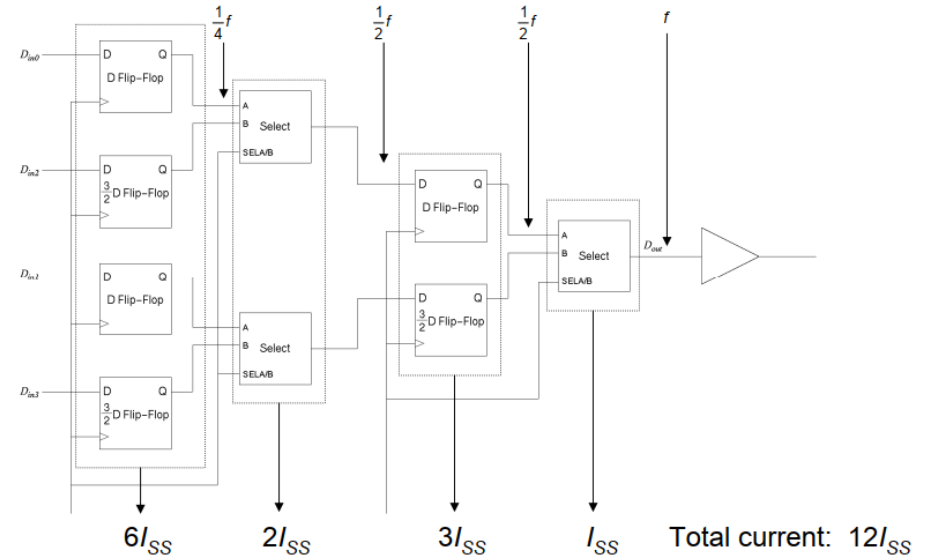

**Assume all blocks have:**

- Tail current  $I_{SS}$
- Resistor  $R$
- Diff pair transistor sizes  $W/L$

What's the difference ?





## Tx. buffer and equalization

How to exit the chip at max. BW ?  
ESD, package, line reflections etc..

max bw = no ISI ~ 3/4bit rare rule

If process is slow.- CML approach.

Evolution :

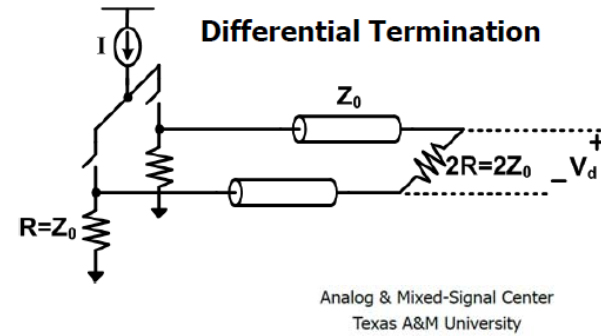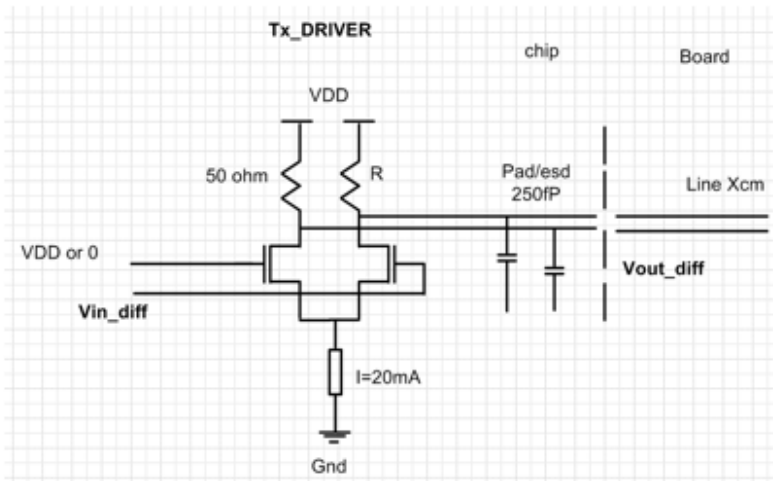


$$V_{d,1} = (I/4)(2R)$$

$$V_{d,0} = -(I/4)(2R)$$


$$V_{d,pp} = IR$$

$$I = \frac{V_{d,pp}}{R}$$

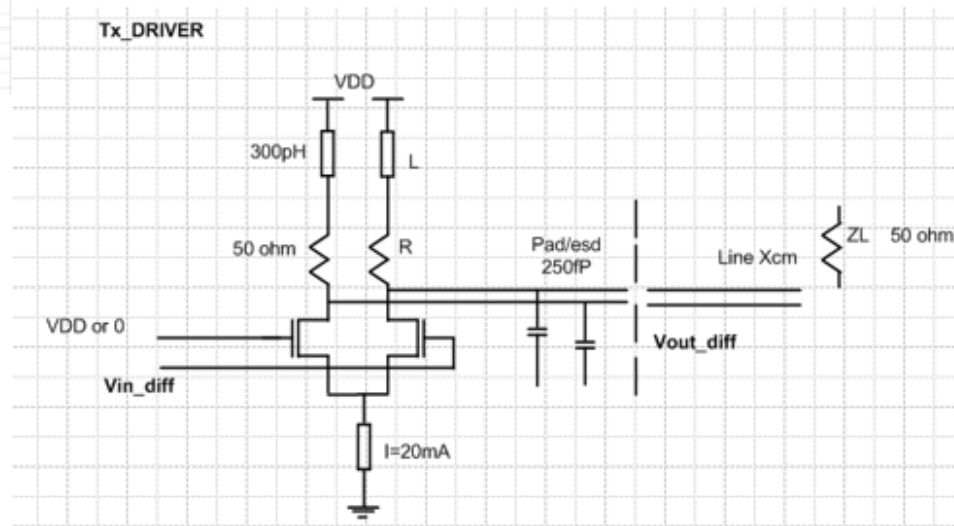
We can add L to make a peaking =  
\*\*cancel the C\*\*



Better way: voltage mode driver.

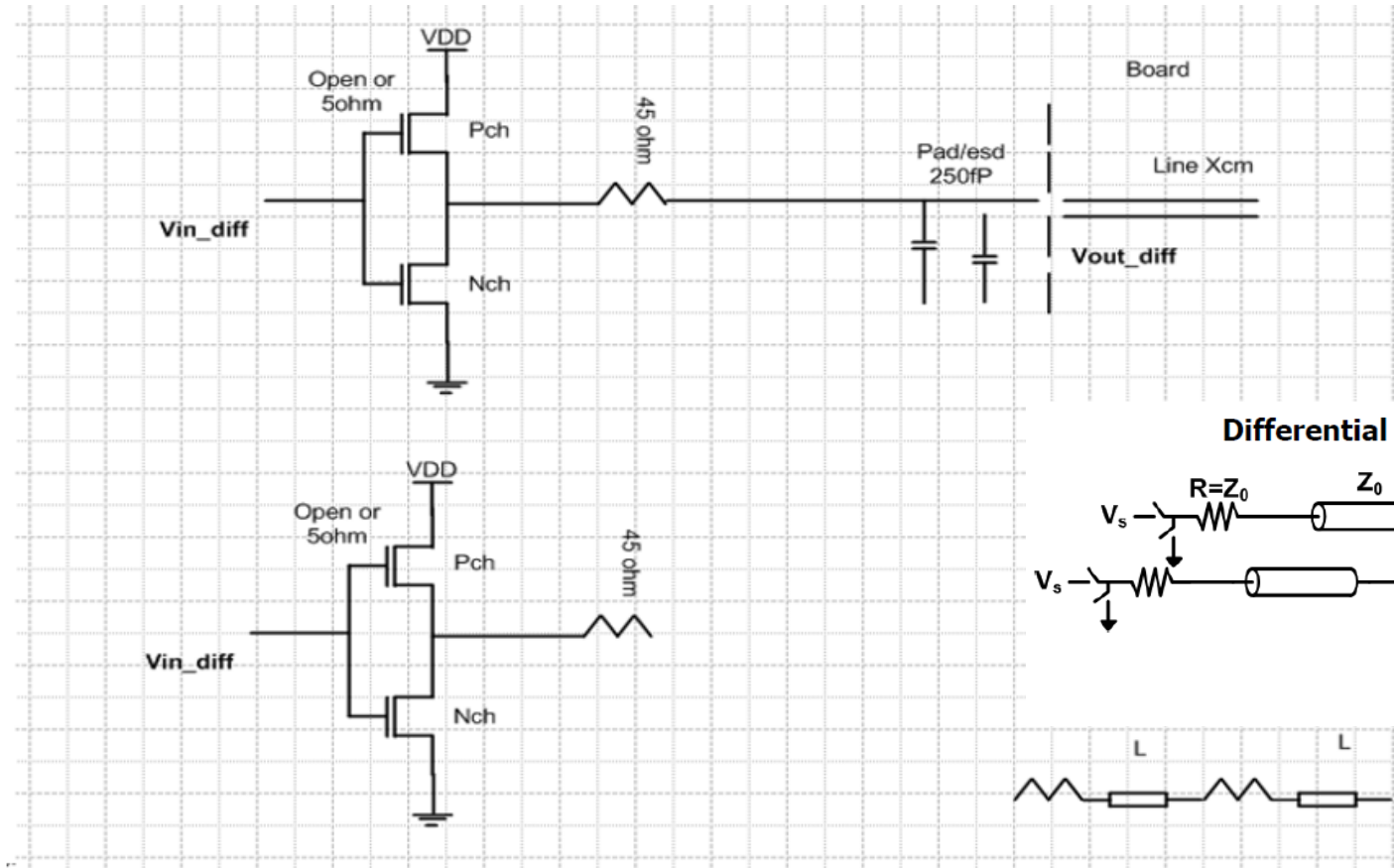

Differential Termination

 

$$V_{d,1} = (V_s/2)$$

$$V_{d,1} = -(V_s/2)$$

$$V_{d,pp} = V_s$$

$$I = (V_s/4R)$$

$$I = \frac{V_{d,pp}}{4R}$$


Analog & Mixed-Signal Center  
Texas A&M University



Figure 19: Voltage mode driver

Power waist is generally about 25% of the CML.


Now lets \*\*add BW\*\*

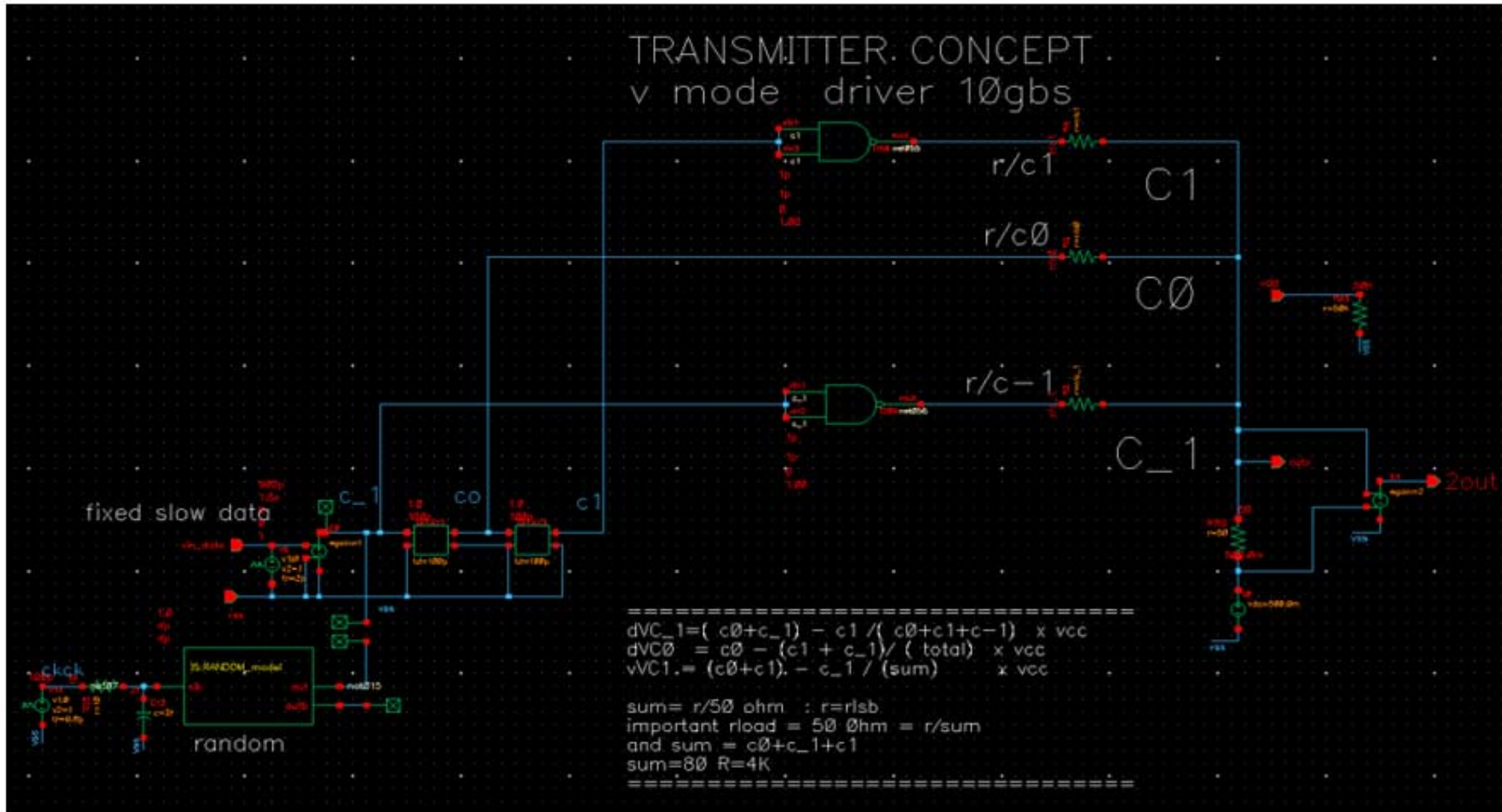

We pay in amplitude sum of R=50 oms


Figure 20: Single ended spice model of a Transmitter concept using 3 taps filter

## How does equalization work ?

 

Tx output view  
 if no capacitance  
 Z-1 and Z-2

## Real v-mode driver

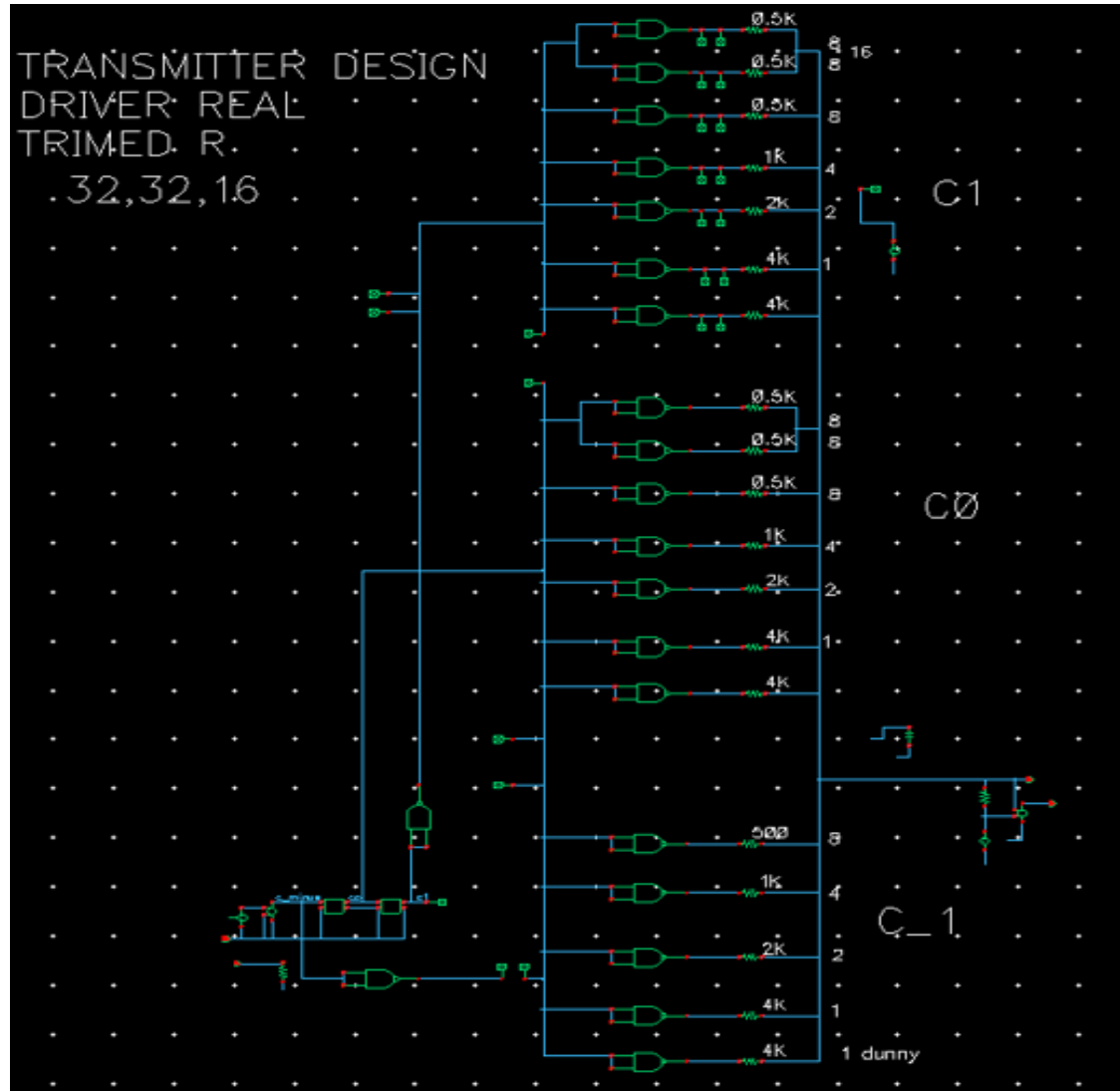

This controls all coef.

And keep 50 ohm  
looking back..



Resulting eye : heavy burden on Z-1..= effective ampl. down

20cm line TF for 10gbit data  
-15dB at 10Ghz

 


Figure 32: Loss in a 20cm line using simple RC filter: AC analysis

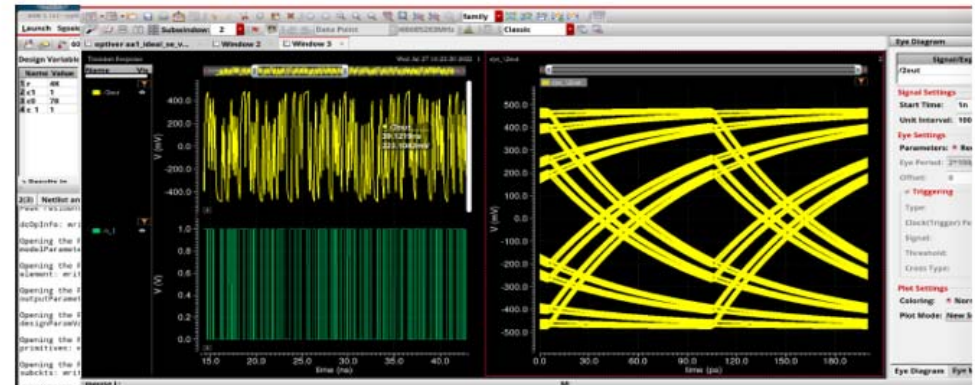


Figure 33: First run non equalized line

Second run with equalization using C1 showing, in red color, is how the line is equalized better.

Name	
1 r	4K
2 c1	19
3 c0	60
4 c 1	1


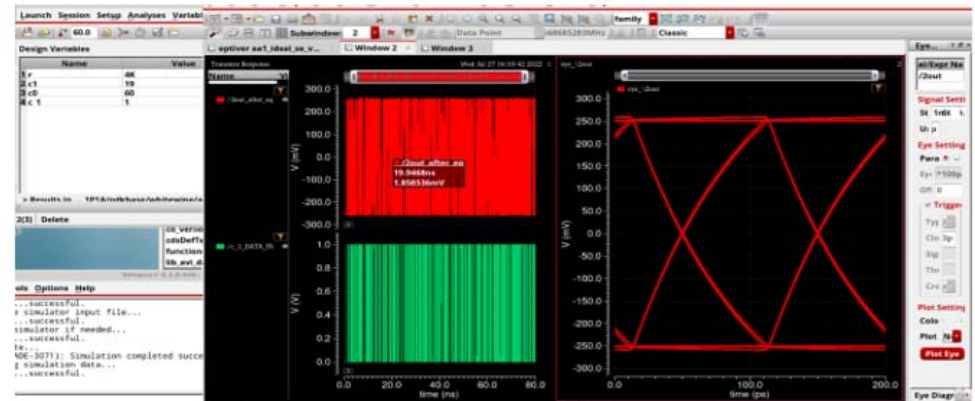


Figure 34: Second run with equalization using C1

## Line length and applications

### CEI-56G Application Space

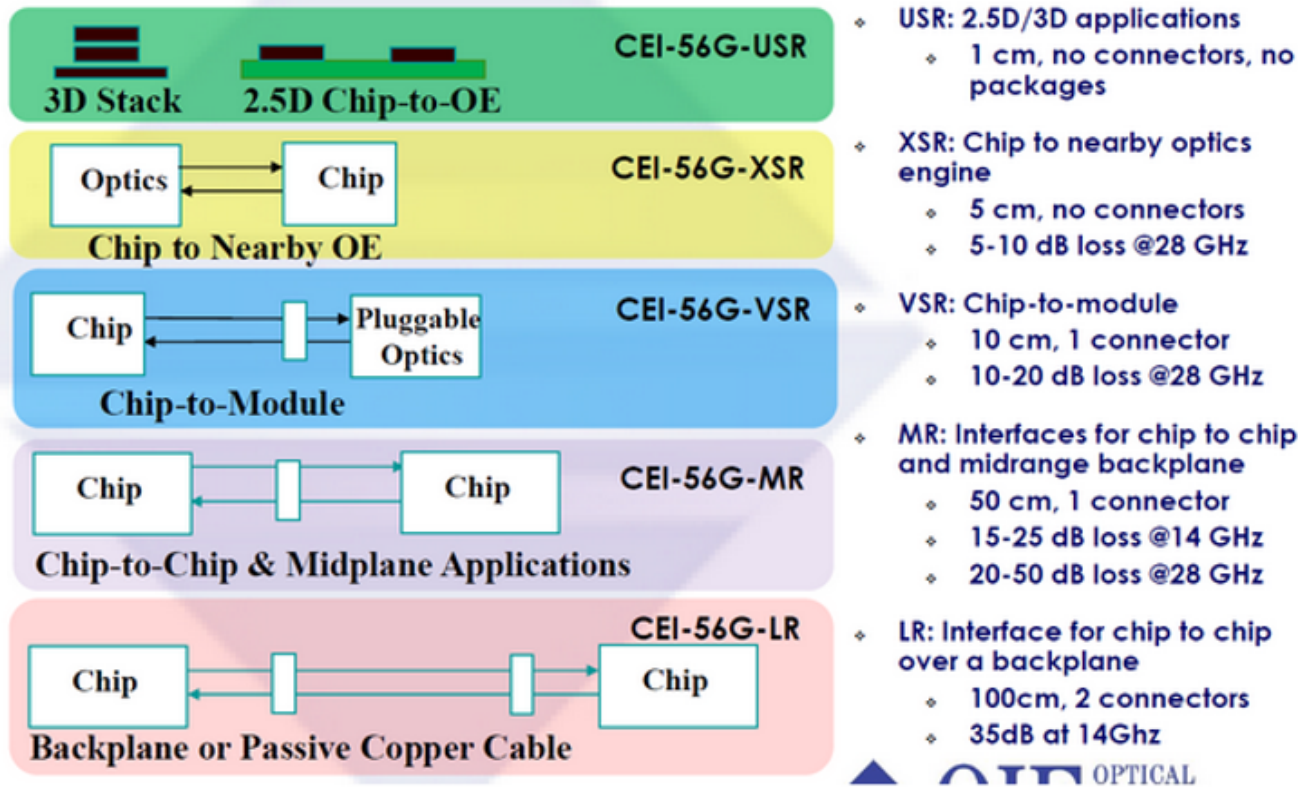

1m "KR" is also challenge



## Line model

The basic equations governing the line shown below.

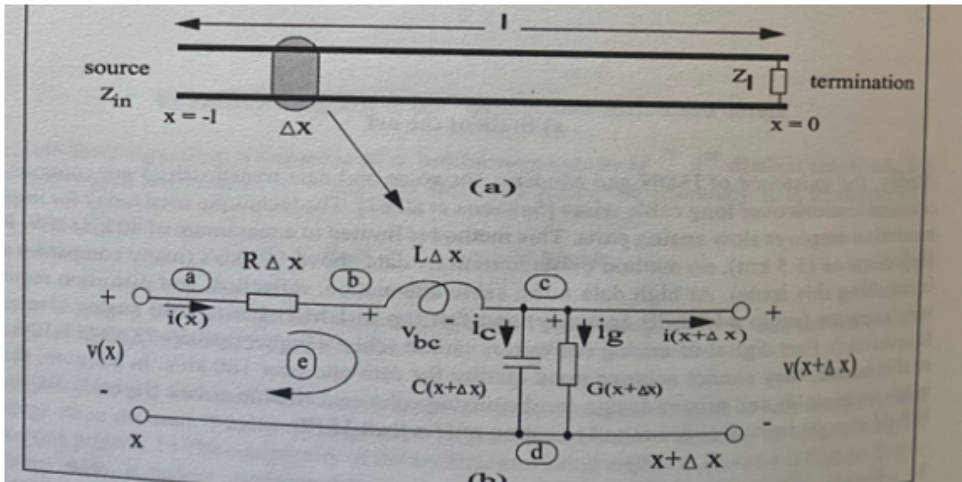


Figure 28: a) uniform transmission line b) lumped parameters

Break the line to segments.

$$\frac{\partial^2 v}{\partial x^2} = RGv + (RC + LG)\frac{\partial v}{\partial t} + LC\frac{\partial^2 v}{\partial t^2}$$

$$\frac{\partial^2 i}{\partial x^2} = RGi + (RC + LG)\frac{\partial i}{\partial t} + LC\frac{\partial^2 i}{\partial t^2}$$

The solution of this model gives the famous \*Telegraph equations\*



# Cable Model

## Copper Cable Model



$$|H(\omega)| \approx e^{-L\alpha\sqrt{\omega}}$$

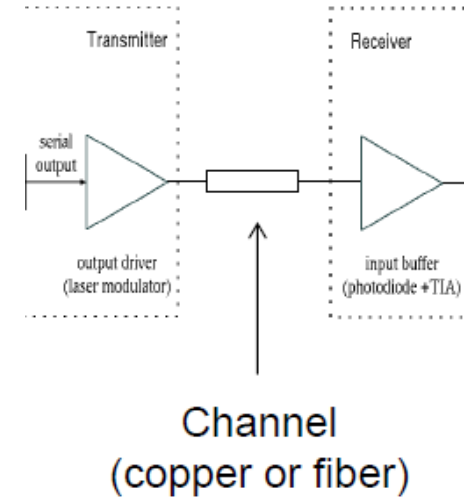 Where:  $L$  is the cable length  
 $a$  is a cable-dependent characteristic



## results

The magnitude response solution of those equations assuming matched line

$$|H(f, l)| = e^{-l\alpha(f)} = e^{-Kl \frac{\sqrt{\pi f/2}}{Z_0}}$$

The above is true if:

$$Z_{in} = Z_0 \cong \sqrt{\frac{L}{C}}$$

$$|H(f, l)|_{dB} = -0.016 \cdot l \cdot \sqrt{f}$$

Eq. 1: Line response in dB the constant -0.016 is only related to cable.

Double the length half the amplitude  
 Double f (at low f) not so steep  
 Double f (at high f) close to the amplitude

### CONCLUSION

**Key \*\*Rule of Thumb\*\*:**

In dB the Insertion loss double if we double the distance

In dB the Insertion loss double in frequency (actually as SQRT(f))

Latency is 30cm=1ns (in air but in FR-4 it's about 2ns).

A LOSS of about 2"/dB for FR-4 at 10GHz.


# Receiver

Receiver front: terminations, equalization, vga.

# Rx equalization.
 
# Passive CTLE

- Passive structures offer excellent linearity, but no gain at Nyquist frequency





$$H(s) = \frac{R_2}{R_1 + R_2} \frac{1 + R_1 C_1 s}{1 + \frac{R_1 R_2}{R_1 + R_2} (C_1 + C_2) s}$$

$$\omega_z = \frac{1}{R_1 C_1}, \quad \omega_p = \frac{1}{\frac{R_1 R_2}{R_1 + R_2} (C_1 + C_2)}$$

$$\text{DC gain} = \frac{R_2}{R_1 + R_2}, \quad \text{HF gain} = \frac{C_1}{C_1 + C_2}$$
 
$$\text{Peaking} = \frac{\text{HF gain}}{\text{DC gain}} = \frac{\omega_p}{\omega_z} = \frac{R_1 + R_2}{R_2} \frac{C_1}{C_1 + C_2}$$




 


$$H(s) = \frac{g_m}{C_p} \frac{s + \frac{1}{R_S C_S}}{\left(s + \frac{1 + g_m R_S / 2}{R_S C_S}\right) \left(s + \frac{1}{R_D C_P}\right)}$$

$$\omega_z = \frac{1}{R_S C_S}, \quad \omega_{p1} = \frac{1 + g_m R_S / 2}{R_S C_S}, \quad \omega_{p2} = \frac{1}{R_D C_P}$$

$$\text{DC gain} = \frac{g_m R_D}{1 + g_m R_S / 2}, \quad \text{Ideal peak gain} = g_m R_D$$

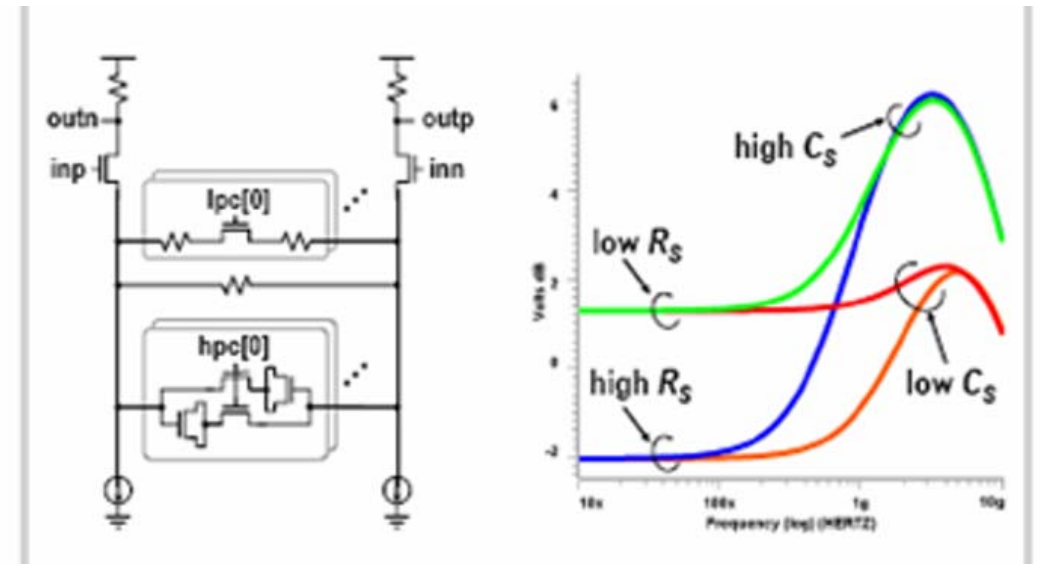 
$$\text{Ideal Peaking} = \frac{\text{Ideal peak gain}}{\text{DC gain}} = \frac{\omega_{p1}}{\omega_z} = 1 + g_m R_S / 2$$





## More equalization in Rx- active CTLE
 
### Active CTLE

Below shown a high pass linear filter used as a CTLE. 2 transistors to convert the voltage input to current injected into the  $V_{o+}$  and  $V_{o-}$ . Are used. The sources of the two transistors now uses a filter R and C which can be thought as impedance varying in frequency. This \*open loop\* amplifier has a gain and Band width all related to the load resistance and the source filter.



without

  


with



 
# CDR

Already reviewed it basics ..  
So lets just go over jitter..and..BER


 
## PLL BERs and Jitter..

- Jitter at a given BER is computed considering both leading and trailing edges



$$BER_{total}(t) = 0.5 \left[ \operatorname{erfc} \left( \frac{t - DJ_{se}/2}{\sqrt{2}\sigma_{se}} \right) + \operatorname{erfc} \left( \frac{t + DJ_{se}/2}{\sqrt{2}\sigma_{se}} \right) \right], \quad BER_{total}(t) = 0.5 \left[ \operatorname{erfc} \left( \frac{UI - t - DJ_{se}/2}{\sqrt{2}\sigma_{se}} \right) + \operatorname{erfc} \left( \frac{UI}{\sqrt{2}\sigma_{se}} \right) \right]$$

where  $\operatorname{erfc}(t) = \frac{2}{\sqrt{\pi}} \int_t^{\infty} e^{-x^2} dx$

TABLE 13-1.  $Q_{BER}$  as a Function of the Bit Error Rate

BER	$Q_{BER}$	BER	$Q_{BER}$	BER
$1 \times 10^{-3}$	6.180	$1 \times 10^{-10}$	12.723	$1 \times 10^{-17}$
$1 \times 10^{-4}$	7.438	$1 \times 10^{-11}$	13.412	$1 \times 10^{-18}$
$1 \times 10^{-5}$	8.530	$1 \times 10^{-12}$	14.069	$1 \times 10^{-19}$
$1 \times 10^{-6}$	9.507	$1 \times 10^{-13}$	14.698	$1 \times 10^{-20}$
$1 \times 10^{-7}$	10.399	$1 \times 10^{-14}$	15.301	$1 \times 10^{-21}$
$1 \times 10^{-8}$	11.224	$1 \times 10^{-15}$	15.882	$1 \times 10^{-22}$
$1 \times 10^{-9}$	11.996	$1 \times 10^{-16}$	16.444	$7.7 \times 10^{-24}$

$$(\text{Random } J * Q_{ber}) + DJ$$

## System Jitter Budget

- For a system to achieve a minimum BER performance

$$UI \geq DJ_{\delta\delta}(sys) + Q_{BER} \sigma_{RMS}(sys)$$

- The convolution of the individual deterministic jitter components is approximated by linear addition of the terms

$$DJ_{\delta\delta}(sys) = \sum_i DJ_{\delta\delta}(i)$$

- The convolution of the individual random jitter components results in a root-sum-of-squares system rms value

$$\sigma_{RMS}(sys) = \sqrt{\sum_i \sigma_{RMS}^2(i)}$$

be careful: what is the relations of phase noise to Jitter ?- integral..

Figure 45: BER and Jitter relations

Data comes with Tx jitter +Tx. buffer+CTLE  
And Recovered clock from CDR Clock (VCO+shaped).

• For a system to achieve a minimum BER performance

$$UI \geq DJ_{off}(sys) + Q_{BER} \sigma_{RON}(sys)$$

**SerDes pll budget**

97 ps

10.3125Gbps

Margin=48.5 ps

Min Data

CDR Clock

ckj=pll jitter rms per side

48.5ps=(14\*2ckj)+12ps(ISI)+8ps(set/hold)+10ps(unsymerty)

• Jitter at a given BER is computed considering both leading and trailing edges

$$BER_{-}(t) = 0.5 \left[ \text{erfc} \left( \frac{t - DJ_{off}}{\sqrt{2} \sigma_{RON}} \right) \right] + \text{erfc} \left( \frac{t + DJ_{off}}{\sqrt{2} \sigma_{RON}} \right) \right], BER_{+}(t) = 0.5 \left[ \text{erfc} \left( \frac{t - DJ_{off}}{\sqrt{2} \sigma_{RON}} \right) \right] + \text{erfc} \left( \frac{t + DJ_{off}}{\sqrt{2} \sigma_{RON}} \right) \right]$$

where  $\text{erfc}(t) = \frac{2}{\sqrt{\pi}} \int_t^{\infty} e^{-x^2} dx$

TABLE 13-1.  $Q_{BER}$  as a Function of the Bit Error Rate

BER	$Q_{BER}$	BER	$Q_{BER}$
$1 \times 10^{-3}$	6.180	$1 \times 10^{-10}$	12.723
$1 \times 10^{-4}$	7.438	$1 \times 10^{-11}$	13.412
$1 \times 10^{-5}$	8.530	$1 \times 10^{-12}$	14.069
$1 \times 10^{-6}$	9.507	$1 \times 10^{-13}$	14.698
$1 \times 10^{-7}$	10.399	$1 \times 10^{-14}$	15.301
$1 \times 10^{-8}$	11.224	$1 \times 10^{-15}$	15.882
$1 \times 10^{-9}$	11.996	$1 \times 10^{-16}$	16.444

Solve for ckj -> PLL max jitter= 660fsx2=1.2ps  
T sav keep it under 400fs

END

And.. Good luck (with some hard work) on the project

