

Welcome to
0510.7720.01 Winter semester 2021
Mixed Signal Electronic Circuits
Instructor: Dr. M. Moyal

Lecture 9 (after lect. 10/11)02/06/2021..

SUCCESSIVE APPROXIMATION ADC: Operation

Design of Time Continuous SARs

Design of Switch C SAR

Error sources

❑ ADC Architectures

❑ SAR ADCs

❑ Error Sources

A/D Converter ca. 1954


- ◆ 19" x 15" x 26"
- ◆ 150 lbs
- ◆ 500W
- ◆ \$8,500.00




Courtesy,
Analogic Corporation
8 Centennial Drive
Peabody, MA 01960
<http://www.analogic.com>

Figure 4.3: 1954 "DATRAC" 11-bit, 50-kSPS SAR ADC
Designed by Bernard M. Gordon at EPSCO


Common Data Acquisition Architectures

 

FLASH ADC

 


Sub ranging

 


With S/H


SAR

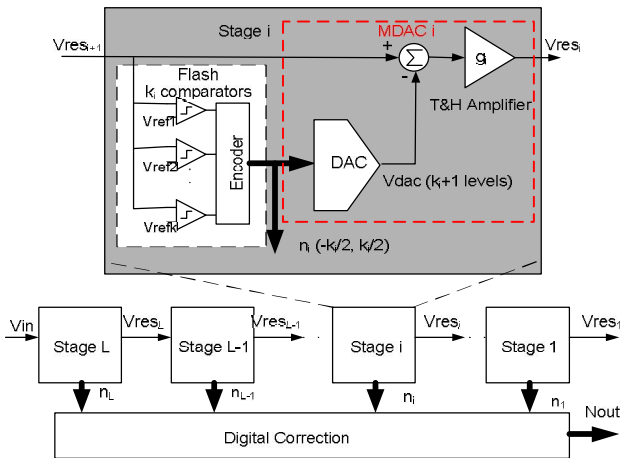

TAU 05 Pipe Line

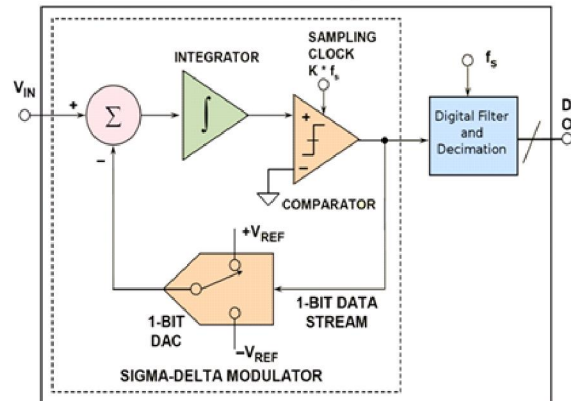

Sigma Delta

 


SD multi bits




miki

Technion

ADC Architectures

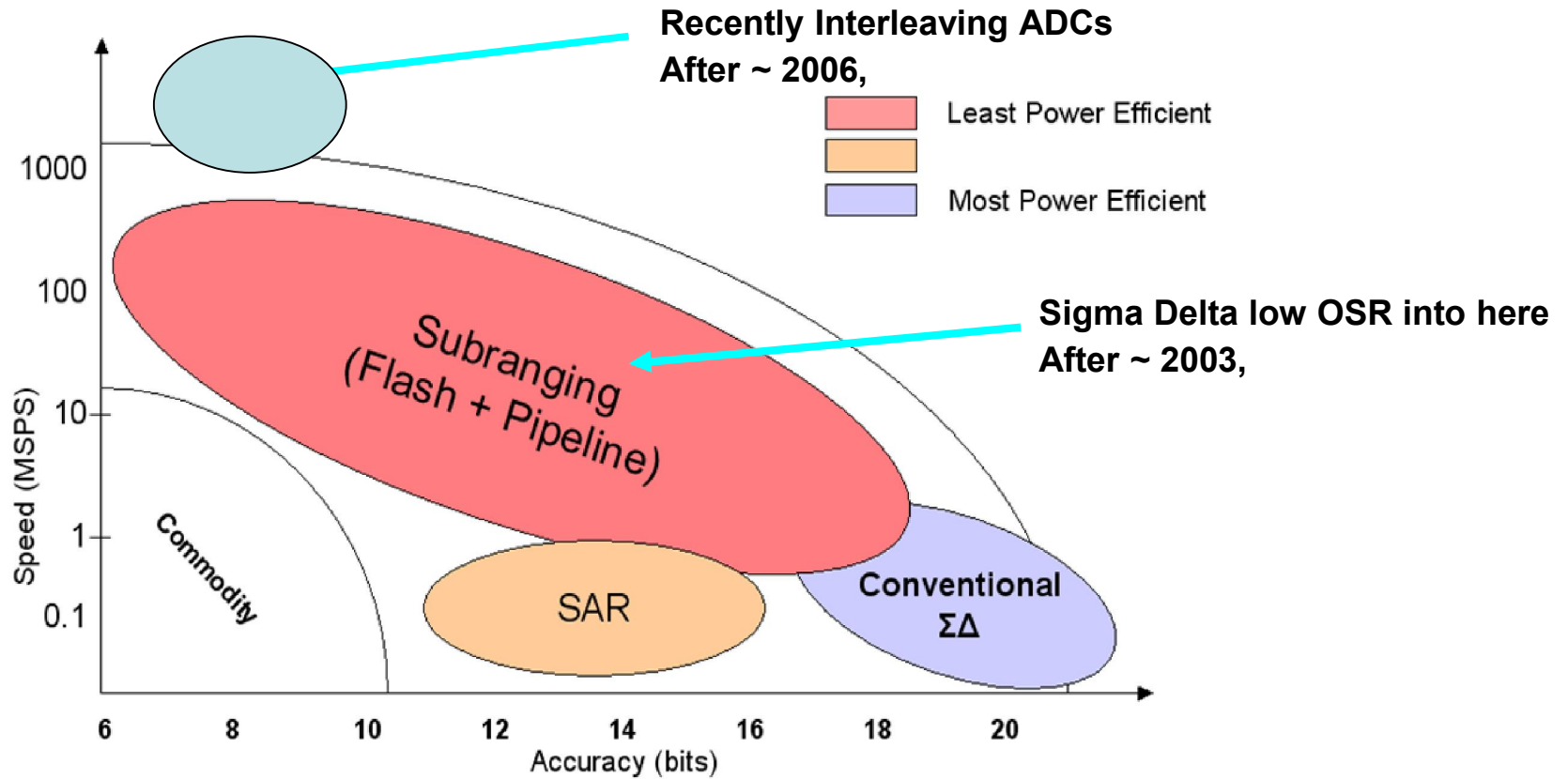

SAR ADC FOM History

 


2006 → 12b & 100Ks/s (180nm CMOS)

2007 → 9b & 50Ms/s (90nm CMOS)

2008 → 9b & 40Ms/s (90nm CMOS)
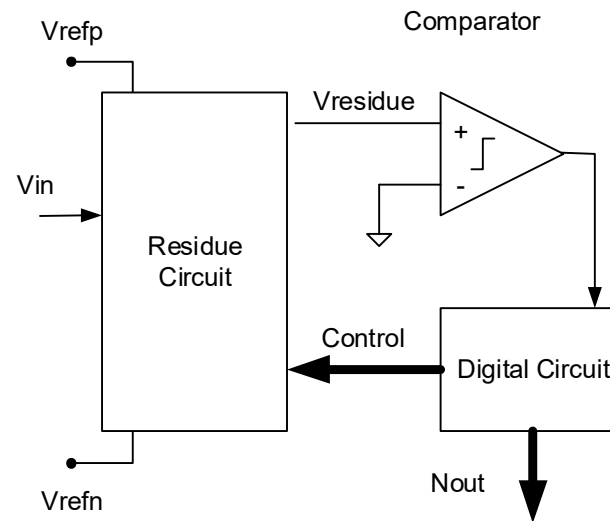
$$\frac{\text{Energy}}{\text{Decision}} = \frac{\text{Power}}{\text{SamplingRate} \times 2^{N\text{bit}}}$$



- $V_{residue}$ is a function of $V_{in} - V_{ref}$.
- The Residue sets the source of Linearity Errors
- The Comparator set the source Speed (Offset may be a problem)

- Must check always:
 - Distortion (non linearity's) and ckt noise.
 - Speed and Power

Successive approximation ADC



If T_s is twice maximum BW


And if N =desire bits

It requires minimum of $p= N \times T_s$ passes to generate N bit

Output words limiting the through put

It requires N -bit accurate DAC


It requires faster settling elements

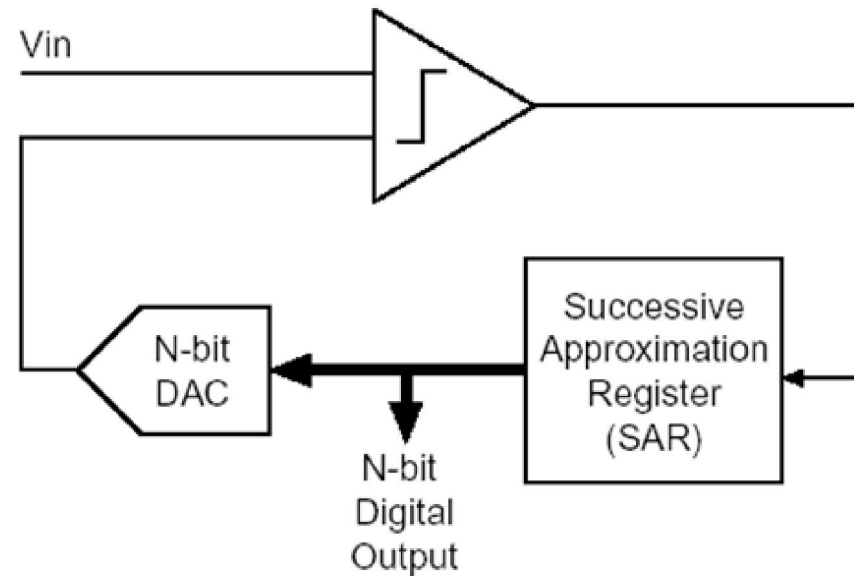


Strict timing is involved- transforming analog to digital each cycle

Comparator runs inside an open loop circuit
therefore stability and closed loop Band width is not an issue.


Flow Chart of SAR ADC

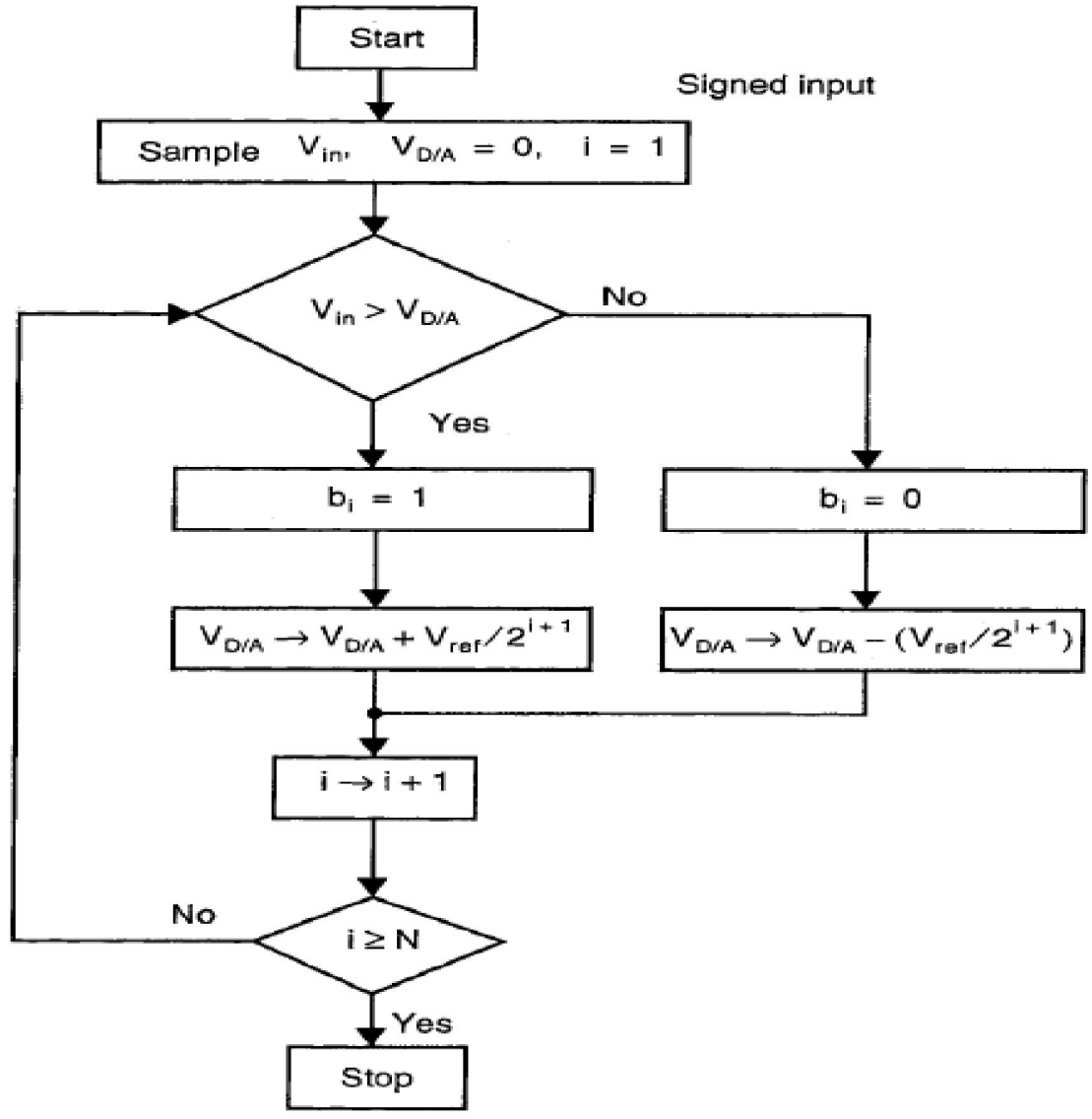


SAR ADC Details

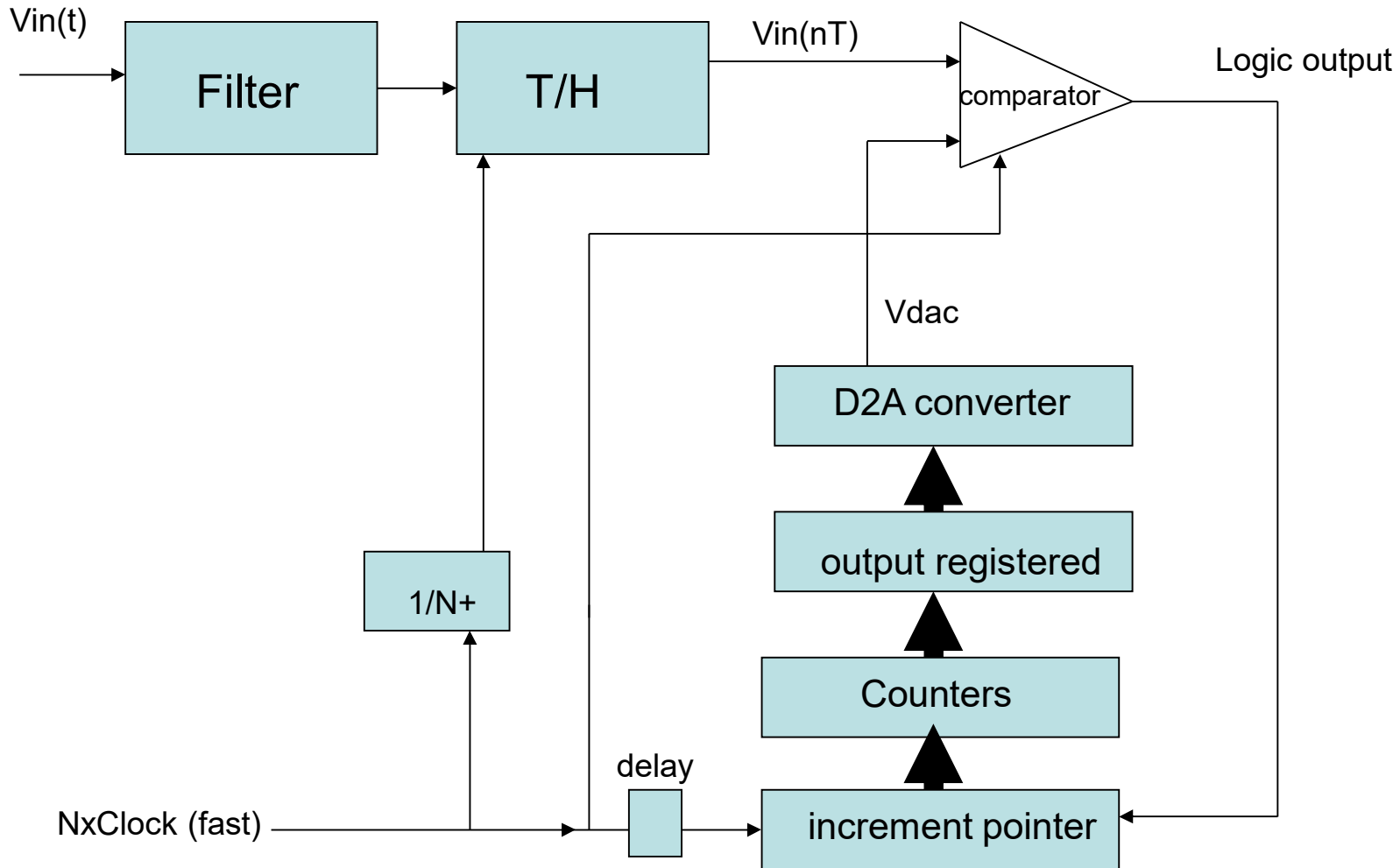

SAR ADC – Timing

 

SAR Operation/Design

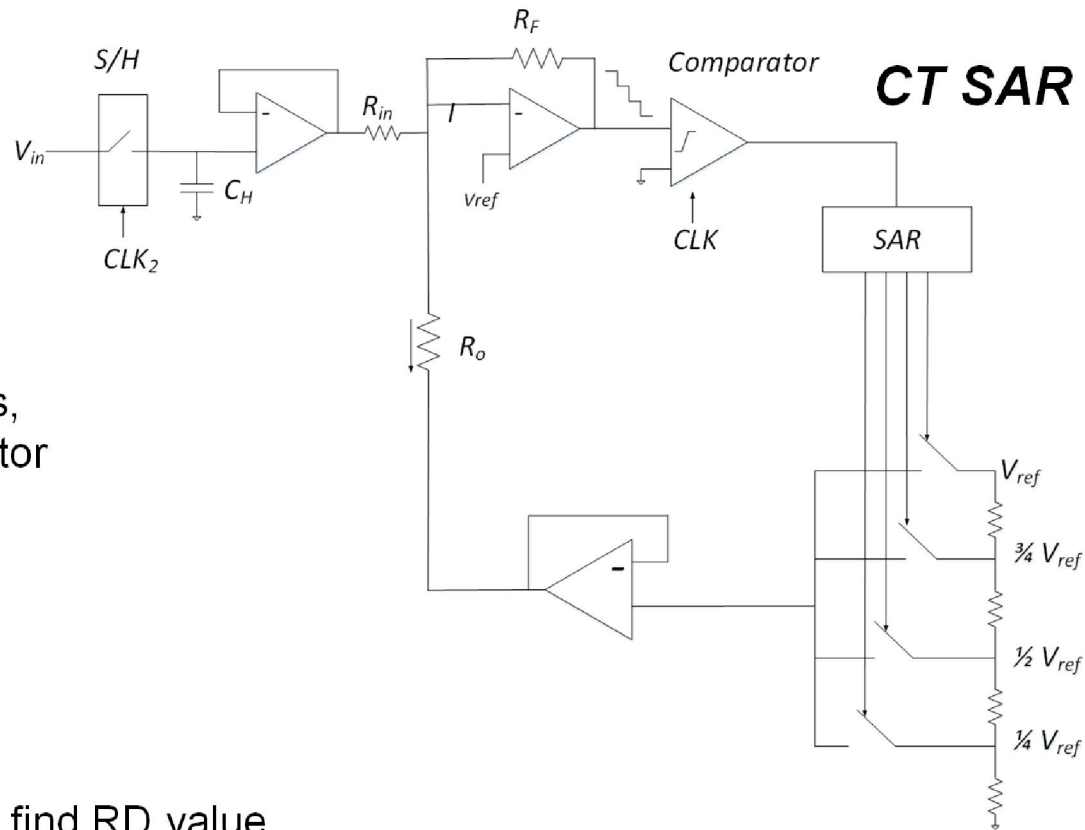


Continuous,
w. sub tractor

How to find RD value

$$R_D \gg \frac{V_{in_max}}{R_{in}} = \frac{V_{ref}}{R_D}$$

$$R_D = \left[\frac{V_{in_F.scale}}{V_{ref}} \right]^{-1} R_{in}$$

❑ 1st step sample and hold

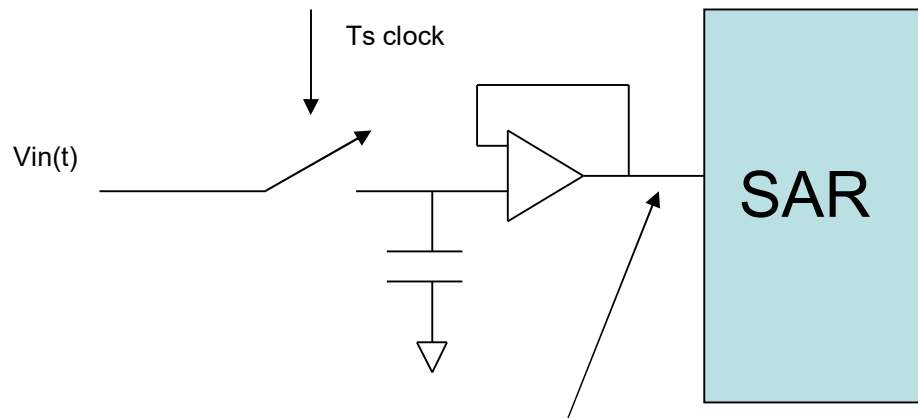


Will be Covered later

- ❑ We know the errors,
- ❑ We know the speed needed
- ❑ We can proceed to build the block



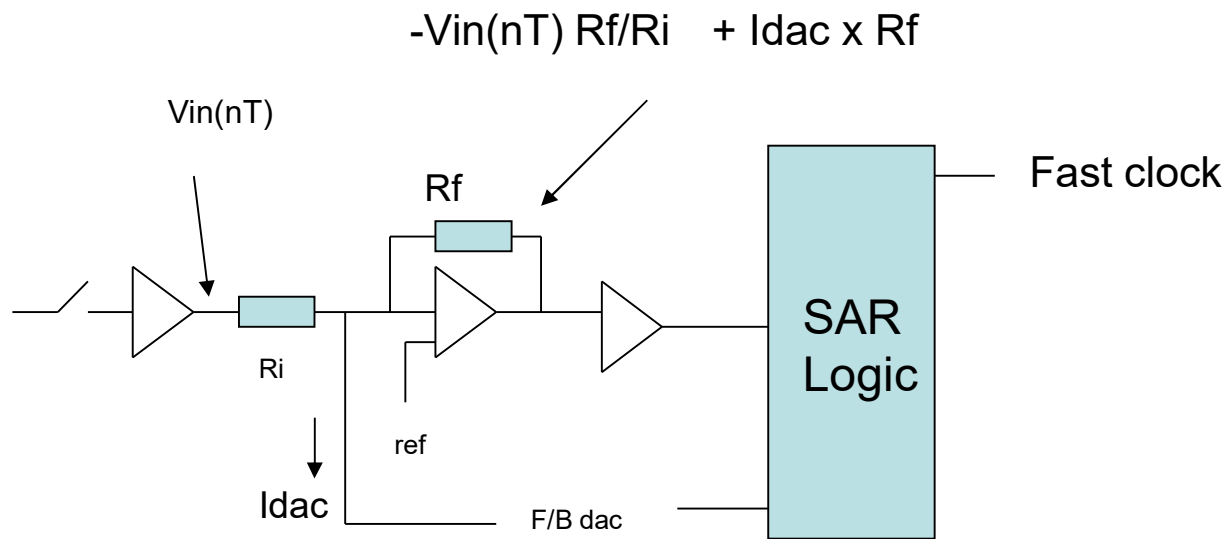
□ 2nd step the sampled voltage part is being converted to I



Next how to build IDAC

SAR IDAC Feedback Generation

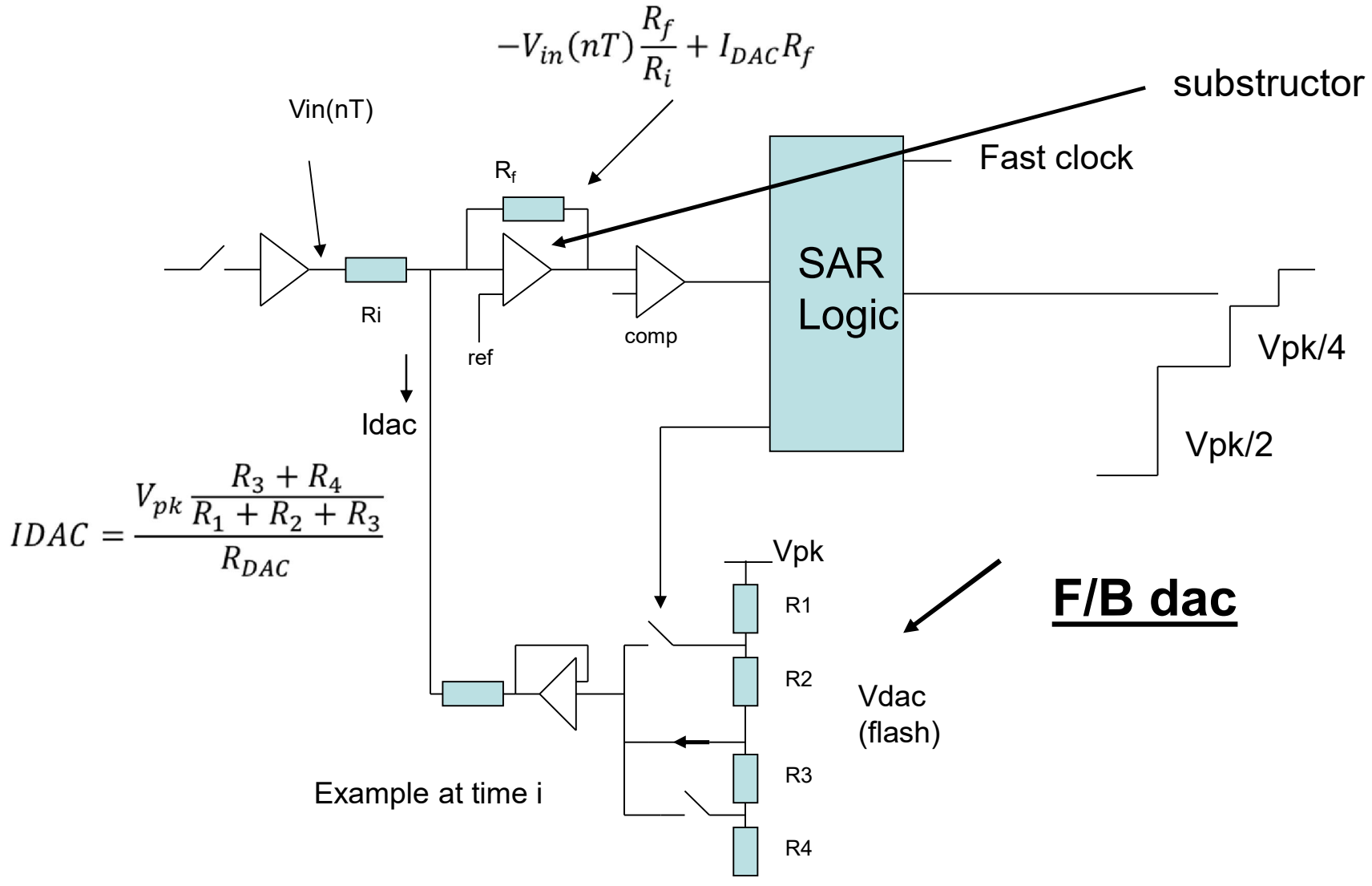- 3rd step the I_{in} and IDAC is compared around the loop n times




- Go to DAC lecture pick another type ?
- We got transistors they are small
- Current is always easy to generate with transistors

SAR DAC – Another DAC – Speed and Area Improvement


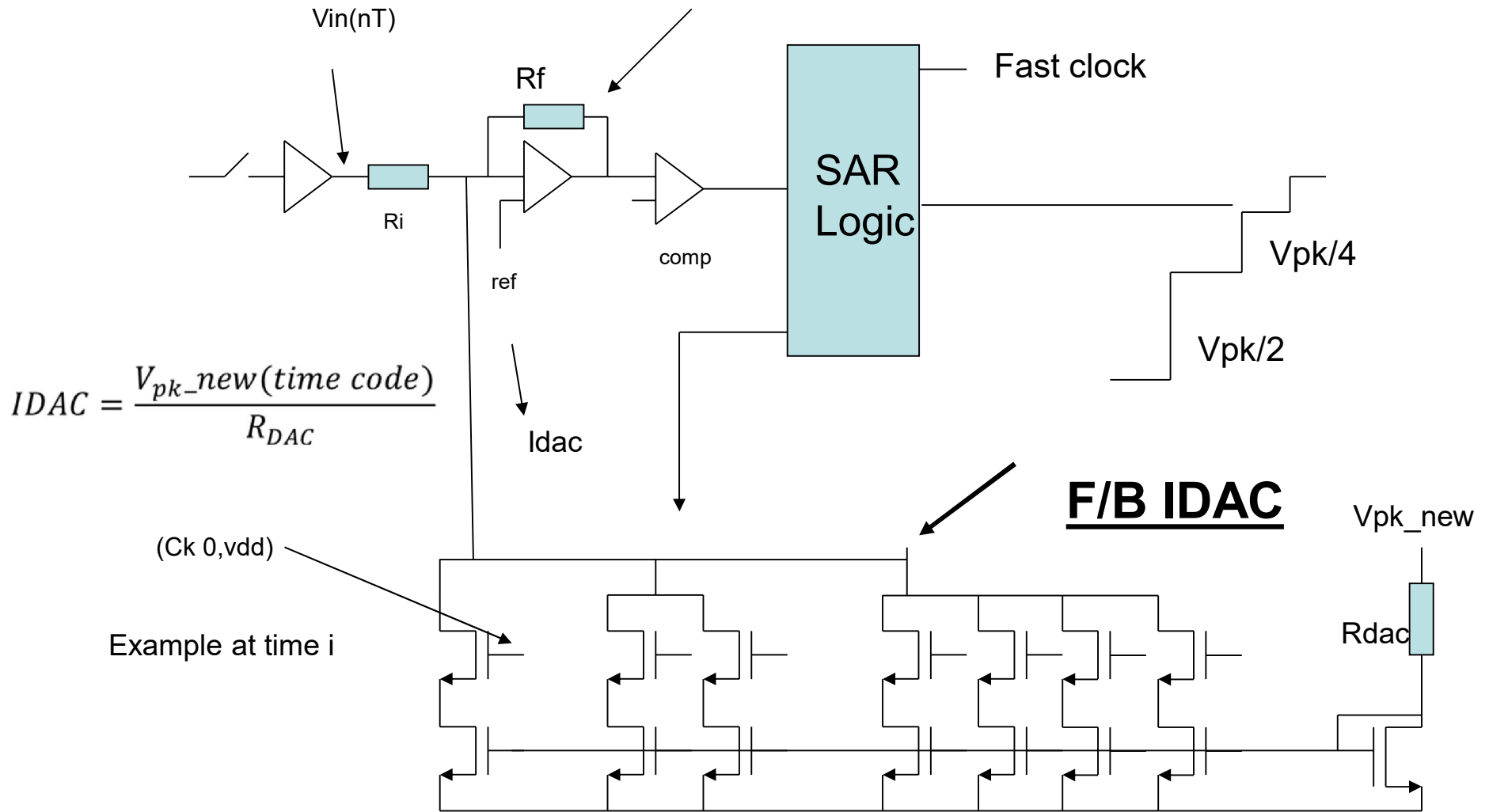
$$-V_{in}(nT) \frac{R_f}{R_i} + I_{DAC} R_f$$



- We used “not so efficient design”

- Speed issues:
 - BW amplifier,
 - Subtraction with amplifier
 - S/H - or Track and Hold.
 - Area

- Can we do it other way?
- Lead to a simpler architecture
- No amplifiers ! !
- With capacitors we can easily subtract**
- Speed per cycle may be faster


We want to generate

$V_{ref}/2$	1 st clock cycle
$V_{ref}/2 \pm V_{ref}/4$..	2 nd clock cycle
$V_{ref}/2 \pm V_{ref}/4 \pm V_{ref}/8$	3 rd clock cycle
Etc...., ,	

So lets use capacitor DAC to do this.

Charge Distribution SAR DAC Operation

 Step 1.- clock $n=1$, reset everything to 0 point – “wasted state” but needed because capacitors plates are held at a “value” for DC





$V_{out} = 0v$ all capacitors plates are shorted to 0
In reality after $nR_{on}C/2$ time ($R_{on}=1/u_{cox}(v_{gs}-v_t)(w/l)$)

Generate $V_{ref}/2$ to Compare



  Step 2.- clock n=2, generate $v_{ref}/2$ to compare with input




$$V_{out}(2T) = 0 + \frac{1/S0.5C}{(1/S0.5C + 1/S0.5C)} V_{ref}$$

$$V_{out}(2T) = \frac{1/0.5}{(1/0.5 + 1/0.5)} V_{ref}$$

$$\mathbf{V_{out}(2T) = V_{ref}/2}$$


Compare to $V_{ref}/2$ and Generate $V_{ref}/2 + V_{ref}/4$

still in time = "2"

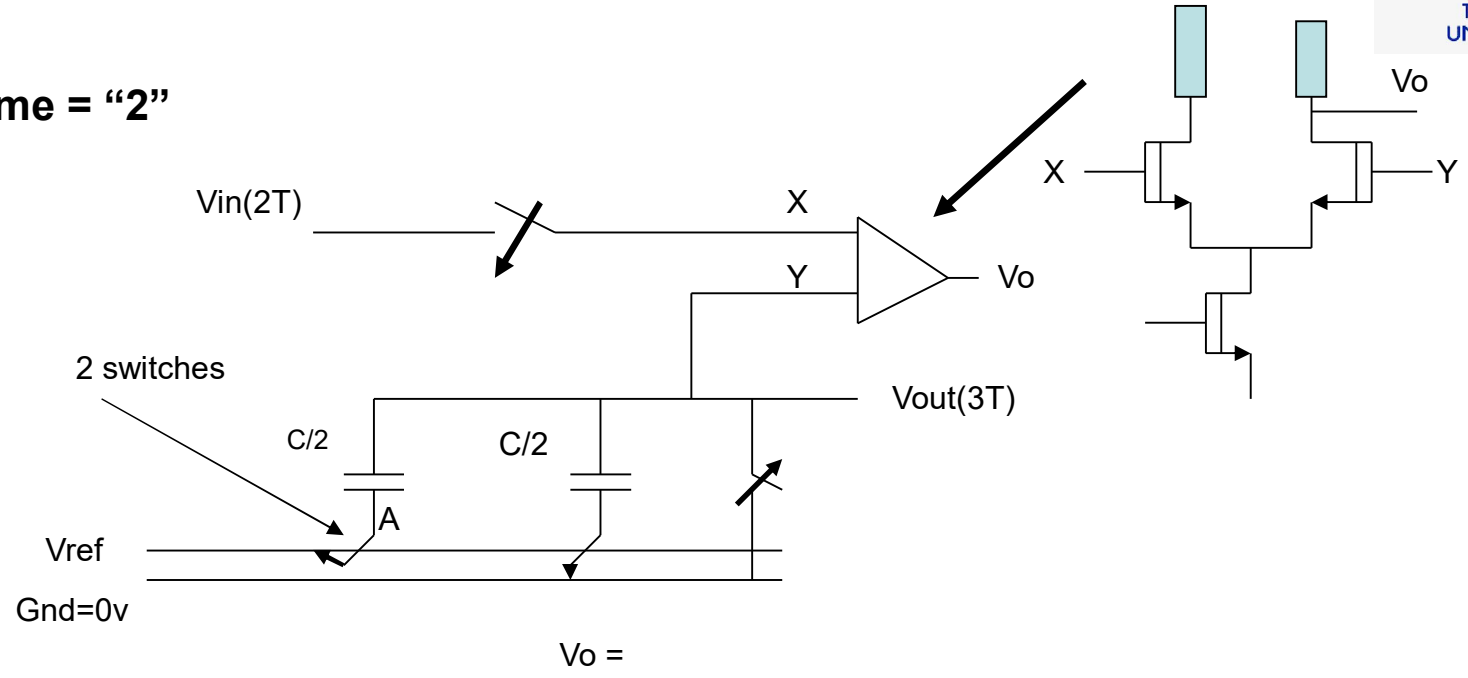


in time = "3" add $1/4$ vref

Re arrange C to units

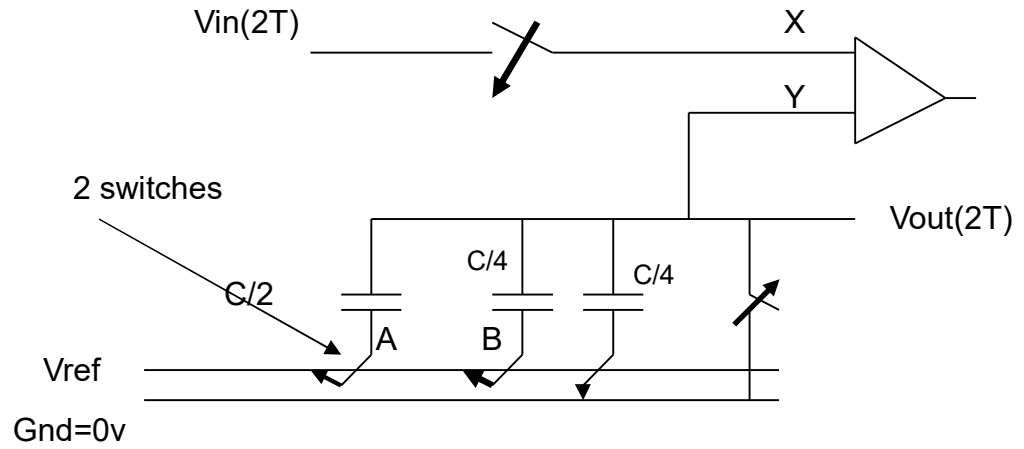

Generate $V_{ref}/2 + V_{ref}/4$

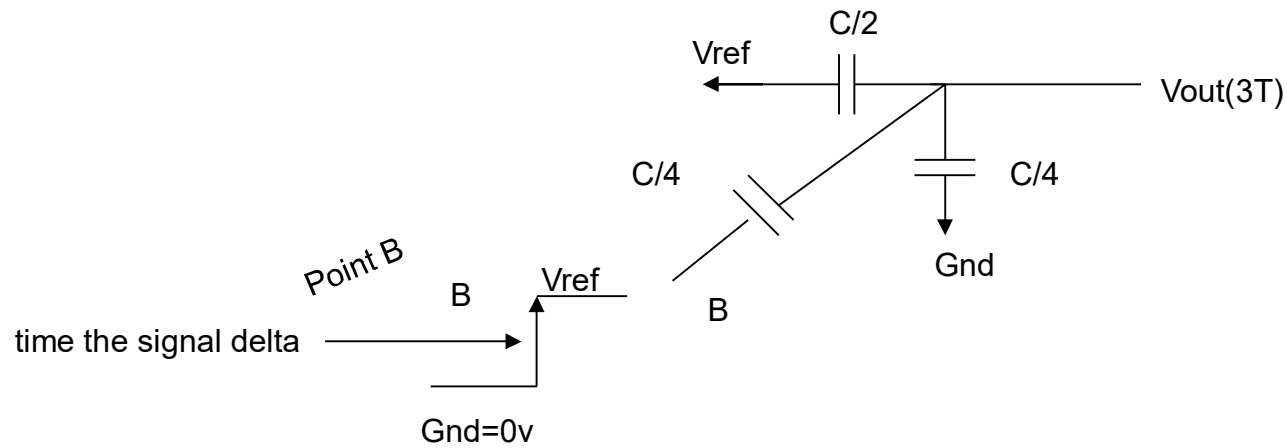

$$\Delta V_{out(3T)} = (0.25C / C) V_{ref}$$

$$\Delta V_{out(3T)} = 1/4 (\text{time the signal delta})$$


$$V_{out(3T)} = V_{ref(2T)} + 1/4 V_{ref}$$

$$\mathbf{V_{out(3T)} = V_{ref}/2 + V_{ref}/4}$$

Generate the Minus $\rightarrow V_{ref}/2 - V_{ref}/4$

in time = "3" add $-1/4 vref$


2 operations

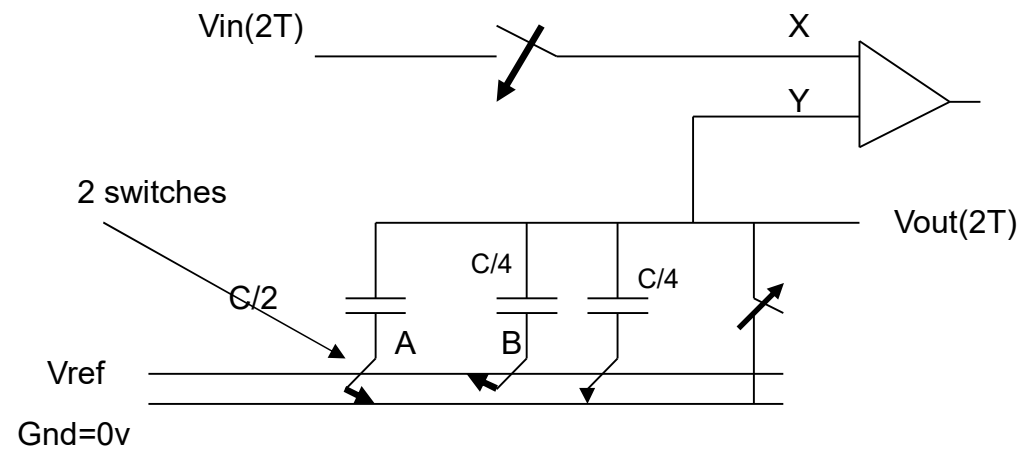

$$\Delta V_{out}(3T) = -0.5 + 0.25$$

$$V_{out}(3T) = V(2T) + -0.5 + 0.25$$


$$\Delta V_{out}(3T) = 1/4 V_{ref}$$

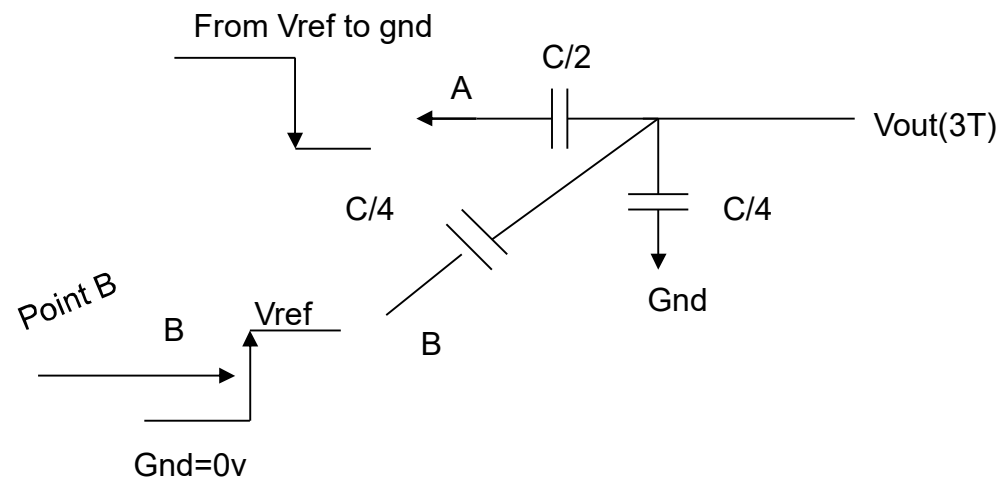


Generate the Minus of the Input as well Easily



$T=1$

 


$T=2$

 

And on.. And on.. Until the number of bits $M+1$

.... Let's Look at Charges SAR



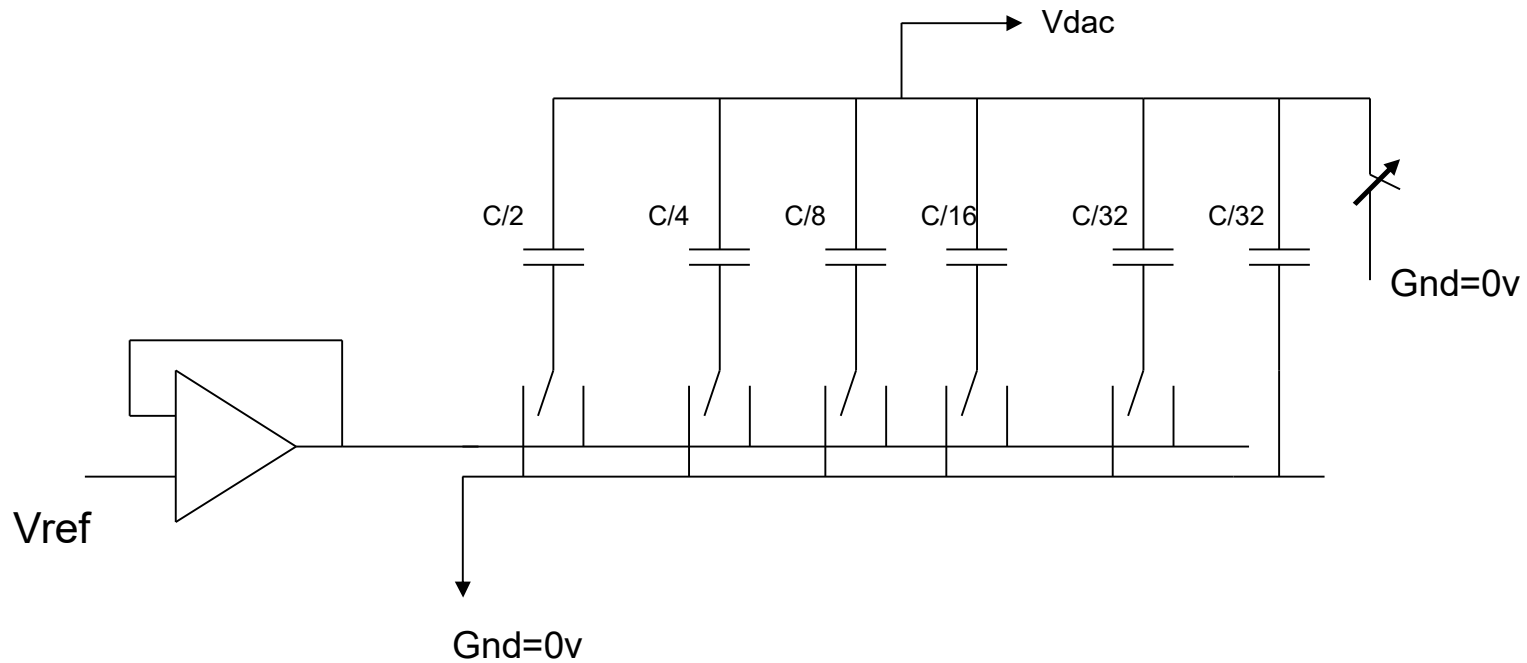


5bit dac

Fring. Caps to Improve Area Density (capacitors on IC)


   
$$C = C_o WL \longrightarrow \bar{C} = C_o WL + 2C_{fr} (W + L)$$




Accuracy in silicon is low ~ +/-20%

Low temperature/V dependency

Matched well. What about plate parasitic ?

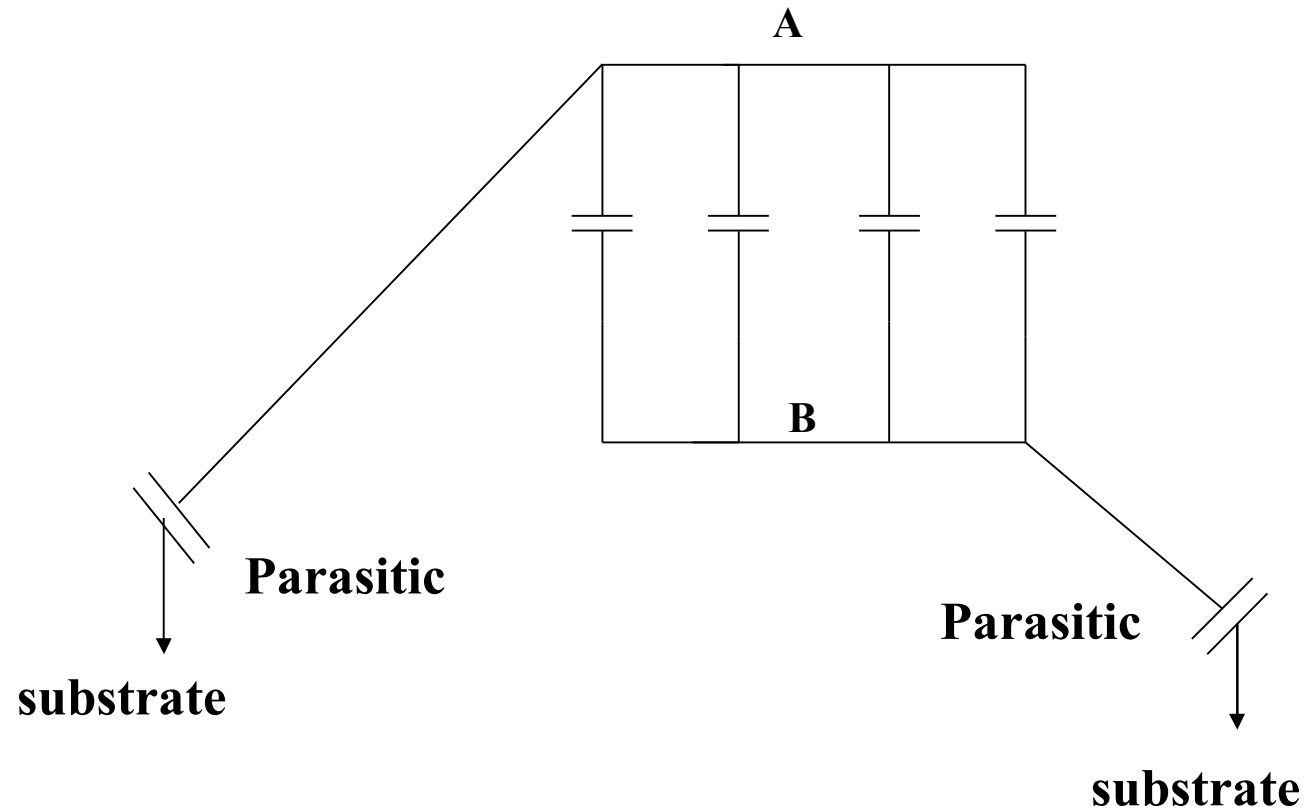$C_o = 1-2 \text{ ff/uu}$ if Metal to Metal sandwiched
With Fringing effect into the picture:



C parasitic $\sim 0.1-0.2C$ total! – how to design it out..



Capacitors from MOS (transistor) → triki.- watch the plates potential.

In accumulation (off) → $V_{gs} < V_t$ (n ch)


$$C = C_o WL$$

$C_o \sim 12\text{ff}$ if thin oxide is used (90nm)
Cap is to the substrate (N well probably)
In depletion (on) → $V_{gs} > V_t$


P can be in both

  

$$C = C_{ox}$$

 


 Cap is to the drain sources!
Next to V_t – C drops to ~ 0.3 its max value
It's a voltage dependent capacitor –
doesn't work good with 0 volt across it (integrator and opamp)





Why not work here ? – ah.. Veractor..

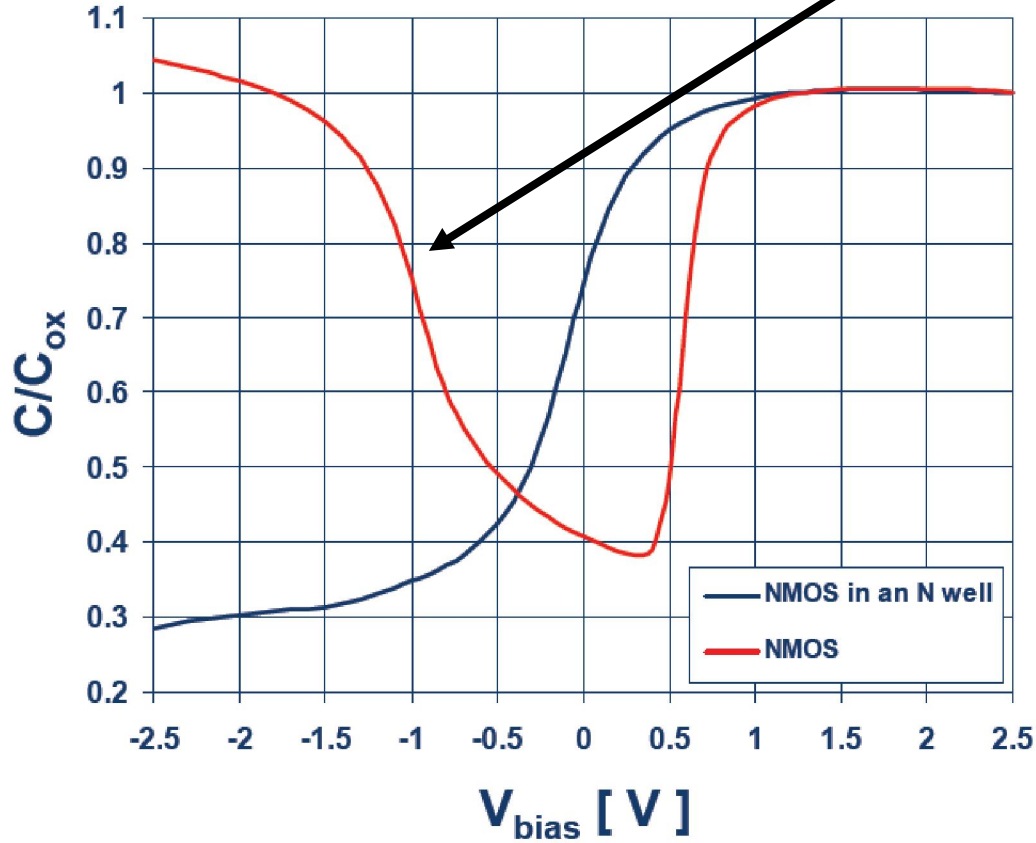

The NMOS capacitor is in inversion for $V > 0$.

Giovanni Anelli, CERN

- ❑ Its an accurate structure
- ❑ Subtraction using caps
- ❑ Low/average power: SH, one comparator, DAC, and Logic
- ❑ 8b-200msps is possible
- ❑ But: Need Accuracy in the DAC.
- ❑ Comparator offset $< \sim 0.5$ LSB – Easily calibrated

ACCURACY : FUNCTION OF DAC (CAPACITORS) MATCHING

$$C \approx \epsilon \frac{WL}{t} \longrightarrow \left(\frac{\Delta C}{C}\right)^2 = \left(\frac{\Delta \epsilon_r}{\epsilon_r}\right)^2 + \left(\frac{\Delta t_{\text{ox}}}{t_{\text{ox}}}\right)^2 + \left(\frac{\Delta L}{L}\right)^2 + \left(\frac{\Delta W}{W}\right)^2$$

- Once again can correlate to area with good accuracy
- How is it given

1. $A_{\Delta C/C}$ is based on sigma of $(\Delta C / C)$ vs. $1/\sqrt{WL}$
typ. number 2fF/micron square

To get to the best matched number you need to :

- ❖ Use identical geometries
- ❖ Use large unity capacitance (minimize fringing)
- ❖ Use common centroid arrangement
- ❖ Use dummy capacitors
- ❖ Use shielding
- ❖ Account for the connections' contribution
- ❖ Don't run connections over capacitor
- ❖ Place capacitor in low stress areas
- ❖ Place capacitors far from power devices

An Example

Find the LSB capacitor size (and total capacitors)
 for a 12b SAR ADC Given that 10ff unit match to 0.8%. (to 1 sigma)

$$C_{unit} = 10fF \quad \left(\frac{\Delta C}{C}\right)_{unit} = 0.8\%$$

$$\Delta_{noise} = \sqrt{\frac{\Delta^2}{12} + [Distortions]^2 + \frac{KT}{C_T}}$$

$$1pF \sim 64E^{-6} V / \sqrt{Hz}$$

Let give $[Distortions] \gg \frac{1}{3} LSB$ wight

$$\left[\frac{\Delta C}{C}\right]_{Full\ Scale} = \frac{1}{3} \left[\frac{1}{2^n - 1}\right] = 0.0081\%$$

$$\left[\frac{\Delta C}{C}\right]_{LSB} = [0.0081] \sqrt{2^n - 1} = 0.518\%$$


$$C_{LSB} = [C_{unit}] \left[\frac{0.8}{0.518}\right]^2 = 23.85fF$$

$$C_{total} = 97.67pF$$

Not to influency the converter


$$C_{LSB} = [C_{unit}] \frac{\left[\left(\frac{\Delta C}{C}\right)_{Full\ scale} \sqrt{2^n - 1}\right]^2}{\left[\left(\frac{\Delta C}{C}\right)_{unit}\right]^2}$$

 Example of Matching Requirement on F. Scale (MSBs)




2 to the n x 2/3
(2/3 only as example not to give all the error to the linearity)

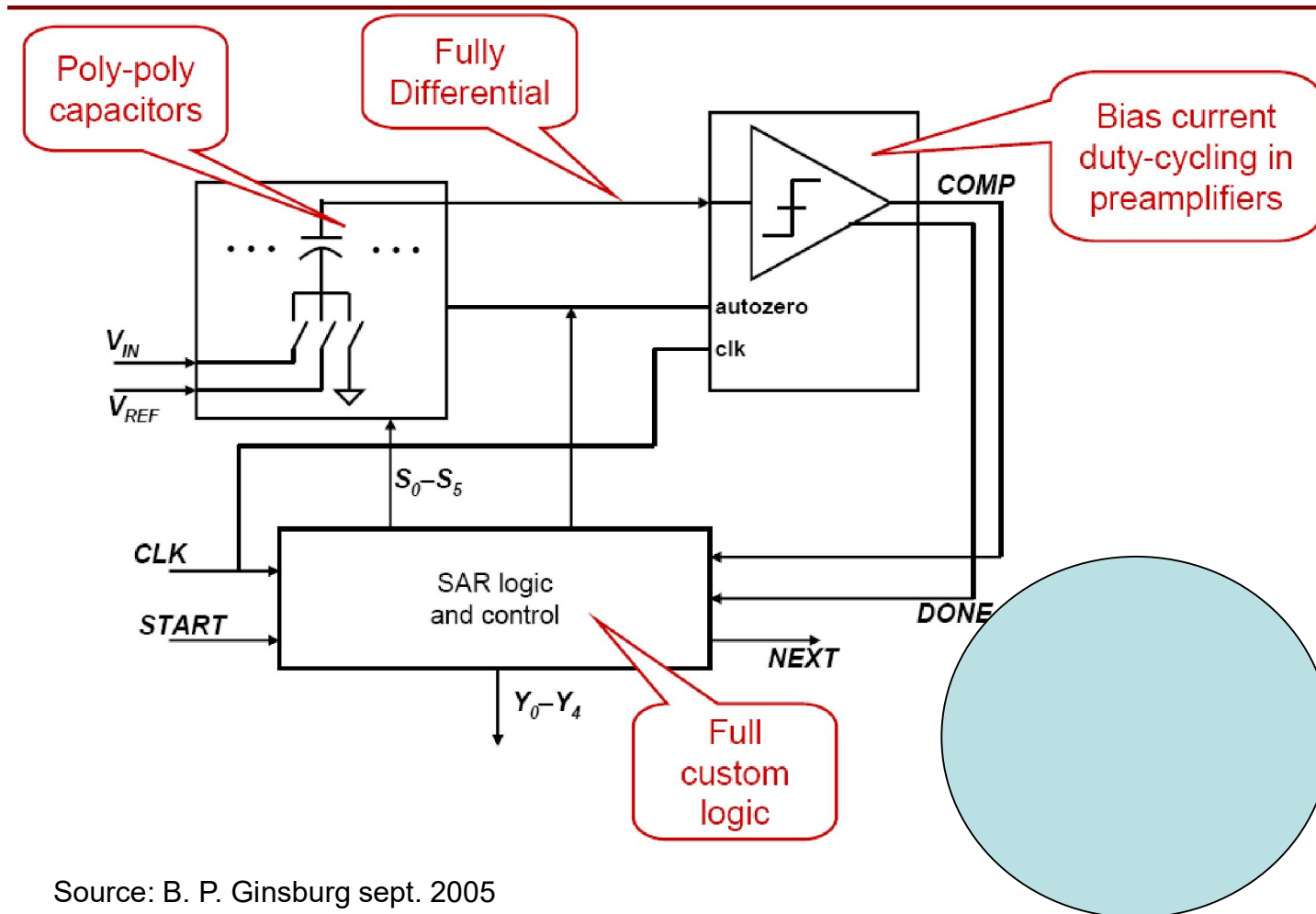How to Build One – What is Needed to Look for



Source: B. P. Ginsburg sept. 2005

 


References issues:

REFERENCE HOLDING BREF IS HARD TO DO:

During switching phase references
has to settle every clock (fast) They are op amp
driven therefore make the design almost as op-amp based

 Also the comparator must settle every cycle. (faster)



- ❑ Most time absolute value can move $\pm 15\%$ to $\pm 20\%$ and does not significantly matter but ratios do
- ❑ However, the bigger the area the better the matching
- ❑ Typical values 30ff can match 3-sigma to better $\sim 0.5\%$
- ❑ Matching is area dependent generally by the root of $(W \times L)$
- ❑ In SAR there is contradiction large is good for matching however speed is degraded a lot $R \text{ switch} \times C$ and its multiplied N bit for a complete cycle.

- Without amplifiers power is set by S/H, References, 1 comparator, and digital blocks+clocks
- Generally for lower number of bits – logic may be significant
- Area. For many bits analog set the power waist.
- Logic running multiple times for each conversion and capacitor size (forcing a large drive current)
- Power waist : S/H + Comparator + Reference + Switching/logic

Good:

- Lowest possible power- FOM
- Fewer analog elements,
- T/H or S/H drive low capacitance

- ❑ The Feed Back ADC (SAR) offers significant hardware savings compared to flash ADCs because the coarse Quantizer (comparator) resolution m can be much smaller than the converter resolution. N

- ❑ However, its suffer from drawbacks making it not suitable for many applications because:
 - ❑ It requires $p = N/m$ passes to generate N bit output words limiting the through put
 - ❑ It requires N ; bit accurate DAC
 - ❑ It requires faster settling elements
 - ❑ but No need amplifiers !

- ❑ **So, if speed is a problem should we combine SARs in time ??**

End Lecture 9