

Welcome to
7718 semester 1 2022
Mixed Signal Electronic Circuits

Instructor: Dr. Miki Moyal



Lectures

<http://www.gigalogchip.com/lectures.html>

Project suggestions.

Course Grading: 70%

A) 4 bits 2GS/s FLASH ADC

your target
ENOB=3.2bit

B) 10 bits 10MS/s SAR ADC

ENOB=9bit

C) D) 10gbps CDR

Jitter tolerance "pass" 10khz/10UI

D) 10Gbps transmitter with 5cm line

with Z-1 C+1 equalizer 0.1UI ISI

E) 10GHZ PLL

Design bw=1MHZ , ckin= 78.125MHz

- At the university we have a workstation with Cadence and a general 90nm PDK.
- Can use MATLAB/Simulink for the project.
- Can use Cadence Analog-Lib, mixed with its libraries

Requirements: for A and B Project

4 deliveries

a) Paper search: review, find at least 4 papers for showing this project: tabulate : Year, Power, FOM, Area, Architecture, type, enob, fs, CLOCK-RATE

(**Delivery 1: List and describe shortly the papers and compose a table to tabulate those parameters ~ 1-2page**)

b) Using Cadence, Excel, Matlab or any software you like : Build your architecture in ****high level**** . analysis (can be matlab/analoglib sim.) – show that it works (put an input sine Wave show the outputs digital bits (convert them to numbers and plot – DAC them).:

(**Delivery 2 : Build your Architecture, document it, ~ 2-3 pages. Resistors, Capacitors, comparator model, logic gate model**)

Delivery 3: Input a sine wave and show; Time plot input and output, frequency domain plot maximum input and output in frequency domain) calculate the SNRD,

(remember for SNR you need to do FFT)

Do only one of the below:

C1) Add to your model at least 1 error (linearity, or thermal noises, jitter) you can skew one resistor.. etc..

Show that it works: SNRD meet project spec

(**Delivery 4: show output and input in frequency domain calculate resulting SNRD)**

Or:

C2) Circuit design/analysis: take one block contain transistors (Comparator T&H..all-Logic)

Delivery4 : Show it in transistor levels.

Requirements: for C-D Project

4 Deliveries

a) Paper search: review, find at least 4 papers for showing this project: tabulate : Power, Area, Architecture type, clock rate

(**Delivery 1** : : List and describe shortly the papers and compose a table to tabulate those parameters ~ 1-2page)

(**Delivery 2** : Build- sketch your Architecture, document it, ~ 2-3 pages. You may use models like inverters VCOs, LPF, etc.

using CAD: Cadence, Excel, Matlab or any software you like : Build your architecture in ****high level**** . analysis (can be matlab/analoglib sim.) – show that it works (stable if cdr or pll,or use delivery 3)

Delivery 3: Input a random data or clock; show the output/s (data recovered, clock) **SHOW EYE DIAGRAMS** and time for data few bits.

Next:

Circuit design/analysis: take one block contain transistors (flip flops, Comparators, vco, phase detector ,charge pump, tx driver-inv+resistors)

Delivery4 : Show it in transistor levels explain how it works.

Basic parameters to choose for skew project

Take a generic sub micron CMOS if you have one if not make your own

For mismatch you can use 1 or more of those numbers

As in lect take capacitor mismatch as for 10 ff 0.8% ($C=1.5\text{ff}$ for $1\mu\text{m} \times 1\mu\text{m}$)

As in lec: Resistor mismatch for $1\mu\text{m} \times 1\mu\text{m}$ use 1 sigma 2% (400 ohm/square)

Offset: For transistor use for 1-sigma =4mv for $w \times l = 1\mu \times 1\mu$

Noise: For transistor noise use $2.7\text{nv}/\sqrt{g_m}$ for every $g_m=1\text{e-}3$

For jitter use 1% of the clock period as jitter

All resistors and capacitors range +/- 15% in absolute value

For project CDR use 512 random data skew the frequency 50000ppm

בהצלחה!